
 


# CMOS Timing

Last updated 12/23/23
 
# CMOS Timing

- Gate level timing
  - Each gate **input** has an equivalent input load factor
    - Models the input capacitance
    - Load equivalent (LE)
    - Technology / Process dependent




# CMOS Timing

- Gate level timing
  - Each gate has internal delay
    - Assumes no external load (just parasitics)
    - Circuit dependent – but fixed
    - Technology / Process dependent



$t_{pd\text{inv}}$

 


$t_{pd\text{nand}}$
 
# CMOS Timing

- Gate level timing
  - Each gate has a variable delay factor -  $r$ 
    - Function of the gate's drive capability
    - Modifies the circuit delay based on the amount of loading
    - Circuit dependent


$$t_{pd} = t_{pd_{gate}} + (r \times \# \text{ of LEs})$$



$$t_{pd} = t_{pd_{inv}} + r \times 1 \text{ LE}$$
 
# CMOS Timing

- Gate level timing
  - Long wires have enough capacitance to impact delays
    - Model long wires in terms of load equivalents (LEs)
    - Modifies the circuit delay based on the amount of loading
    - Circuit dependent



$$t_{pd} = t_{pd_{inv}} + (r \times (3 \text{ LE} + 1 \text{ LE}))$$


# CMOS Timing

- Gate level timing

$$t_{pd} = t_{\text{fixed\_delay}} + r_{\text{variable\_delay\_factor}} * \text{Load Equivalents}$$

Standard

Gate	INV	2-NAND	2-NOR	4-NAND	4-NOR
Input load factor (LE)	0.8	1.0	2.0	1.66	3.33
Fixed delay factor	50ps	65ps	65ps	80ps	80ps
Variable delay factor	5ps/LE	8ps/LE	8ps/LE	12ps/LE	12ps/LE

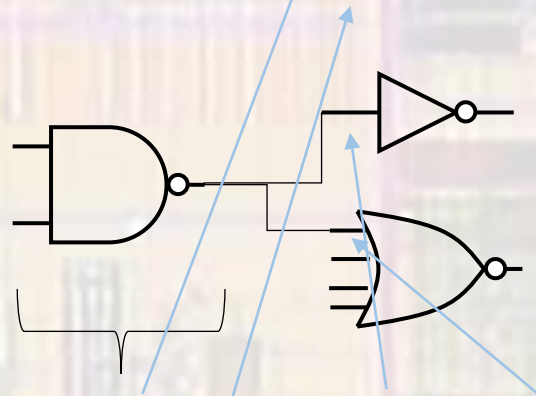

$$t_{pd} = 65\text{ps} + 8\text{ps/LE} * (0.8\text{LE} + 3.33\text{LE}) = 98\text{ps}^{**}$$

\*\* we are assuming interconnect capacitance is negligible


# CMOS Timing

- Gate level timing

$$t_{pd} = t_{\text{fixed\_delay}} + r_{\text{variable\_delay\_factor}} * \text{Load Equivalents}$$

Standard


Gate	INV	2-NAND	2-NOR	4-NAND	4-NOR
Input load factor (LE)	0.8	1.0	2.0	1.66	3.33
Fixed delay factor	50ps	65ps	65ps	80ps	80ps
Variable delay factor	5ps/LE	8ps/LE	8ps/LE	12ps/LE	12ps/LE

 





$$t_{pd} = 65ps + 8ps/LE * (0.8LE + 3.33LE + 3.0LE) = 122ps$$
 
# CMOS Timing

- Driving a Large Capacitive Load
  - Clk signals
  - Long wires
  - External circuitry



Moved the problem

    



 
# CMOS Timing

- Driving a Large Capacitive Load

- $N$  – number of stages
- $s$  – scale factor from stage to stage
- $C_{inv}$  – base inverter input capacitance
- $C_{load}$  – load capacitance
- $\gamma$  – Ratio of an inverters output capacitance to input capacitance (Typically  $\leq 1$ )
- $t_{p0}$  – base inverter delay




$$s = \sqrt[N]{C_{load} / C_{inv}}$$

$$t_{pd} = N t_{p0} \left( 1 + \frac{\sqrt[N]{C_{load} / C_{inv}}}{\gamma} \right)$$
 
# CMOS Timing

- Driving a Large Capacitive Load
  - How many stages?



$$s_{opt} = \exp\left(1 + \gamma/s_{opt}\right)$$

- Only has an analytic solution for  $\gamma = 0$

$$s_{opt} = e = 2.718 \quad N_{opt} = \ln\left(C_{load}/C_{inv}\right)$$


- For the more realistic value of  $\gamma = 1$

$$s_{opt} \approx 3.6 \quad N_{opt} = \log_{3.6}\left(C_{load}/C_{inv}\right)$$

# C-MOS Timing

- Switching speeds
  - Midpoint in, to midpoint out
    - $t_{phl}$ ,  $t_{plh}$
  - Assume only one device active
    - Charging/discharging the capacitor
- Devices start in saturation and transition to non-saturation

Details — not required

 

# C-MOS Timing

- Switching speeds

- Super simple estimation

- Assume in saturation up to the switching point

$$I = C \frac{dv}{dt} = \frac{k'_n W}{2 L} (V_{gs} - V_t)^2$$


$$I = C \frac{dv}{dt} = \frac{k'_n W}{2 L} (V_{dd} - V_t)^2$$

$$dt = C \frac{1}{\frac{k'_n W}{2 L} (V_{dd} - V_t)^2} dv$$

$$t_{nl} = C \frac{1}{\frac{k'_n W}{2 L} (V_{dd} - V_t)^2} \frac{V_{dd}}{2}$$

$$t_{pd} = t_{nl} + t_{lh}$$

Details — not required

 


$$t_{lh} = C \frac{1}{\frac{k'_p W}{2 L} (V_{dd} - V_t)^2} \frac{V_{dd}}{2}$$

# C-MOS Timing

- Switching speeds
  - Super simple estimation
    - Assume in saturation up to the switching point

Details – not required

 

$$t_{hl} = C \frac{1}{\frac{k'_n W}{2} \frac{V_{dd}}{L} (V_{dd} - V_t)^2}$$

$$t_{lh} = C \frac{1}{\frac{k'_p W}{2} \frac{V_{dd}}{L} (V_{dd} - V_t)^2}$$

$$t_{pd} = t_{hl} + t_{lh}$$

- Assuming N and P matched for switching point

$$t_{pd} = \frac{C V_{dd}}{\frac{k'_n W}{2} \frac{V_{dd}}{L} (V_{dd} - V_t)^2}$$

# C-MOS Timing

- Switching speeds
  - Super simple estimation
    - Assume in saturation upto the switching point
  - Matched devices

$$t_{pd} = \frac{C_{load} V_{dd}}{\frac{k'_n W}{2} \frac{V_{dd}}{L} (V_{dd} - V_t)^2}$$

- Reduce  $t_{pd}$ 
  - Increase  $V_{dd}$
  - Increase  $W/L$
  - Decrease  $C_{load}$

Increasing  $V_{dd}$  reduces gate delays  
→ higher operating frequency

