

Counters

Last updated 2/8/24

Counters

- Counters
 - Used as individual blocks
 - Used inside a block
 - Timers – delays, time-out, ...
 - Collectors – cash, presses, ...
 - Variations
 - Up, Down, Up-Down
 - Wrapping, non-wrapping
 - Modulo
 - Fixed size, n-bit
 - Fixed increment, m-increment

Counters

- Counter - n bit - unsigned

```
-- counter_unsigned_n_bit.vhdl
-- created 2/29/17
-- tj
-- rev 0
-----
-- n bit unsigned up-counter example
-----
-- Inputs: rstb, clk
-- Outputs: cnt[7:0]
-----
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
entity counter_unsigned_n_bit is
    generic(
        N: natural := 8
    );
    port (
        i_clk :    in std_logic;
        i_rstb :   in std_logic;

        o_cnt :    out std_logic_vector((N - 1) downto 0)
    );
end entity;
```

```
architecture behavioral of counter_unsigned_n_bit is
    -- internal signals
    signal cnt_sig:  unsigned((N - 1) downto 0);
begin
    counter: process(i_clk, i_rstb)
    begin
        -- reset
        if (i_rstb = '0') then
            cnt_sig <= (others => '0');
        -- rising clk edge
        elsif (rising_edge (i_clk)) then
            cnt_sig <= cnt_sig + 1;
        end if;
    end process;


    -- output logic
    o_cnt <= std_logic_vector(cnt_sig);
end behavioral;
```

why?
2 - reasons

cast

Counters

- Counter - n bit – unsigned – (default)

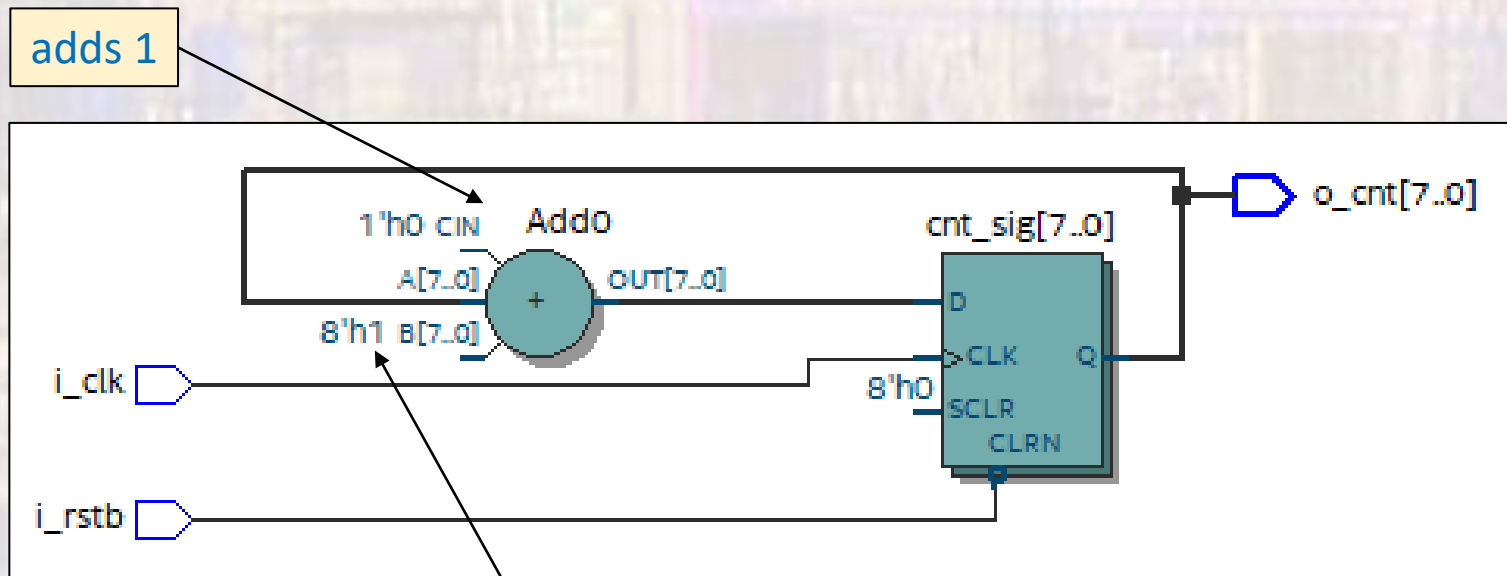

Format
num_bits ' format value
8'h1 → 8 bits, hex, value 1


Counters

- Counter - n bit – unsigned
 - Testbench - 6 bit version

```
-----  
-- counter_unsigned_n_bit_tb.vhdl  
--  
-- created: 1/26/18  
-- by: johnsontim  
-- rev: 0  
--  
-- testbench for n bit counter  
-- of counter_unsigned_n_bit.vhdl  
-- brute force implementation  
--  
-----  
library ieee;  
use ieee.std_logic_1164.all;  
entity counter_unsigned_n_bit_tb is  
  generic(  
    NUM_BITS: natural := 6  
  );  
  -- no ports - testbench  
end entity;
```

```
architecture testbench of counter_unsigned_n_bit_tb is  
  signal CLK: std_logic;  
  signal RSTB: std_logic;  
  
  signal CNT: std_logic_vector((NUM_BITS - 1) downto 0);  
  constant PER: time := 20 ns;  
  
  -----  
  -- Component prototype  
  -----  
  COMPONENT counter_unsigned_n_bit  
  generic(  
    N: natural := 4  
  );  
  PORT  
  (  
    i_rstb : IN STD_LOGIC;  
    i_clk  : IN STD_LOGIC;  
    o_cnt  : OUT STD_LOGIC_VECTOR((N - 1) downto 0)  
  );  
  END COMPONENT;  
  -----  
begin  
  
  -----  
  -- Device under test (DUT)  
  -----  
  DUT: counter_unsigned_n_bit  
  generic map(  
    N => NUM_BITS  
  )  
  port map(  
    i_rstb => RSTB,  
    i_clk  => CLK,  
    o_cnt  => CNT  
  );  
end;
```

```
-----  
-- Test processes  
-----  
  
-- Clock process  
clock: process -- no sensitivity list allowed  
begin  
  CLK <= '0';  
  wait for PER/2;  
  infinite: loop  
    CLK <= not CLK; wait for PER/2;  
  end loop;  
end process clock;  
  
-- Reset process  
reset: process -- no sensitivity list allowed  
begin  
  RSTB <= '0'; wait for 2*PER;  
  RSTB <= '1'; wait;  
end process reset;  
  
-- Run Process  
-- empty  
  
-----  
-- End test processes  
-----  
end architecture;
```

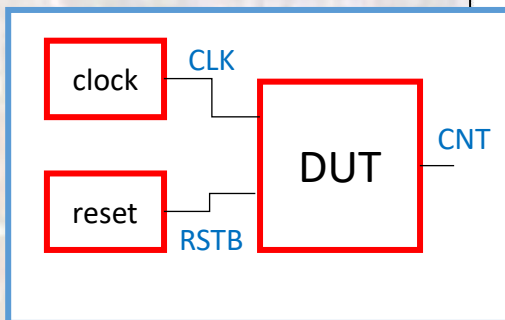


Counters


- Counter - n bit – unsigned
 - Testbench - 6 bit version

reset

counting

 

wrap

 

Counters

Mod counter

MOD x counts x times

Range $0 - (x - 1)$

Counters

- Mod 11 counter
 - Mod 11 only needs to compare 4 bits, no need to optimize the roll over test

```
-----  
-- counter_mod_11.vhdl  
--  
-- created 3/17/17  
-- tj  
--  
-- rev 0  
-----  
--  
-- mod 11 counter example  
-----  
--  
-- Inputs: rstb, clk  
-- Outputs: cnt[3:0]  
--  
-----  
library ieee;  
use ieee.std_logic_1164.all;  
use ieee.numeric_std.all;  
  
entity counter_mod_11 is  
  port (  
    i_clk : in std_logic;  
    i_rstb : in std_logic;  
  
    o_cnt : out std_logic_vector(3 downto 0)  
  );  
end entity;
```

```
architecture behavioral of counter_mod_11 is  
  --  
  -- internal signals  
  --  
  signal cnt_sig: unsigned(3 downto 0);  
  
begin  
  
  count: process(i_clk, i_rstb)  
  begin  
    --  
    -- reset  
    --  
    if (i_rstb = '0') then  
      cnt_sig <= (others => '0');  
    --  
    -- rising clk edge  
    --  
    elsif (rising_edge(i_clk)) then  
      if (cnt_sig < 10) then  
        cnt_sig <= cnt_sig + 1;  
      else  
        cnt_sig <= (others => '0');  
      end if;  
    end if;  
  end process;  
  
  --  
  -- Output logic  
  --  
  o_cnt <= std_logic_vector(cnt_sig);  
  
end behavioral;
```


Why < 10

Counters

- Mod 11 counter

Special adder (subtracts) and check for < 0
 $\text{cnt} - 10$ (4bit, hex a)


control selection of
 $\text{cnt}+1$ or 0

 

add 1

Counters

- Mod 11 counter
 - Testbench results

 

Counters

Up/Down counter

Counters




- up/down signed n-bit counter

```
-----  
-- counter_updn_signed_nb.vhdl  
-- created 2/29/17  
-- tj  
--  
-- rev 0  
-----  
-- n bit up/down signed counter example  
-----  
--  
-- Inputs: rstb, clk, dir  
-- Outputs: cnt[n-1:0]  
-----  
--  
-- counts up when dir = 0  
-- counts down when dir = 1  
-----  
library ieee;  
use ieee.std_logic_1164.all;  
use ieee.numeric_std.all;  
entity counter_updn_signed_nb is  
  generic(  
    N: natural := 8  
  );  
  port (  
    i_clk:   in std_logic;  
    i_rstb:  in std_logic;  
    i_dir:   in std_logic;  
  
    o_cnt :  out std_logic_vector((N - 1) downto 0)  
  );  
end entity;
```

```
architecture behavioral of counter_updn_signed_nb is  
  --  
  -- internal signals  
  --  
  signal cnt_sig:  signed((N - 1) downto 0);  
begin  
  count: process(i_clk, i_rstb)  
  begin  
    -- reset  
    --  
    if (i_rstb = '0') then  
      cnt_sig <= (others => '0');  
    --  
    -- rising clk edge  
    --  
    elsif (rising_edge(i_clk)) then  
      if(i_dir = '0') then  
        cnt_sig <= cnt_sig + 1;  
      else  
        cnt_sig <= cnt_sig - 1;  
      end if;  
    end if;  
  end process;  
  
  --  
  -- output logic  
  --  
  o_cnt <= std_logic_vector(cnt_sig);  
end behavioral;
```

Counters

- up/down signed n-bit counter (default 8 bit)

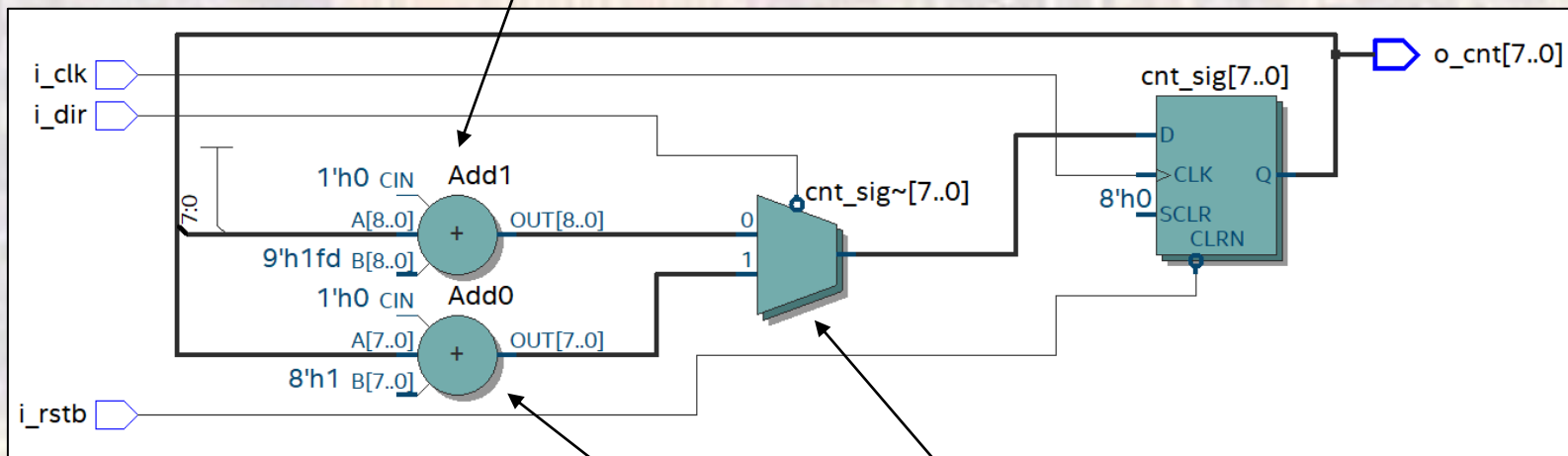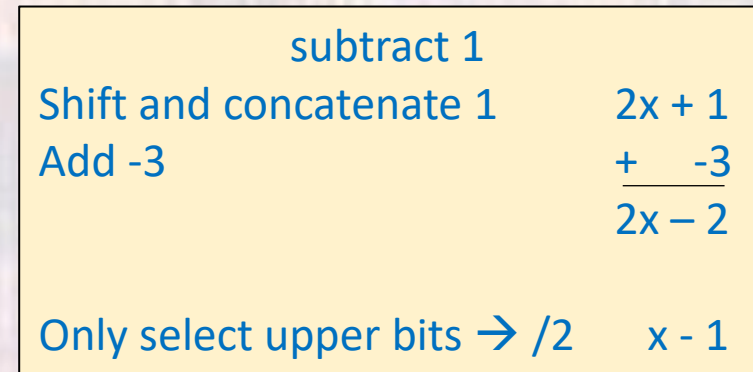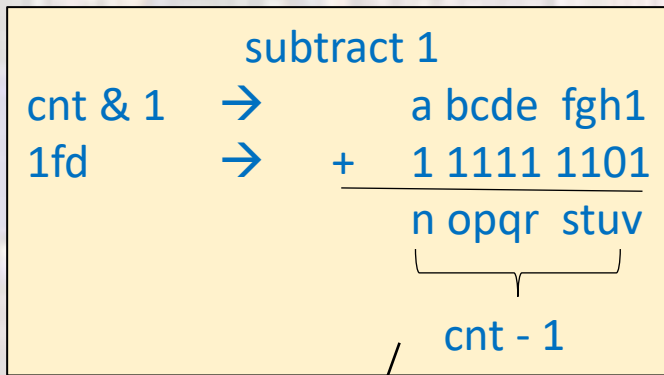

add 1

select + or -

Counters

- up/down signed n-bit counter
 - Testbench - 6 bit test

```

-----
-- counter_updn_signed_nb_tb.vhd1
--
-- created: 3/17/18
-- by: johnsontimoj
-- rev: 0
--
-- testbench for up down counter
-- of counter_updn_signed_nb.vhd1
-----
library ieee;
use ieee.std_logic_1164.all;

entity counter_updn_signed_nb_tb is
    generic(
        NUM_BITS: natural := 6
    );
    -- no port entry - testbench
end entity;
    
```

```

architecture testbench of counter_updn_signed_nb_tb is
    signal CLK: std_logic;
    signal RSTB: std_logic;
    signal DIR: std_logic;

    signal CNT: std_logic_vector((NUM_BITS - 1) downto 0);

    constant PER: time:= 20 ns;

    -----
    -- Component prototype
    -----
    COMPONENT counter_updn_signed_nb
        generic(
            N: natural := 8
        );
        port (
            i_clk: in std_logic;
            i_rstb: in std_logic;
            i_dir: in std_logic;

            o_cnt : out std_logic_vector((N - 1) downto 0)
        );
    END COMPONENT;

begin

    -----
    -- Device under test (DUT)
    -----
    DUT: counter_updn_signed_nb
        generic map(
            n => NUM_BITS
        )
        port map(
            i_clk => CLK,
            i_rstb => RSTB,
            i_dir => DIR,
            o_cnt => CNT
        );
    
```

```

-----
-- Test processes
-----


-- Clock process
clock: process -- no sensitivity list allowed
begin
    CLK <= '0';
    wait for PER/2;
    infinite: loop
        CLK <= not CLK; wait for PER/2;
    end loop;
end process clock;

-- Reset process
reset: process -- no sensitivity list allowed
begin
    RSTB <= '0'; wait for 2*PER;
    RSTB <= '1'; wait;
end process reset;

-- Run Process
run: process -- no sensitivity list allowed
begin
    -- initialize inputs
    DIR <= '0';
    -- run code
    wait for 68*PER;
    DIR <= '1';
    wait for 68*PER;
end process run;

-----
-- End test processes
-----

end architecture;
    
```

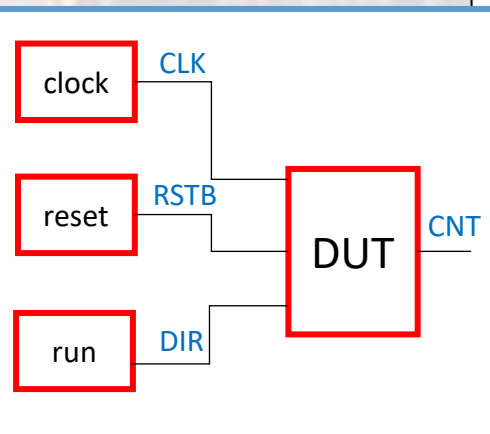


Counters

- up/down signed n-bit counter
 - Testbench - 6 bit


reset

counting up

 

transition to negative

transition to positive

 

counting down

