
 


Demultiplexors

Last updated 8/22/24

Demultiplexer

 - A demultiplexer routes the input to one of several outputs
 - Unused outputs are forced to '0'
 - The input and outputs can be single wires or busses



sel1	sel0	d	c	b	a
0	0	0	0	0	in
0	1	0	0	in	0
1	0	0	in	0	0
1	1	in	0	0	0

demultiplexor

- 4 output demultiplexor

```
-- demultiplexor_4.vhd1
-- created 8/22/24
-- tj
-----
-- demultiplexor examples for the notes
-----
-- inputs: data signal and 2 wire select
-- outputs: 4 data output signals
-----
library ieee;
use ieee.std_logic_1164.all;
entity demultiplexor_4 is
  port (
    i_in : in std_logic;
    i_sel : in std_logic_vector(1 downto 0);


    o_outa : out std_logic;
    o_outb : out std_logic;
    o_outc : out std_logic;
    o_outd : out std_logic
  );
end entity;
architecture behavioral of demultiplexor_4 is
  -- no internal signals
  begin
    demux : process(i_in, i_sel)
    begin
      case i_sel is
        when "00" => o_outa <= i_in ;
                    o_outb <= '0';
                    o_outc <= '0';
                    o_outd <= '0';

        when "01" => o_outa <= '0';
                    o_outb <= i_in;
                    o_outc <= '0';
                    o_outd <= '0';

        when "10" => o_outa <= '0';
                    o_outb <= '0';
                    o_outc <= i_in;
                    o_outd <= '0';

        when others => o_outa <= '0';
                      o_outb <= '0';
                      o_outc <= '0';
                      o_outd <= i_in;

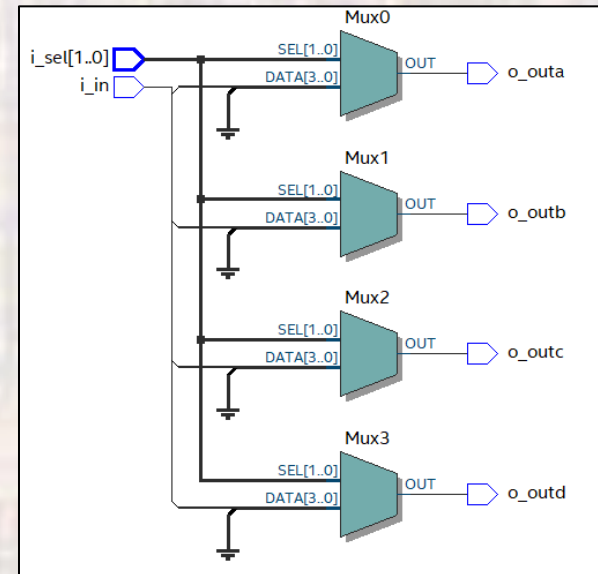      end case;
    end process;
  end architecture;
```




Demultiplexor

- n output demultiplexor – N must be a power of 2

```
-- demultiplexor_n.vhdl
-- created 8/22/24
-- tj
-----
-- demultiplexor examples for the notes
-----
-- inputs: data signal and log2(N) wire select
-- outputs: data outputs
-----
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
use ieee.math_real.all;

entity demultiplexor_n is
  generic(
    N : natural := 8
  );
  port (
    i_data_in : in std_logic;
    i_sel      : in std_logic_vector((integer(ceil(log2(real(N)))) - 1) downto 0);
    o_data_out : out std_logic_vector((N - 1) downto 0)
  );
end entity;

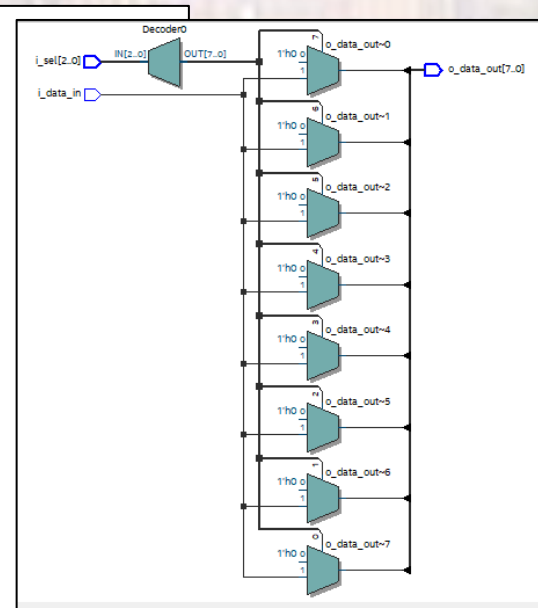architecture behavioral of demultiplexor_n is
  -- no internal signals
  begin
    demux_n : process(i_data_in, i_sel)
    begin
      o_data_out <= (others => '0'); -- force non-selected outputs to 0
      o_data_out(to_integer(unsigned(i_sel))) <= i_data_in;
    end process;
  end architecture;
```



although the data outputs are configured as a vector – they would be connected as individual wires

Demultiplexor


- n input demultiplexor – check if N is a power of 2

```
-- demultiplexor_n.vhdl
-- created 8/22/24
-- tj
-----
-- demultiplexor examples for the notes
-----
-- inputs: data signal and log2(N) wire select
-- outputs: data outputs
-----
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
use ieee.math_real.all;

entity demultiplexor_n is
  generic(
    N : natural := 8
  );
  port (
    i_data_in  : in std_logic;
    i_sel      : in std_logic_vector((integer(ceil(log2(real(N)))) - 1) downto 0);
    o_data_out : out std_logic_vector((N - 1) downto 0)
  );
end entity;

architecture behavioral of demultiplexor_n is
  -- no internal signals
  begin
    -- Assert that N is a power of 2
    assert (integer(log2(real(N))) = (integer(ceil(log2(real(N))))))
    report "Error: multiplexor_n generic:N must be a power of 2"
    severity error;

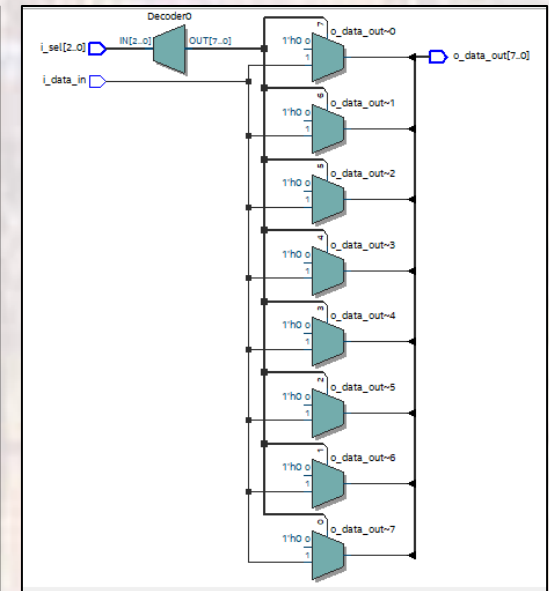    demux_n : process(i_data_in, i_sel)
    begin
      o_data_out <= (others => '0'); -- force non-selected outputs to 0
      o_data_out(to_integer(unsigned(i_sel))) <= i_data_in;
    end process;
  end architecture;
```



Create a compiler error
if N is NOT a power of 2

Demultiplexor

- bus demultiplexor – 8 wire, 4 way

```

-- demultiplexor_bus8_4.vhd
-- created 8/22/24
-- tj
-----
-- demultiplexor examples for the notes
-----
-- inputs: 8 wire data bus signal, 2 wire select
-- outputs: 4, 8 wire data bus outputs
-----
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
use ieee.math_real.all;

entity demultiplexor_bus8_4 is
  port (
    i_in : in std_logic_vector(7 downto 0);
    i_sel : in std_logic_vector(1 downto 0);

    o_outa : out std_logic_vector(7 downto 0);
    o_outb : out std_logic_vector(7 downto 0);
    o_outc : out std_logic_vector(7 downto 0);
    o_outd : out std_logic_vector(7 downto 0)
  );
end entity;



architecture behavioral of demultiplexor_bus8_4 is
  -- no internal signals
begin
  demux : process(i_in, i_sel)
  begin
    case i_sel is
      when "00" => o_outa <= i_in ;
                   o_outb <= "00000000";
                   o_outc <= "00000000";
                   o_outd <= "00000000";

      when "01" => o_outa <= std_logic_vector(to_unsigned(0,8));
                   o_outb <= i_in;
                   o_outc <= std_logic_vector(to_unsigned(0,8));
                   o_outd <= std_logic_vector(to_unsigned(0,8));

      when "10" => o_outa <= (others => '0');
                   o_outb <= (others => '0');
                   o_outc <= i_in;
                   o_outd <= (others => '0');

      when others => o_outa <= "00000000";
                    o_outb <= "00000000";
                    o_outc <= "00000000";
                    o_outd <= i_in;
    end case;
  end process;
end architecture;

```

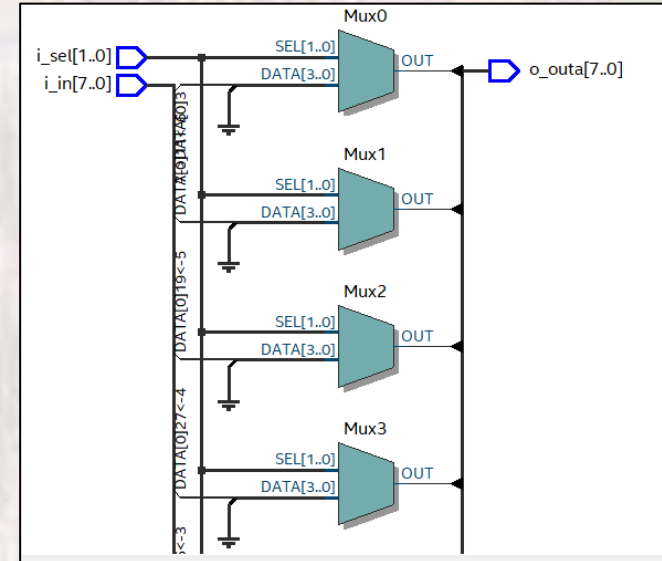 

multiple ways to set the unselected outputs to 0

Demultiplexor

- bus demultiplexor – M wire, N way

see if you can do this