

Domain Crossing

Last updated 1/25/24



Domain Crossing

- Primary (Modern) Logic Domains
 - Supply voltage (logic levels)
 - Clock Frequency and/or synchronicity
 - Single vs. Differential signaling

Domain Crossing


- Logic Level Review

  - V_{OH} , V_{OL} must be 'outside' V_{IH} , V_{IL} for guaranteed signal transfer between gates



Domain Crossing

 - Voltage Domain Crossing
 - 3.3V CMOS or LVTTTL → 5V TTL
 - No issues
 - 5V TTL → 3.3V CMOS or LVTTTL
 - Overdrive inputs
 - Need a buffer
 - 3.3V CMOS <-> 2.5V CMOS <-> 1.8V CMOS
 - Level mismatches
 - Need a buffer
 - Example buffer circuit




Domain Crossing

- Clock Domain Crossing
 - No design level guarantee that the asynchronous data coming from the source will not violate the sink's setup or hold time
 - Output from the sink's receiver flip-flop is unpredictable
 - Called Metastability
 - Output may switch states multiple times due to failed setup/hold timing

Domain Crossing

- Clock Domain Crossing
 - Metastability

 

Domain Crossing

- Clock Domain Crossing
 - Metastability

