 


Simple Finite State Machines

Last updated 7/18/23

Simple FSMs

- Finite State Machine
 - Moore Machine
 - Outputs depend only on the current state(S)




Simple FSMs

- Finite State Machine

- Mealy Machine

 - Outputs depend on the current state(S) and the inputs



Simple FSMs

- Finite State Machine
 - To create an FSM in VHDL you combine
 - Enumerated types
 - Simple register logic
 - Combinatorial logic (process)
 - Reset
 - Enumerated type
 - User defined type that only has the allowed states as values

```
type STATETYPE is (rst,A,B,C,D,E,F,G,det);
signal state:      STATETYPE;
signal state_next: STATETYPE;
```

Allowed state names

State signals of the enumerated type
Can only have the values associated with the states


Simple FSMs

- Finite State Machine
 - Rules
 - Ensure that all states have entry and exit conditions
 - Ensure that all states are covered in the code
 - An abstraction of the FSM is used for RTL simulation
 - You cannot see the next state/register logic

Simple FSMs

- Sequence detector - CD

- Detecting 11001101

 

Simple FSMs

- Sequence detector - CD

```
-- sequence_detector_CD_fsm.vhd1
-- created 4/12/2018
tj
-- rev 0
-----
-- sequence detector state machine
-----
-- Inputs: rstb, clk, Din
-- Outputs: Detect
-----

library ieee;
use ieee.std_logic_1164.all;

entity sequence_detector_CD_fsm is
  port (
    i_clk:      in std_logic;
    i_rstb:     in std_logic;
    i_D:        in std_logic;

    o_Detect:   out std_logic
  );
end entity;

architecture behavioral of sequence_detector_CD_fsm is

  -- internal signals
  --
  type STATETYPE is (rst,A,B,C,D,E,F,G,det);
  signal state:      STATETYPE;
  signal state_next: STATETYPE;

begin
```


```
-- next state logic
--
process(all)
begin
  case state is
    when rst =>
      if i_D = '1' then
        state_next <= A;
      else
        state_next <= rst;
      end if;
    when A =>
      if i_D = '1' then
        state_next <= B;
      else
        state_next <= rst;
      end if;
    when B =>
      if i_D = '0' then
        state_next <= C;
      else
        state_next <= B;
      end if;
    when C =>
      if i_D = '0' then
        state_next <= D;
      else
        state_next <= A;
      end if;
    when D =>
      if i_D = '1' then
        state_next <= E;
      else
        state_next <= rst;
      end if;
    when E =>
      if i_D = '1' then
        state_next <= F;
      else
        state_next <= rst;
      end if;
    when F =>
      if i_D = '0' then
        state_next <= G;
      else
        state_next <= B;
      end if;
    when G =>
      if i_D = '1' then
        state_next <= det;
      else
        state_next <= D;
      end if;
    when others =>
      state_next <= rst;
  end case;
end process;
```

Simple FSMs

- Sequence detector - CD

```
-- Register logic
process(i_clk, i_rstb)
begin
    -- reset
    if (i_rstb = '0') then
        state <= rst;
    -- rising clk edge
    elsif (rising_edge(i_clk)) then
        state <= state_next;
    end if;
end process;
```

```
-- next state logic
process(all)
begin
    case state is
        when rst =>
            if i_D = '1' then
                state_next <= A;
            else
                state_next <= rst;
        when A =>
            if i_D = '1' then
                state_next <= B;
            else
                state_next <= rst;
        when B =>
            if i_D = '0' then
                state_next <= C;
            else
                state_next <= B;
        when C =>
            if i_D = '0' then
                state_next <= D;
            else
                state_next <= A;
        when D =>
            if i_D = '1' then
                state_next <= E;
            else
                state_next <= rst;
        when E =>
            if i_D = '1' then
                state_next <= F;
            else
                state_next <= rst;
        when F =>
            if i_D = '0' then
                state_next <= G;
            else
                state_next <= B;
        when G =>
            if i_D = '1' then
                state_next <= det;
            else
                state_next <= D;
        when others =>
            state_next <= rst;
    end case;
end process;
```

 


```
-- output logic
process(state)
begin
    case state is
        when rst => o_Detect <= '0';
        when A  => o_Detect <= '0';
        when B  => o_Detect <= '0';
        when C  => o_Detect <= '0';
        when D  => o_Detect <= '0';
        when E  => o_Detect <= '0';
        when F  => o_Detect <= '0';
        when G  => o_Detect <= '0';
        when det => o_Detect <= '1';
        when others => o_Detect <= '0';
    end case;
end process;
```

end behavioral;


Simple FSMs

- Sequence detector - CD

 


Simple FSMs

- Sequence detector - CD

 


Simple FSMs

- Sequence detector - CD

 

full sequence

re-start

 

repeat B


Back to start

Back to A

Back to start

Simple FSMs

 - Priority Stoplight
 - Stays in current mode if traffic is detected in that direction



Simple FSMs

- Priority Stoplight

```
-- stoplight_nsew_fsm.vhd1
-- created 3/30/18
-- tj
-- rev 0
-- NS/EW Stoplight
-- 
-- Inputs: rstb, clk, TNS, TEW
-- Outputs: lights_ew, lights_ns
-- 

library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity stoplight_nsew_fsm is
  port (
    i_clk :      in std_logic;
    i_rstb :     in std_logic;
    i_tns :      in std_logic;
    i_tew :      in std_logic;

    o_lights_ns : out std_logic_vector(1 downto 0);
    o_lights_ew : out std_logic_vector(1 downto 0)
  );
end entity;
```

```
architecture behavioral of stoplight_nsew_fsm is
  --
  -- internal signals
  --
  type STATE_TYPE is (GR, YR, RG, RY);
  signal state:        STATE_TYPE;
  signal state_next:   STATE_TYPE;

  constant R : std_logic_vector(1 downto 0) := "11";
  constant Y : std_logic_vector(1 downto 0) := "10";
  constant G : std_logic_vector(1 downto 0) := "01";

begin
  --
  -- next state logic
  --
  process(all)
  begin
    case state is
      when GR =>
        if(i_tns = '1') then
          state_next <= GR;
        else
          state_next <= YR;
        end if;
      when YR =>
        state_next <= RG;
      when RG =>
        if(i_tew = '1') then
          state_next <= RG;
        else
          state_next <= RY;
        end if;
      when others =>
        state_next <= GR;
    end case;
  end process;
```

Simple FSMs


- Priority Stoplight

```
-- Register logic
--
process(i_clk, i_rstb)
begin
    -- reset
    if (i_rstb = '0') then
        state <= GR;
    -- rising clk edge
    elsif (rising_edge(i_clk)) then
        state <= state_next;
    end if;
end process;

-- Output logic
--
process(all)
begin
    case state is
        when GR =>
            o_lights_ns <= G;
            o_lights_ew <= R;
        when YR =>
            o_lights_ns <= Y;
            o_lights_ew <= R;
        when RG =>
            o_lights_ns <= R;
            o_lights_ew <= G;
        when others =>
            o_lights_ns <= R;
            o_lights_ew <= Y;
    end case;
end process;
end behavioral;
```


Simple FSMs

- Priority Stoplight

 

Simple FSMs

- Priority Stoplight

 

normal cycle



N/S Priority