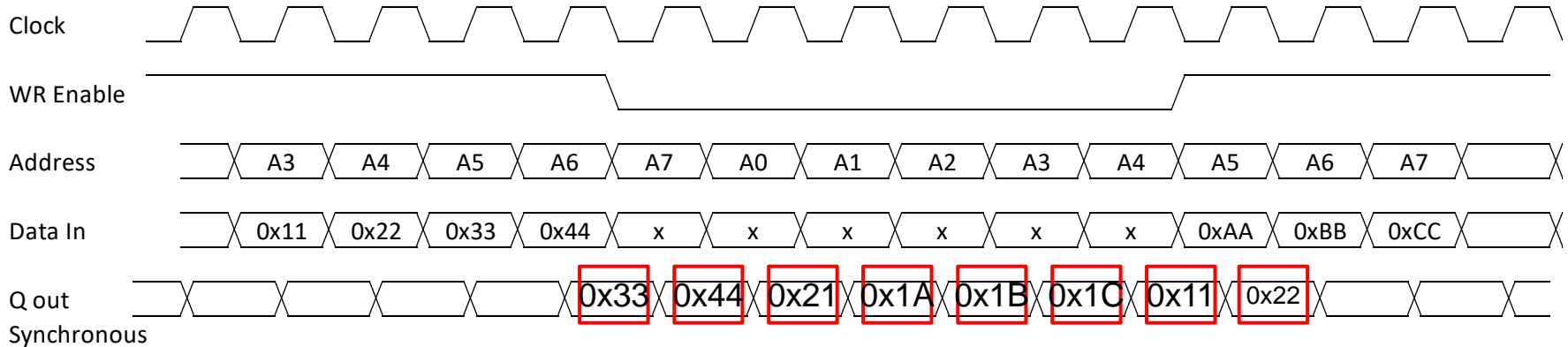


1 - Simple single port memory: Given the timing diagram below for the simple single port memory, **fill in the values for the empty boxes on the diagram and the final memory values.** Assume a new data output model 40 pts



	Mem Hex BEFORE	Mem Hex AFTER
A0	0x1A	0x1A
A1	0x1B	0x1B
A2	0x1C	0x1C
A3	0x1D	0x11
A4	0x1E	0x22
A5	0x1F	0xAA
A6	0x20	0xBB
A7	0x21	0xCC

2 - Review the Max10 spec and provide the ranges for n and m in the PLLs. Calculate the greatest multiply possible, the greatest divide possible, and the closest frequency to the original clock that can be created (that is not the same as the original clock) **Note – assume the C dividers = 1** 10 pts

$$600\text{Hz} < f_{\text{VCO}} < 1.3\text{GHz}$$

$$f_{\text{VCO}} = f_{\text{REF}} \times m = f_{\text{IN}} \frac{m}{n}$$

N: 1 to 512
M: 1 to 512

Biggest multiple	512
Biggest Divide	1/512
Closest value	511/512 or 512/511

3 - Create a 7bit x 9bit multiplier using the Mega Wizard

a) Provide your module code

10 pts

b) Provide an RTL schematic

10 pts

c) Create a testbench that runs all input combinations (do not create an exhaustive list – use a loop or similar construct)

20 pts

d) Provide your testbench code

127x511

10 pts

```

--- multiplier_7x9.vhdl
--- by: johnsontimoj
--- created: 8/17/2018
--- version: 0.0
---
-----
---
--- Multiplier 7 x 9 for HW
--- inputs: multiplier, multiplicand
--- outputs: product
---
-----

library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity multiplier_7x9 is
  port (
    i_multiplicand: in std_logic_vector(6 downto 0);
    i_multiplier:   in std_logic_vector(8 downto 0);
    o_product:     out std_logic_vector(15 downto 0)
  );
end entity;


```

```

architecture behavioral of multiplier_7x9 is
  component mult_7x9
  PORT
  (
    dataa    : IN STD_LOGIC_VECTOR (6 DOWNT0 0);
    datab   : IN STD_LOGIC_VECTOR (8 DOWNT0 0);
    result   : OUT STD_LOGIC_VECTOR (15 DOWNT0 0)
  );
  end component;

begin
  dut1 : mult_7x9
  PORT MAP (
    dataa    => i_multiplicand,
    datab   => i_multiplier,
    result   => o_product
  );
end architecture;

```

 

```

-- run process
run: process
begin
  -- Initialize values
  MULTIPLICAND <= (others => '0');
  MULTIPLIER <= (others => '0');

  wait for 2*PER;

  for i in 0 to 127 loop
    for j in 0 to 511 loop
      MULTIPLICAND <= std_logic_vector(to_unsigned(i,7));
      MULTIPLIER <= std_logic_vector(to_unsigned(j,9));
      wait for 1*PER;
    end loop;
  end loop;
end process;

```

0x

	Msgs												
/multiplier_7x9_tb/MULTIPLICAND	0	0											
/multiplier_7x9_tb/MULTIPLIER	48	0	1	2	3	4	5	6	7	8	9	10	
/multiplier_7x9_tb/PRODUCT	0	0											

4x

	Msgs												
/multiplier_7x9_tb/MULTIPLICAND	10	4											
/multiplier_7x9_tb/MULTIPLIER	428	284		285		286			287			288	
/multiplier_7x9_tb/PRODUCT	4280	1136		1140		1144			1148			1152	

Max values

	Msgs												
/multiplier_7x9_tb/MULTIPLICAND	127	127											
/multiplier_7x9_tb/MULTIPLIER	511	505	506	507	508	509	510	511					
/multiplier_7x9_tb/PRODUCT	64897	64135	64262	64389	64516	64643	64770	64897					