


1 – Analysis: Create a table of the **calculated** expected v_{in} from 0V to 5V in 0.5V increments.

Note: be sure to confirm the NMOS operating

NOTE: $V_{dsat} = V_{GS} - V_t$

General approach:
 Check for cutoff
 Assume sat – find I_D , calc V_{DS}
 check V_{dsat}
 If fails – Solve linear eqn for V_{DS}
 2 solutions
 put back in eqn
 only 1 should work

 Specific approach:
 $V_{DS} = V_{DD} - I_D \cdot R_1$




Specific approach:
 In this case we know that when V_{in} is just above V_t we will get a small current \rightarrow V_{DS} still very large \rightarrow sat – find I_D , calc V_{DS}
 check V_{dsat}
 If fails – Solve linear eqn for V_{DS}
 2 solutions
 put back in eqn
 only 1 should work

$V_t = 1v$
 $K_n' = 2e-3A/V^2$
 $W/L = 1$

Vin	ID	VDS	Mode
0	0.00E+00	5.000	cutoff
0.5	0.00E+00	5.000	cutoff
1	0.00E+00	5.000	cutoff
1.5	2.50E-04	4.625	sat
2	1.00E-03	3.500	sat
2.5	2.25E-03	1.625	sat
3	2.75E-03	0.880	lin
3.5	2.89E-03	0.667	lin
4	2.97E-03	0.544	lin
4.5	3.02E-03	0.463	lin
5	3.06E-03	0.403	lin

 - 2 – Create a truth table and a SOP or POS logic equation for the circuit below .
This is called a compound gate. 30pts



A	B	C	OUT
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0

$$a'b'c' + a'bc' + ab'c'$$

3 – Use DeMorgan’s theorem to reduce the logic equation in problem 2.


Implement the solution with NANDs, NORs, and Inverters. Compare the 6-transistor solution in problem 2 to your solution above with respect to area and speed
30pts

$$a'b'c' + a'bc' + ab'c'$$

$$a'c'(b + b') + ab'c'$$

$$a'c' + ab'c'$$

$$c'(a' + ab')$$

 

$$\overline{c + (a' + ab')}$$

$$\overline{c + a(\overline{ab'})}$$

$$\overline{c + a(a' + b)}$$

$$\overline{c + aa' + ab}$$

$$\overline{c + ab}$$

$$\overline{\overline{c + ab}}$$

Compound gate is:

Faster (1 delay vs. 3 delays)

Smaller (6T vs. 10T)

Most logic libraries include a large number of compound gates