

- 1 – Create VHDL code and RTL for a D-FF with asynchronous resetb and synchronous set. Follow all best practices.

20pts

```

-----
-- ff_d_syncs.vhdl
--
-- created 2/1/2018
-- tj
--
-- rev 0
-----
--
-- special DFF with synchronous set
-----
--
-- Inputs: clk, rstb, d, t
-- Outputs: q
-----
library ieee;
use ieee.std_logic_1164.all;

entity ff_d_syncs is
  port (
    i_clk : in std_logic;
    i_rstb : in std_logic;
    i_D : in std_logic;
    i_set : in std_logic;
    o_Q : out std_logic
  );
end entity;

```


```

architecture behavioral of ff_d_syncs is
begin
  process(i_clk, i_rstb)
  begin
    if (i_rstb = '0') then
      o_Q <= '0';
    elsif (rising_edge(i_clk)) then
      if (i_set = '0') then
        o_Q <= i_D;
      else
        o_Q <= '1';
      end if;
    end if;
  end process;
end behavioral;

```

async resetb

sync set

 

2 – Create VHDL code and RTL for a JK-FF with synchronous resetb and

30pts

```

-- ff_jk_special.vhdl
-- created 2/1/2018
-- tj
-- rev 0
-----
-- JK flip-flop w/ sync resetb and asy set
-----
--
-- Inputs: clk, rstb, j, k
-- Outputs: q, qb
-----
library ieee;
use ieee.std_logic_1164.all;

entity ff_jk_special is
  port (
    i_clk : in std_logic;
    i_rstb : in std_logic;
    i_set : in std_logic;
    i_J : in std_logic;
    i_K : in std_logic;


    o_Q : out std_logic;
    o_Qb : out std_logic;
  );
end entity;
    
```

```

architecture behavioral of ff_jk_special is
begin
  process(i_clk, i_set)
  begin
    if (i_set = '1') then
      o_Q <= '1';
      o_Qb <= '0';
    elsif (rising_edge(i_clk)) then
      if (i_rstb = '0') then
        o_Q <= '0';
        o_Qb <= '1';
      elsif ((i_J = '0') and (i_K = '0')) then
        o_Q <= o_Q;
        o_Qb <= o_Qb;
      elsif ((i_J = '0') and (i_K = '1')) then
        o_Q <= '0';
        o_Qb <= '1';
      elsif ((i_J = '1') and (i_K = '0')) then
        o_Q <= '1';
        o_Qb <= '0';
      elsif ((i_J = '1') and (i_K = '1')) then
        o_Q <= not o_Q;
        o_Qb <= not o_Qb;
      else
        o_Q <= o_Q;
        o_Qb <= o_Qb;
      end if;
    end if;
  end process;
end behavioral;
    
```

async set

sync resetb

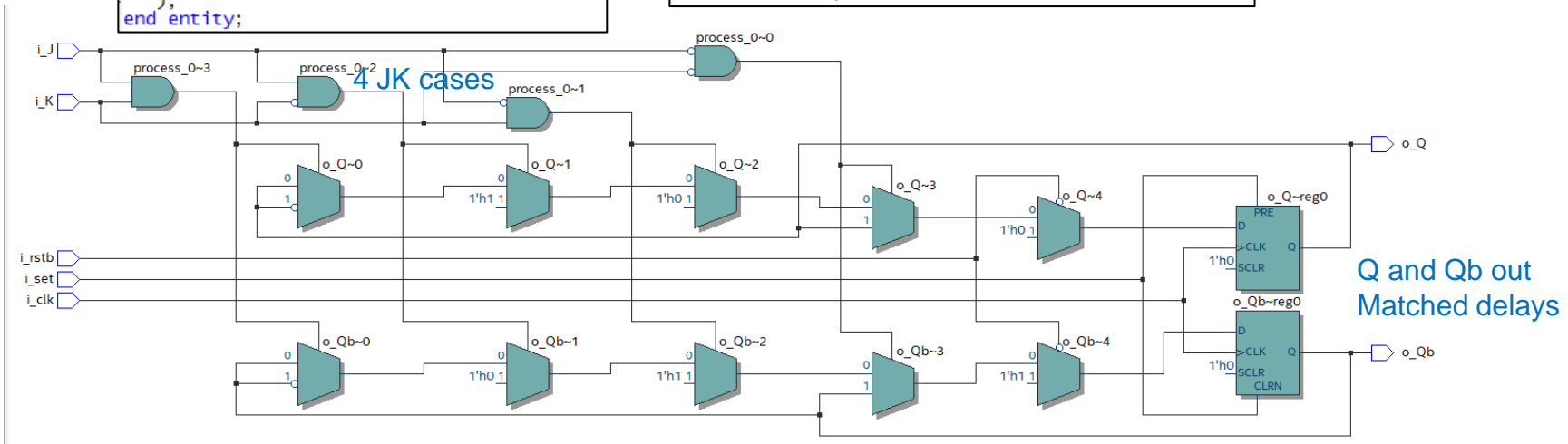

- 3 – Create VHDL code and RTL for a special new FlipFlop you have conceived of – this is a normal D-FF (with async rstb) but has a second data input called Toggle(T). When T is low, the DFF operates normally, when T is high, the DFF ignores the D input and synchronously toggles the output. Follow all best practices. 50pts

```

--
-- ff_d_t.vhdl
--
-- created 2/1/2018
-- tj
--
-- rev 0
--
-- special DFF with toggle mode
--
-----
--
-- Inputs: clk, rstb, d, t
-- Outputs: q
--
-----
library ieee;
use ieee.std_logic_1164.all;

entity ff_d_t is
    port (
        i_clk : in std_logic;
        i_rstb : in std_logic;
        i_D : in std_logic;
        i_T : in std_logic;

        o_Q : out std_logic
    );
end entity;

```

```

architecture behavioral of ff_d_t is
begin
    process(i_clk, i_rstb)
    begin
        if (i_rstb = '0') then
            o_Q <= '0';
        elsif (rising_edge(i_clk)) then
            if (i_T = '0') then
                o_Q <= i_D;
            else
                o_Q <= not o_Q;
            end if;
        end if;
    end process;
end behavioral;

```

