

Measuring Gate Delays




Last modified 1/8/24

Measuring Gate Delays

- Source Effects
 - Need to guard against source effects in both simulation and lab testing
 - Ideal sources do not exist in real designs
 - Unlimited current
 - No over/under shoot
 - No limits on slew rate
- Load Effects
 - The standard for measuring gate delays differs for:
 - Designs using discrete parts on a PCB
 - Use a fixed load capacitance (10pF, 25pF, 50pf)
 - Integrated circuit designs
 - Use one input from a minimum 2 input NAND gate

Measuring Gate Delays

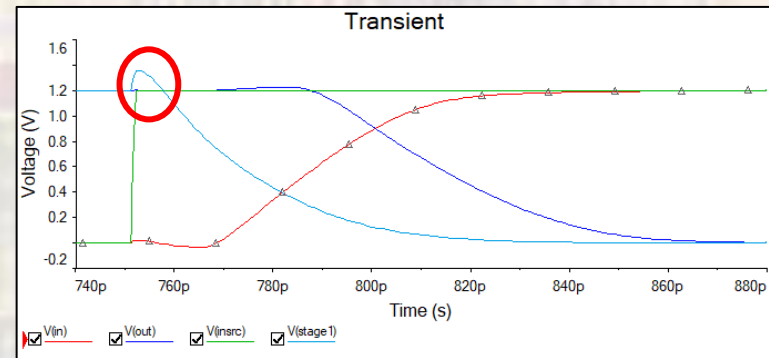 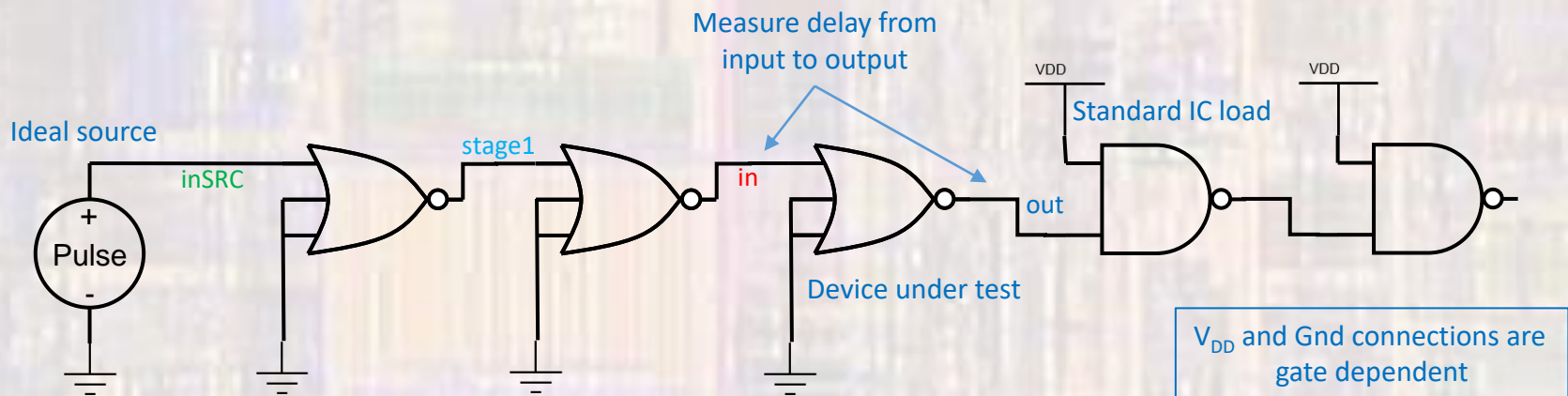- Isolate the source
 - Chain gates of the same type to isolate the source



Example test for 3 input NOR (IC method)