

Mixed Signal Design


Last updated 1/25/24

Mixed Signal Design

- Most of the real world is analog
 - Temperature, pressure, voltage, current, ...
 - To work with these values in a computer we must convert them to/from digital representations
 - Analog to Digital Conversion
 - Digital to Analog Conversion

Analog to Digital Conversion

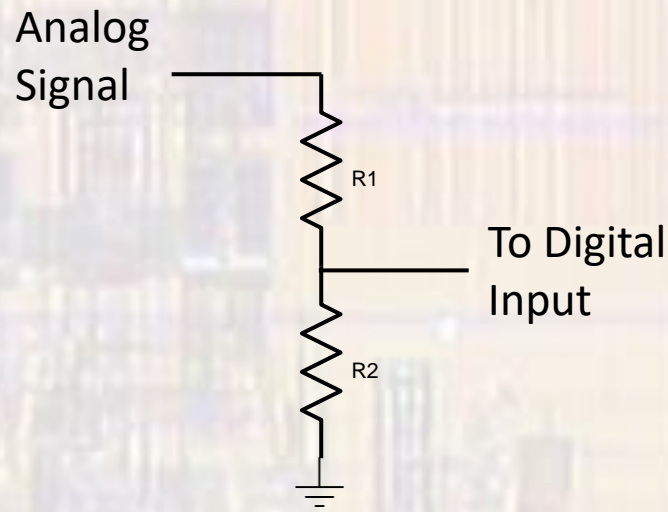- 1 bit conversion
 - Rough conversion
 - We know CMOS gates transition around $V_{DD}/2$
 - Use a resistor divider to convert the analog signal (desired switching level) to $V_{DD}/2$



Analog signal ranges from 0V to 5V
Want the switching point to be 2.5V

Digital circuit runs at 3.3V (~1.65V transition point)



Choose: $R_2 = 50\text{K}\Omega \rightarrow R_1 = 26\text{K}\Omega$

Analog to Digital Conversion

- N-bit conversion
 - Break the analog signal into 2^N steps
 - 3 steps in the conversion
 - Limit the input frequency range
 - Sample the input
 - Convert to the digital value

Analog to Digital Conversion

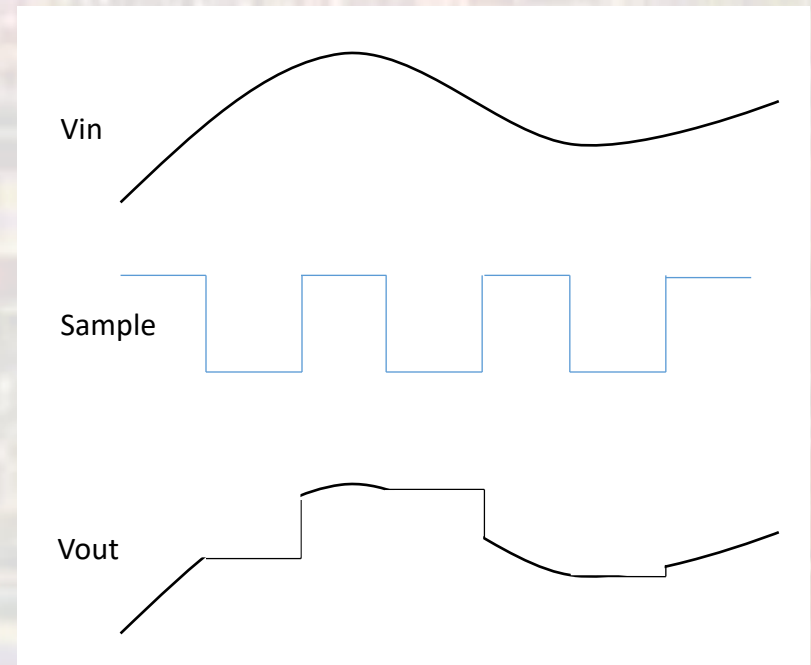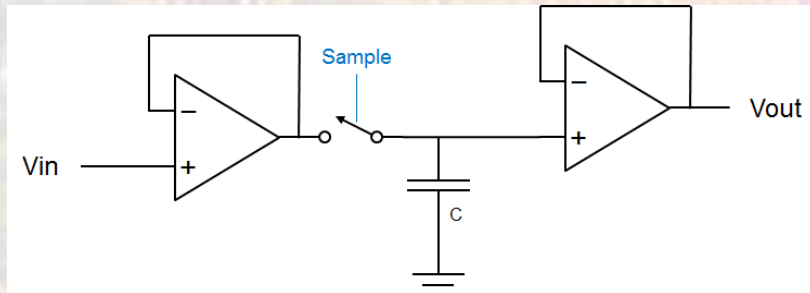
- N-bit Conversion
 - Step 2 – Sample the input
 - A to D Conversion takes a finite amount of time
 - What if the input changes during this time?
 - We must take a snapshot of the input → Sample and Hold



Analog to Digital Conversion

- N-bit Conversion
 - Step 1 – Limit the input frequency range
 - Sampling is a kind of MODULATION
 - Modulation systems are subject to Aliasing
 - $f_{in} < f_s/2$
 - f_s : Nyquist rate

→ LPF the input
(anti-aliasing filter)

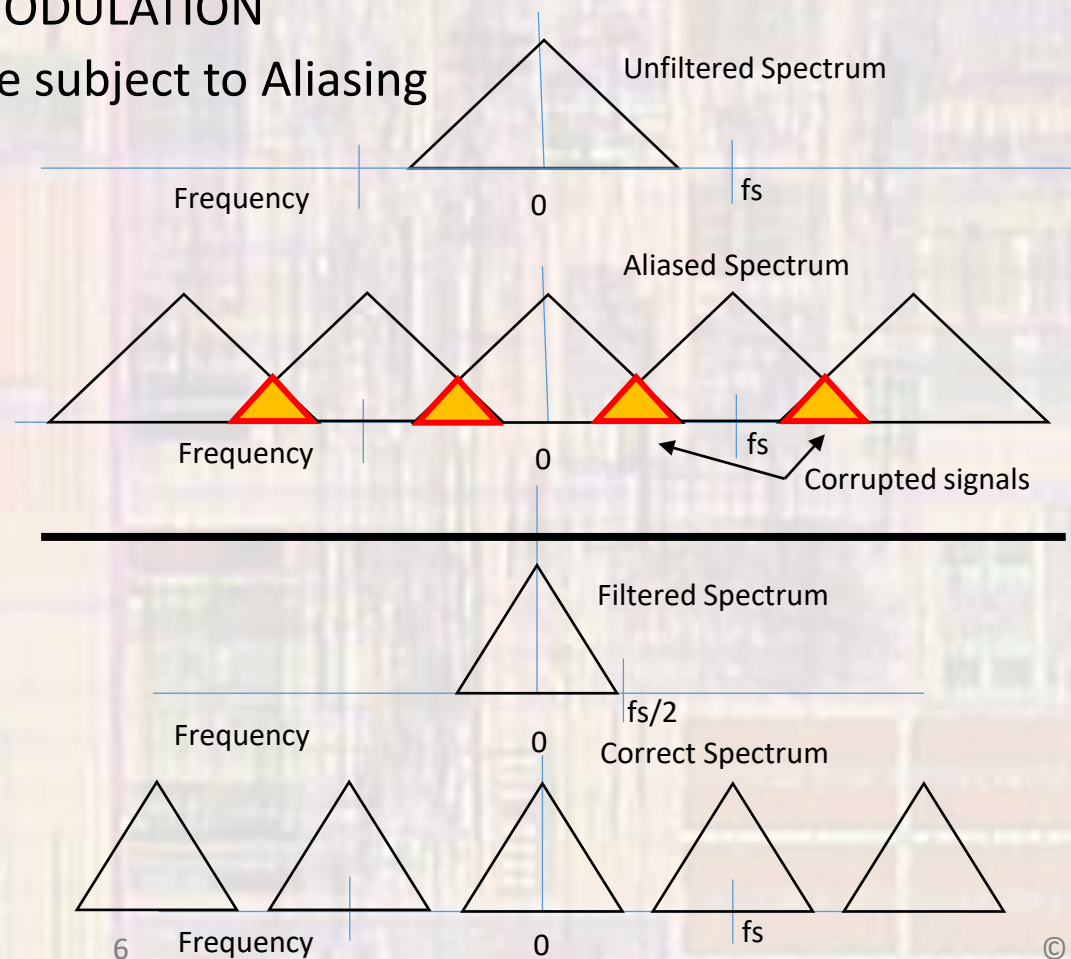

Analog to Digital Conversion

- N-bit Conversion
 - Step 3 – Convert to the digital value
 - Various methods can be used to do the conversion
 - Provide a reference voltage
 - Break the reference voltage into 2^N equal steps
 - Assign a digital value according to the number of steps required to reach the input

5V reference

10bit conversion $\rightarrow 2^{10}$ steps = 1024 steps $\rightarrow 5V/1024\text{steps} = 4.88\text{mV/step}$

3.2V input $\rightarrow 3.2V/4.88\text{mV/step} = 655.36\text{steps} \rightarrow 655$ steps

Output is: 655 in 10 bit binary $\rightarrow 10\ 1000\ 1111 = 0x28F$

Digital to Analog Conversion

- N-bit Conversion
 - Convert the digital value to an analog value
 - Various methods can be used to do the conversion
 - Provide a reference voltage
 - Break the reference voltage into 2^N equal steps
 - Assign an analog value according to the number of steps represented by the digital value

3.3V reference

8 bit conversion $\rightarrow 2^8$ steps = 256 steps $\rightarrow 3.3V/256\text{steps} = 12.89\text{mV/step}$

0xA2 input = 1010 0010 \rightarrow 162 steps

Output is: 162 steps * 12.89mV/step = 2.088V