
 


# Multiplexors

Last updated 8/22/24
 
# Multiplexor

- A multiplexor selects one of several inputs and routes it to the output
- The inputs and output can be single wires or busses



sel1	sel0	out
0	0	a
0	1	b
1	0	c
1	1	d

# Multiplexor


- 4 input multiplexor

```
-- multiplexor_4.vhd1
-- created 8/22/24
-- tj
-----
-- Multiplexor examples for the notes
-----
-- inputs: 4 data signals and 2 wire select
-- outputs: data output
-----
library ieee;
use ieee.std_logic_1164.all;

entity multiplexor_4 is
  port (
    i_a : in std_logic;
    i_b : in std_logic;
    i_c : in std_logic;
    i_d : in std_logic;
    i_sel : in std_logic_vector(1 downto 0);

    o_out : out std_logic
  );
end entity;

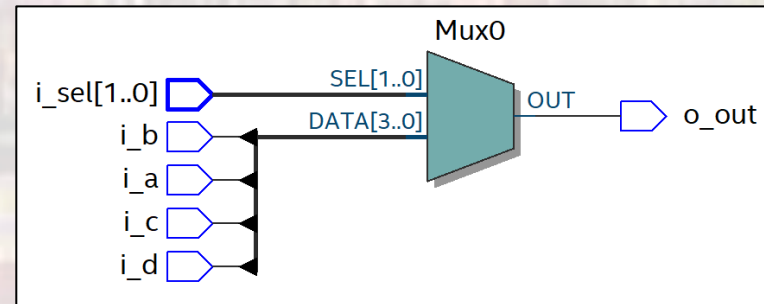architecture behavioral of multiplexor_4 is
  -- no internal signals
begin
  mux : process(i_a, i_b, i_c, i_d, i_sel)
  begin
    case i_sel is
      when "00" => o_out <= i_a ;
      when "01" => o_out <= i_b ;
      when "10" => o_out <= i_c ;
      when others => o_out <= i_d ;
    end case;
  end process;
end architecture;
```




# Multiplexor

- n input multiplexor – N must be a power of 2

```
-- multiplexor_n.vhdl
--
-- created 8/22/24
-- tj
--
-----
-- Multiplexor examples for the notes
--
-----
--
-- inputs: N data signals and log2(N) wire select
-- outputs: data output
--
-----
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
use ieee.math_real.all;

entity multiplexor_n is
  generic(
    N : natural := 8
  );
  port (
    i_data_in : in std_logic_vector((N - 1) downto 0);
    i_sel      : in std_logic_vector((integer(ceil(log2(real(N)))) - 1) downto 0);
    o_data_out : out std_logic
  );
end entity;

 architecture behavioral of multiplexor_n is
  -- no internal signals
begin
  mux_n : process(i_data_in, i_sel)
  begin
    o_data_out <= i_data_in(to_integer(unsigned(i_sel)));
  end process;
end architecture;
```



although the data inputs are configured as a vector – they would be connected as individual wires

# Multiplexor


- n input multiplexor – check if N is a power of 2

```
-- multiplexor_n.vhdl
-- created 8/22/24
-- tj
-----
-- Multiplexor examples for the notes
-----
-- inputs: N data signals and log2(N) wire select
-- outputs: data output
-----
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
use ieee.math_real.all;

entity multiplexor_n is
  generic(
    N : natural := 8
  );
  port (
    i_data_in  : in std_logic_vector((N - 1) downto 0);
    i_sel      : in std_logic_vector((integer(ceil(log2(real(N)))) - 1) downto 0);
    o_data_out : out std_logic
  );
end entity;

architecture behavioral of multiplexor_n is
  -- no internal signals
  begin
    -- Assert that N is a power of 2
    assert (integer(log2(real(N))) = (integer(ceil(log2(real(N))))))
      report "Error: multiplexor_n generic:N must be a power of 2"
      severity error;

     mux_n : process(i_data_in, i_sel)
    begin
      o_data_out <= i_data_in(to_integer(unsigned(i_sel)));
    end process;
  end architecture;
```



Create a compiler error  
if N is NOT a power of 2

# Multiplexor


- bus multiplexor – 8 wire, 4 way

```
-- multiplexor_bus8_4.vhd1
-- created 8/22/24
-- tj
-----
-- Multiplexor examples for the notes
-----
-- inputs: 4 8 wire data bus signals, 2 wire select
-- outputs: 8 wire data bus output
-----
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
use ieee.math_real.all;

entity multiplexor_bus8_4 is
  port (
    i_a : in std_logic_vector(7 downto 0);
    i_b : in std_logic_vector(7 downto 0);
    i_c : in std_logic_vector(7 downto 0);
    i_d : in std_logic_vector(7 downto 0);
    i_sel : in std_logic_vector(1 downto 0);

    o_out : out std_logic_vector(7 downto 0)
  );
end entity;

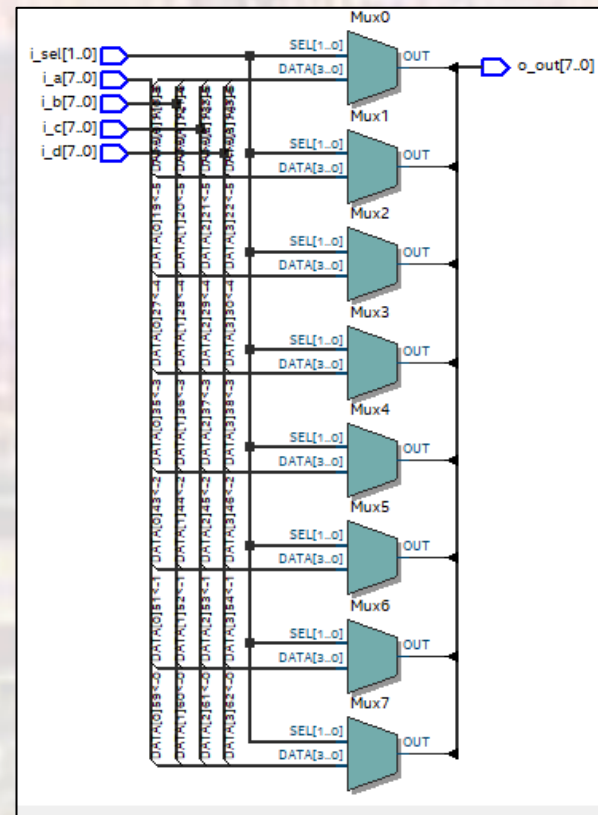architecture behavioral of multiplexor_bus8_4 is
  -- no internal signals
begin
  mux : process(i_a, i_b, i_c, i_d, i_sel)
  begin
    case i_sel is
      when "00" => o_out <= i_a ;
      when "01" => o_out <= i_b ;
      when "10" => o_out <= i_c ;
      when others => o_out <= i_d ;
    end case;
  end process;
end architecture;
```



Instead of implementing this as 4, 8 wire muxes the compiler implemented it as 8, 4 wire muxes each managing 1 wire of the 8 wire inputs

# Multiplexor

- bus multiplexor – M wire, N way

see if you can do this