 


Register Files

Last updated 8/23/24

Register Files

- Register File
 - A register file is a collection of registers treated as a single entity
 - `reg_sel` – chooses which register to pass to `data_out`
chooses which register to write
 - `w_en_b` - enables writing to a register when low, and `clk` ↑



Register Files

- Register File – 8, 16bit registers – 1 in/out

```
-- regfile_16x8x1
--
-- 8 - 16 bit registers
-- single input/output
--
-- created by johnsontimoy
-- 5/7/18
-- rev 0
--
-----
--
-- Inputs: clk, reg_sel, we_bar
-- Outputs: data_out
--
-----
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;


entity regfile_16x8x1 is
  port (
    i_clk : in std_logic;
    i_reg_sel : in std_logic_vector(2 downto 0);
    i_data_in : in std_logic_vector(15 downto 0);
    i_we_b : in std_logic;
    o_data_out : out std_logic_vector(15 downto 0)
  );
end entity;
```

There are more efficient ways to code this – using an array

```
architecture behavioral of regfile_16x8x1 is
  -- register signals
  signal reg_0: std_logic_vector(15 downto 0);
  signal reg_1: std_logic_vector(15 downto 0);
  signal reg_2: std_logic_vector(15 downto 0);
  signal reg_3: std_logic_vector(15 downto 0);
  signal reg_4: std_logic_vector(15 downto 0);
  signal reg_5: std_logic_vector(15 downto 0);
  signal reg_6: std_logic_vector(15 downto 0);
  signal reg_7: std_logic_vector(15 downto 0);


  -- register logic
  process(i_clk)
  begin
    if(rising_edge(i_clk)) then
      if(i_we_b = '0') then
        case(i_reg_sel) is
          when "000" => reg_0 <= i_data_in;
          when "001" => reg_1 <= i_data_in;
          when "010" => reg_2 <= i_data_in;
          when "011" => reg_3 <= i_data_in;
          when "100" => reg_4 <= i_data_in;
          when "101" => reg_5 <= i_data_in;
          when "110" => reg_6 <= i_data_in;
          when "111" => reg_7 <= i_data_in;
          when others => null;
        end case;
      end if;
    end if;
  end process;

  -- output logic
  process(all)
  begin
    case(i_reg_sel) is
      when "000" => o_data_out <= reg_0;
      when "001" => o_data_out <= reg_1;
      when "010" => o_data_out <= reg_2;
      when "011" => o_data_out <= reg_3;
      when "100" => o_data_out <= reg_4;
      when "101" => o_data_out <= reg_5;
      when "110" => o_data_out <= reg_6;
      when "111" => o_data_out <= reg_7;
      when others => o_data_out <= reg_7; -- arbitrary
    end case;
  end process;
end behavioral;
```

 

Register Files

- Register File – multiple outputs

 

Register Files

- Register File – 8, 16bit registers – 4 outputs

```
-- regfile_16x8x4
-- 8 - 16 bit registers
-- 4 outputs
-- created by johnsontimoj
-- 5/7/18
-- rev 0

-----

-- Inputs: clk, reg_sel, wr_sel, we_bar
-- Outputs: data_out a, b, c, d

-----

library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;


entity regfile_16x8x4 is
    port (
        i_clk : in std_logic;
        i_reg_selA : in std_logic_vector(2 downto 0);
        i_reg_selB : in std_logic_vector(2 downto 0);
        i_reg_selC : in std_logic_vector(2 downto 0);
        i_reg_selD : in std_logic_vector(2 downto 0);
        i_wr_sel : in std_logic_vector(2 downto 0);
        i_data_in : in std_logic_vector(15 downto 0);
        i_we_b : in std_logic;

        o_data_outA : out std_logic_vector(15 downto 0);
        o_data_outB : out std_logic_vector(15 downto 0);
        o_data_outC : out std_logic_vector(15 downto 0);
        o_data_outD : out std_logic_vector(15 downto 0)
    );
end entity;
```

```
architecture behavioral of regfile_16x8x4 is
    -- register signals
    signal reg_0 : std_logic_vector(15 downto 0);
    signal reg_1 : std_logic_vector(15 downto 0);
    signal reg_2 : std_logic_vector(15 downto 0);
    signal reg_3 : std_logic_vector(15 downto 0);
    signal reg_4 : std_logic_vector(15 downto 0);
    signal reg_5 : std_logic_vector(15 downto 0);
    signal reg_6 : std_logic_vector(15 downto 0);
    signal reg_7 : std_logic_vector(15 downto 0);

begin
    -- register logic
    process(i_clk)
    begin
        if(rising_edge(i_clk)) then
            if(i_we_b = '0') then
                case(i_reg_sel) is
                    when "000" => reg_0 <= i_data_in;
                    when "001" => reg_1 <= i_data_in;
                    when "010" => reg_2 <= i_data_in;
                    when "011" => reg_3 <= i_data_in;
                    when "100" => reg_4 <= i_data_in;
                    when "101" => reg_5 <= i_data_in;
                    when "110" => reg_6 <= i_data_in;
                    when "111" => reg_7 <= i_data_in;
                    when others => null;
                end case;
            end if;
        end if;
    end process;
```

```
-- output logic
process(all)
begin
    case(i_reg_selA) is
        when "000" => o_data_outA <= reg_0;
        when "001" => o_data_outA <= reg_1;
        when "010" => o_data_outA <= reg_2;
        when "011" => o_data_outA <= reg_3;
        when "100" => o_data_outA <= reg_4;
        when "101" => o_data_outA <= reg_5;
        when "110" => o_data_outA <= reg_6;
        when "111" => o_data_outA <= reg_7;
        when others => o_data_outA <= reg_7;
    end case;
    case(i_reg_selB) is
        when "000" => o_data_outB <= reg_0;
        when "001" => o_data_outB <= reg_1;
        when "010" => o_data_outB <= reg_2;
        when "011" => o_data_outB <= reg_3;
        when "100" => o_data_outB <= reg_4;
        when "101" => o_data_outB <= reg_5;
        when "110" => o_data_outB <= reg_6;
        when "111" => o_data_outB <= reg_7;
        when others => o_data_outB <= reg_7;
    end case;
    case(i_reg_selC) is
        when "000" => o_data_outC <= reg_0;
        when "001" => o_data_outC <= reg_1;
        when "010" => o_data_outC <= reg_2;
        when "011" => o_data_outC <= reg_3;
        when "100" => o_data_outC <= reg_4;
        when "101" => o_data_outC <= reg_5;
        when "110" => o_data_outC <= reg_6;
        when "111" => o_data_outC <= reg_7;
        when others => o_data_outC <= reg_7;
    end case;
    case(i_reg_selD) is
        when "000" => o_data_outD <= reg_0;
        when "001" => o_data_outD <= reg_1;
        when "010" => o_data_outD <= reg_2;
        when "011" => o_data_outD <= reg_3;
        when "100" => o_data_outD <= reg_4;
        when "101" => o_data_outD <= reg_5;
        when "110" => o_data_outD <= reg_6;
        when "111" => o_data_outD <= reg_7;
        when others => o_data_outD <= reg_7;
    end case;
end process;
end behavioral;
```

 

There are more efficient ways to code this – using an array

Register Files

- Register File – 8, 16bit registers – 4 outputs
 - Array implementation

```
-- regfile_16x8x4
-- 8 - 16 bit registers
-- 4 outputs
-- created by johnsontimoj
-- 5/7/18
-- rev 0
-----
-- Inputs: clk, reg_sel, wr_sel, we_bar
-- Outputs: data_out a, b, c, d
-----
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity regfile_16x8x4 is
  port (
    i_clk : in std_logic;
    i_reg_selA : in std_logic_vector(2 downto 0);
    i_reg_selB : in std_logic_vector(2 downto 0);
    i_reg_selC : in std_logic_vector(2 downto 0);
    i_reg_selD : in std_logic_vector(2 downto 0);
    i_wr_sel : in std_logic_vector(2 downto 0);
    i_data_in : in std_logic_vector(15 downto 0);
    i_we_b : in std_logic;
    o_data_outA : out std_logic_vector(15 downto 0);
    o_data_outB : out std_logic_vector(15 downto 0);
    o_data_outC : out std_logic_vector(15 downto 0);
    o_data_outD : out std_logic_vector(15 downto 0)
  );
end entity;
```

