

Registers

Last updated 2/8/24

Registers

- Registers are collections of Flip-Flops
- Registers are created by creating code that conforms to the Flip-Flop synthesis template

```
process (clock signal)
begin
  if(clock edge detection) then
    actions
  end if;
end process;
```


note:

- here the else is not required because the synthesizer recognizes the edge detection
- you can include an else for clarity


Registers

- Register
 - Collection of n Flip-Flops
 - Configured in parallel
 - Common clock, set/reset, enable
 - Stores an n-bit state variable


n-bit register

 

n bit wide bus

 

signal indices n-1 down to 0

 

Registers

- N bit data register

```
library ieee;
use ieee.std_logic_1164.all;

entity reg_n_bit is
  generic(
    N: integer := 8
  );
  port (
    i_D:   in std_logic_vector((N - 1) downto 0);
    i_clk: in std_logic;
    i_rstb: in std_logic;


    o_Q:   out std_logic_vector((N - 1) downto 0)
  );
end entity;

architecture behavioral of reg_n_bit is
begin
  process(i_clk, i_rstb)
  begin
    if (i_rstb = '0') then
      o_Q <= (others => '0');
    elsif (rising_edge(i_clk)) then
      o_Q <= i_D;
    end if;
  end process;
end behavioral;
```

generic section

- defines N
- defaults N to 8
- can be overwritten when instantiated

Vector sizes now defined with N

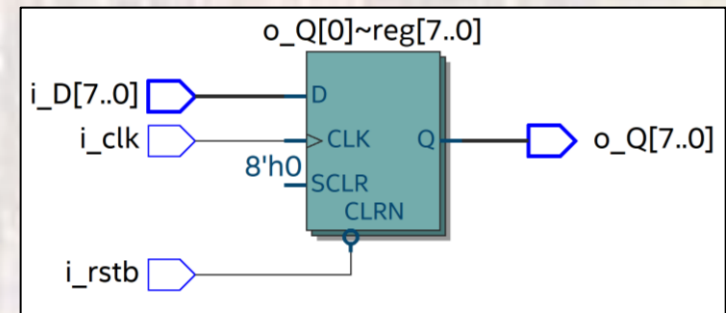

(others => '0') used since N can change

Registers

- N bit data register
 - Enhancements
 - Asynch/synch reset, set
 - Clear
 - Load
 - Preload
 - Enable

Registers

- Shift Register

- Shift a series of bits within a register
- Left/right
- N bit shift

- Wrapping

- Load register with load signal
- Direction, amount

DATA	dir	amt	result
00100	R	1	00010
00010	R	3	01000
01000	L	2	00001

- Non-wrapping

- Data input
- Sign extend
- 0/1 pad


Din	DATA	dir	result
1	00100	R	10010
0	10010	R	01001
1	01001	L	10011

- Depending on what the shift register represents use

- `std_logic_vector`, unsigned or signed

Registers

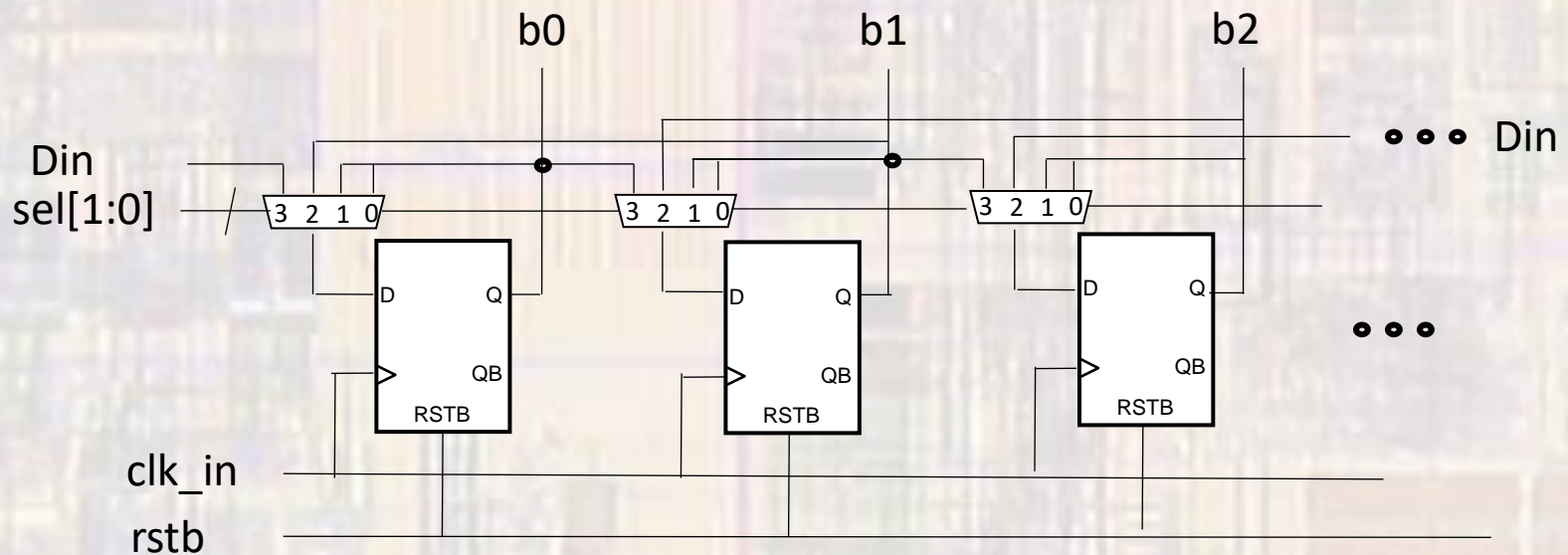- Shift Register
 - Non-wrapping, Data in (from both ends)
 - sel[0]: dir : right(1) / left(0)
 - sel[1]: shift: shift(1) / no-shift(0)
 - Unsigned data



Registers

- Shift Register – n
 - D shifts in from left or right

```
-----  
-- reg_shift_n_bit.vhdl  
-- created 2/29/17  
-- johnsontimoj  
-- rev 0  
-----  
-- n bit L/R shift register example  
-----  
-- Inputs: rstb, clk, D, shift, dir  
-- Outputs: Q[(n-1):0]  
-----  
library ieee;  
use ieee.std_logic_1164.all;  
use ieee.numeric_std.all;  
  
entity reg_shift_n_bit is  
  generic(  
    N: natural := 8  
  );  
  port (  
    i_clk : in std_logic;  
    i_rstb : in std_logic;  
    i_D : in std_logic;  
    i_shift: in std_logic;  
    i_dir : in std_logic; -- 0 for left, 1 for right  
  
    o_Q : out std_logic_vector((N - 1) downto 0)  
  );  
end entity;
```



```
architecture behavioral of reg_shift_n_bit is  
  
  -- internal signals  
  signal q_sig: unsigned((N - 1) downto 0);  
  
begin  
  process(i_clk, i_rstb)  
    begin  
      -- reset  
      if (i_rstb = '0') then  
        q_sig <= (others => '0');  
      -- rising clk edge  
      elsif (rising_edge (i_clk)) then  
        -- shifting  
        if (i_shift = '0') then  
          q_sig <= q_sig;  
        elsif (i_dir = '0') then  
          q_sig <= q_sig((N - 2) downto 0) & i_D;  
        else  
          q_sig <= i_D & q_sig((N - 1) downto 1);  
        end if;  
      end if;  
    end process;  
  
    -- Output logic  
    o_Q <= std_logic_vector(q_sig);  
  
end behavioral;
```

Why do I need this

Why do I need this


Registers

- Shift Register - n

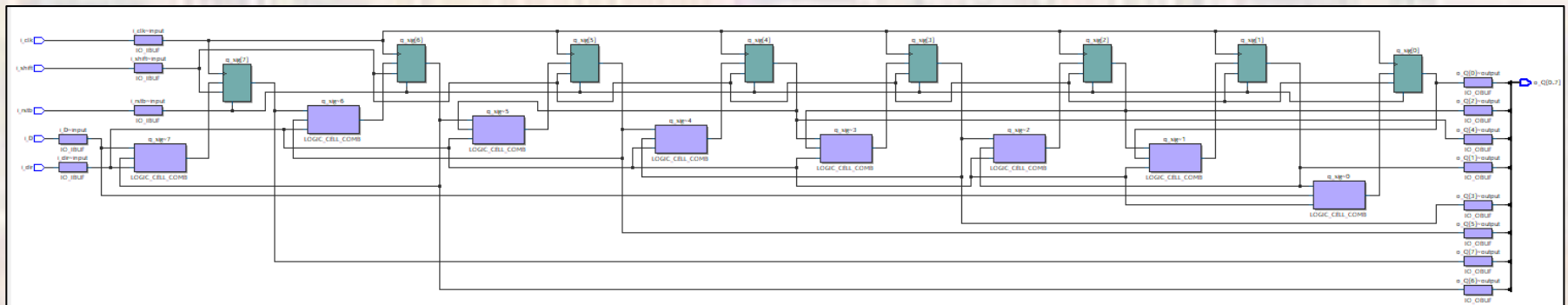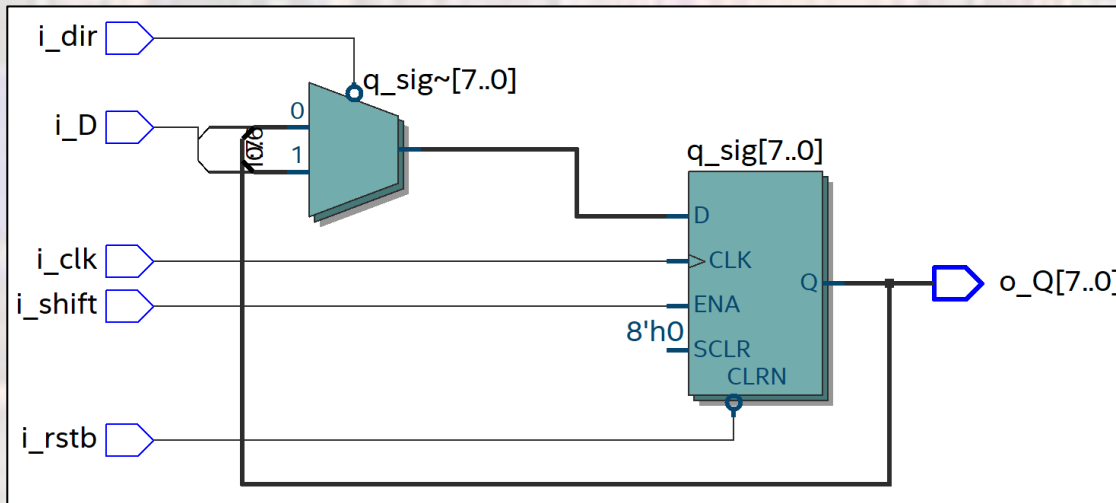

Registers

- Shift Register – n
 - Testbench

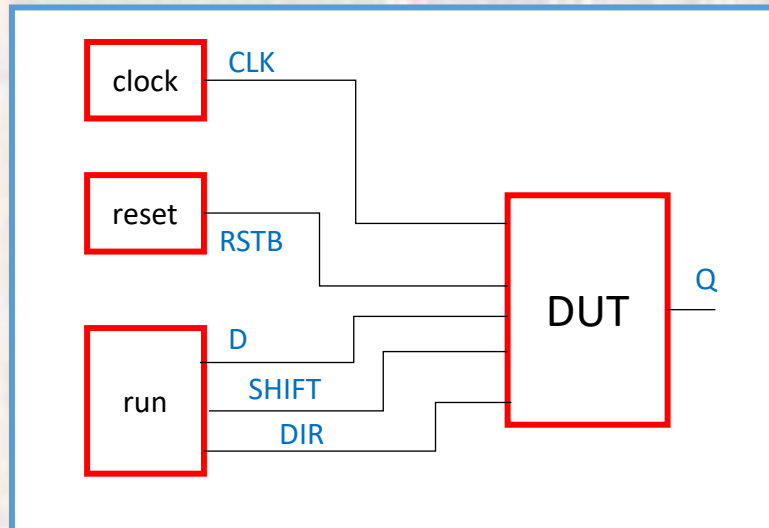

Registers

- Shift Register – n
- Testbench

```
-----  
-- reg_shift_n_bit_tb.vhdl  
--  
-- created: 1/26/18  
-- by: johnsontimoj  
-- rev: 0  
--  
-- testbench for n bit shift register  
-- of reg_shift_n_bit.vhdl  
--  
-- brute force implementation  
-----  
library ieee;  
use ieee.std_logic_1164.all;  
entity reg_shift_n_bit_tb is  
  generic(  
    NUM_BITS: natural := 16  
  );  
  -- no entry - testbench  
end entity;
```

testbench
generic

```
architecture testbench of reg_shift_n_bit_tb is  
  signal CLK:      std_logic;  
  signal RSTB:     std_logic;  
  signal D:        std_logic;  
  signal SHIFT:    std_logic;  
  signal DIR:      std_logic;  
  
  signal Q:        std_logic_vector((NUM_BITS - 1) downto 0);  
  
  constant PER:    time := 20 ns;  
  
  -----  
  -- Component prototype  
  -----  
  COMPONENT reg_shift_n_bit  
    GENERIC ( N : INTEGER := 8 );  
    PORT  
    (  
      i_clk      : IN STD_LOGIC;  
      i_rstb     : IN STD_LOGIC;  
      i_D        : IN STD_LOGIC;  
      i_shift    : IN STD_LOGIC;  
      i_dir      : IN STD_LOGIC;  
      o_Q        : OUT STD_LOGIC_VECTOR(n-1 DOWNTO 0)  
    );  
  END COMPONENT;  
  
  -----  
  begin  
  
  -----  
  -- Device under test (DUT)  
  -----  
  DUT: reg_shift_n_bit  
    generic map(  
      N => NUM_BITS  
    )  
    port map(  
      i_clk      => CLK,  
      i_rstb     => RSTB,  
      i_D        => D,  
      i_shift    => SHIFT,  
      i_dir      => DIR,  
      o_Q        => Q  
    );  
end;
```

module
generic
(reset by TB)

Registers

- Shift Register – n
 - Testbench

```
-----  
-- Test processes  
-----  
  
-- Clock process  
clock: process -- no sensitivity list allowed  
begin  
    CLK <= '0';  
    wait for PER/2;  
    infinite: loop  
        CLK <= not CLK; wait for PER/2;  
    end loop;  
end process clock;  
  
-- Reset process  
reset: process -- no sensitivity list allowed  
begin  
    RSTB <= '0'; wait for 2*PER;  
    RSTB <= '1'; wait;  
end process reset;
```

Note comments

```
-- Run process  
run: process -- no sensitivity list allowed  
begin  
    -- Initialize inputs  
    D <= '0';  
    SHIFT <= '0';  
    DIR <= '0';  
  
    wait for 2*PER; -- wait for reset  
  
    -- verify no shift  
    D <= '1'; wait for PER;  
    D <= '0'; wait for PER;  
  
    -- verify shift lt  
    SHIFT <= '1';  
    D <= '1'; wait for 8*PER;  
    D <= '0'; wait for 8*PER;  
  
    -- verify shift rt  
    DIR <= '1';  
    D <= '1'; wait for 8*PER;  
    D <= '0'; wait for 8*PER;  
end process run;  
  
-----  
-- End test processes  
-----  
  
end architecture;
```

