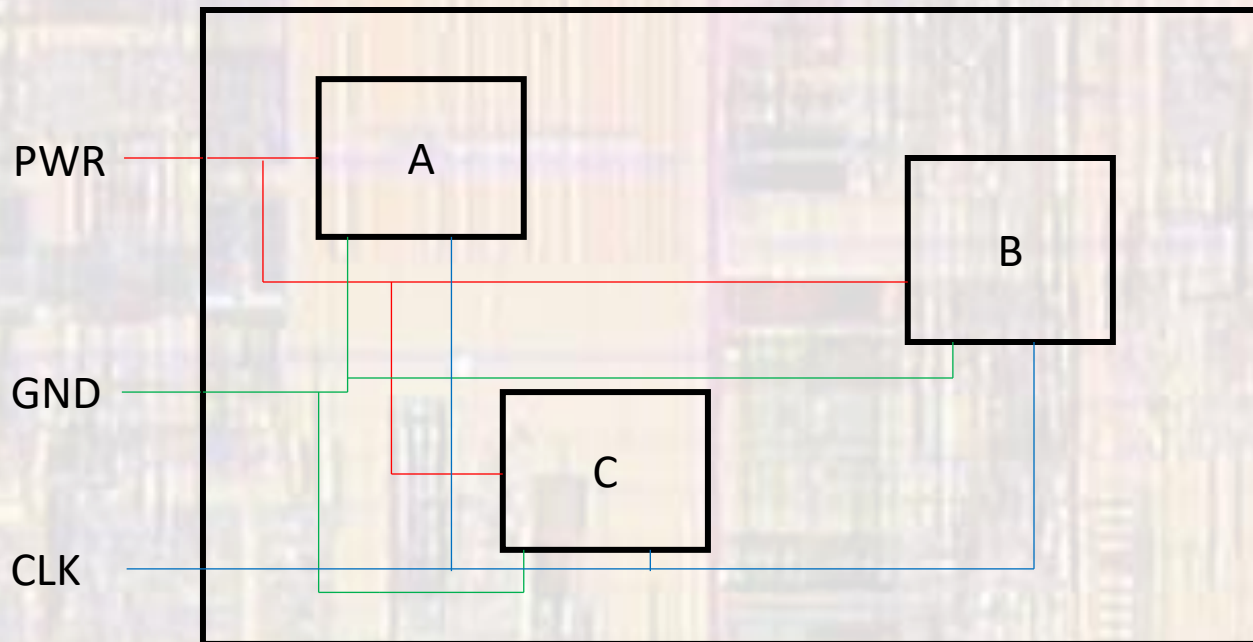


Reset_bar

Last updated 1/9/24


Reset_bar

- Why are we using resetB instead of just reset?
- Consider a system – could be on a chip, a board, or across multiple boards




Reset_bar

 - Why are we using resetB instead of just reset?
- When the system is powered up there is a finite time associated with the rising supply voltage
- Due to inherent impedances (C and R), the signal is received at different blocks at different times





Reset_bar

- Why are we using resetB instead of just reset?
 - Active High Reset – Case 1
 - Somewhere in the system – the reset signal must be generated
 - If it were generated by block A, it is possible the reset signal would be released before block B stabilized (or even had power)
 - If that happens, block B would not be reset, and all the registers would have random values
 - We could resolve this by slowing down the reset signal

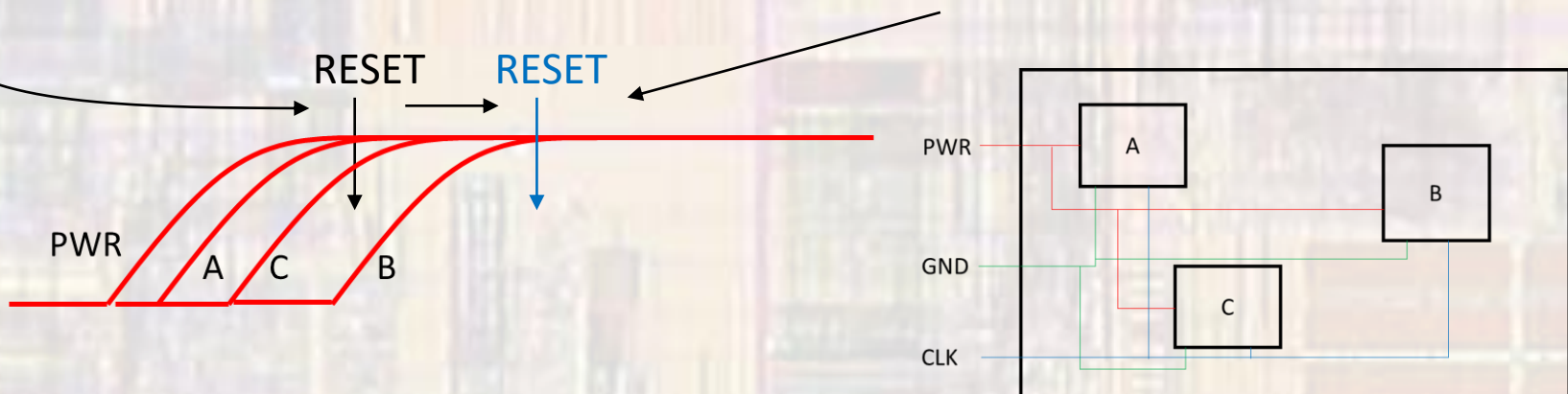


Reset_bar

- Why are we using resetB instead of just reset?
 - Active High Reset – Case 2
 - Somewhere in the system – the reset signal must be generated
 - If it were generated by block B, blocks A and C could be powered up
 - Block B would still be unpowered \rightarrow Reset = 0
 - Blocks A and C would be active – bad things could happen
 - Slowing down the Reset signal (case 1 solution) does not help this situation

  



Reset_bar

- Why are we using resetB instead of just reset?
 - Active Low Reset – Case 1
 - Somewhere in the system – the resetB signal must be generated
 - If it were generated by block A, it is possible the resetB signal would be released before block B stabilized (or even had power)
 - If that happens, block B would not be reset, and all the registers would have random values
 - We could resolve this by slowing down the ResetB signal

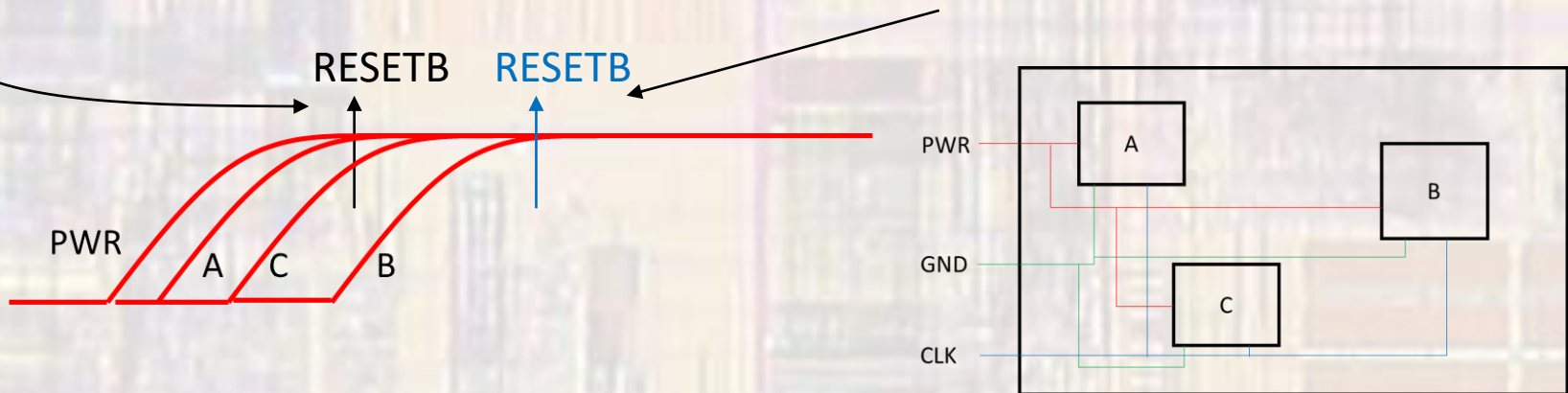

Reset_bar

- Why are we using resetB instead of just reset?
 - Active Low Reset – Case 2
 - Somewhere in the system – the resetB signal must be generated
 - If it were generated by block B, blocks A and C could be powered up
 - Block B would still be unpowered \rightarrow Reset = 0
 - Blocks A and C would be in reset \rightarrow No problem
 - Slowing down the Reset signal (case 1 solution) does not impact this situation

  

Reset_bar

- Why are we using resetB instead of just reset?
 - A slowed down resetB signal works in both situations
- Solution
 - Tie a large capacitor to the resetB signal
 - Design the capacitor to ensure **ALL** supplies are stable before the resetB signal reaches 10% of the supply voltage

