

Sequential Logic Review

Last updated 7/13/23

Sequential Logic Review

- Logical world
 - Basic Signal Values
 - 1, 0
 - High Low
 - True False
 - Set Reset
 - Additional values
 - X, x = don't care
 - U, u = unknown

Sequential Logic Review

- Physical world

- Voltage levels

- System/Circuit dependent (V_{DD} , Gnd)

- Ideal:

3.3v System

'1' = 3.3v

'0' = 0.0v

1.8v System

'1' = 1.8v

'0' = 0.0v


1.2v System

'1' = 1.2v

'0' = 0.0v


- Real world:

3.3v System

 

Sequential Logic Review

- Clock Systems

 


$$F \text{ (frequency)} = 1/T$$


$$\text{Duty Cycle} = \text{High} / T$$

$$50\text{MHz} \leftrightarrow 20\text{ns}$$
 
$$\text{High} = 10\text{ns}, \text{Low} = 10\text{ns}$$





25% duty cycle, 12.5MHz

 



75% duty cycle, 12.5MHz

Logic Review

- Latches

  


S	R	Q	QB
0	0	No change	No change
0	1	0	1
1	0	1	0
1	1	0	0

  

SB	RB	Q	QB
0	0	1	1
0	1	1	0
1	0	0	1
1	1	No change	No change

Logic Review

 - Flip-Flops
 - Edge Triggered
 - Outputs only change on a rising or falling clock edge (**synchronous**)
 - Outputs depend on the state of the inputs **at the clock edge**
 - Some have **asynchronous** set or reset inputs




Logic Review

- Flip-Flops

- Edge Triggered **D** Flip-Flop

- Outputs depend on the state of the inputs **at the rising clock edge**

 - Some have asynchronous set or reset inputs




Set	Reset Bar	D	Q	QB
0	1	0	0	1
0	1	1	1	0
1	1	x	1	0
0	0	x	0	1

} D at the rising clock edge

Logic Review

 - Flip-Flops
 - Edge Triggered **T** Flip-Flop (Toggle)
 - Outputs depend on the state of the inputs **at the rising clock edge**
 - Some have asynchronous set or reset inputs



T		Q	QB
0		Q_{OLD}	QB_{OLD}
1		QB_{OLD}	Q_{OLD}


} T at the rising clock edge

T		Q	QB
0		No Change	No Change
1		Toggle	Toggle

} T at the rising clock edge

Logic Review

 - Flip-Flops
 - Edge Triggered **SR** Flip-Flop (Set/Reset)
 - Outputs depend on the state of the inputs **at the rising clock edge**
 - Some have asynchronous set or reset inputs




R	S		Q	QB
0	0		Q_{OLD}	QB_{OLD}
0	1		1	0
1	0		0	1
1	1		N/A	N/A

S,R at the rising clock edge

Logic Review

 - Flip-Flops
 - Edge Triggered **JK** Flip-Flop
 - Outputs depend on the state of the inputs **at the rising clock edge**
 - Some have asynchronous set or reset inputs




J	K		Q	QB
0	0		Q_{OLD}	QB_{OLD}
0	1		0	1
1	0		1	0
1	1		Toggle	Toggle

J,K at the rising
clock edge


Logic Review

- Parallel Data Register

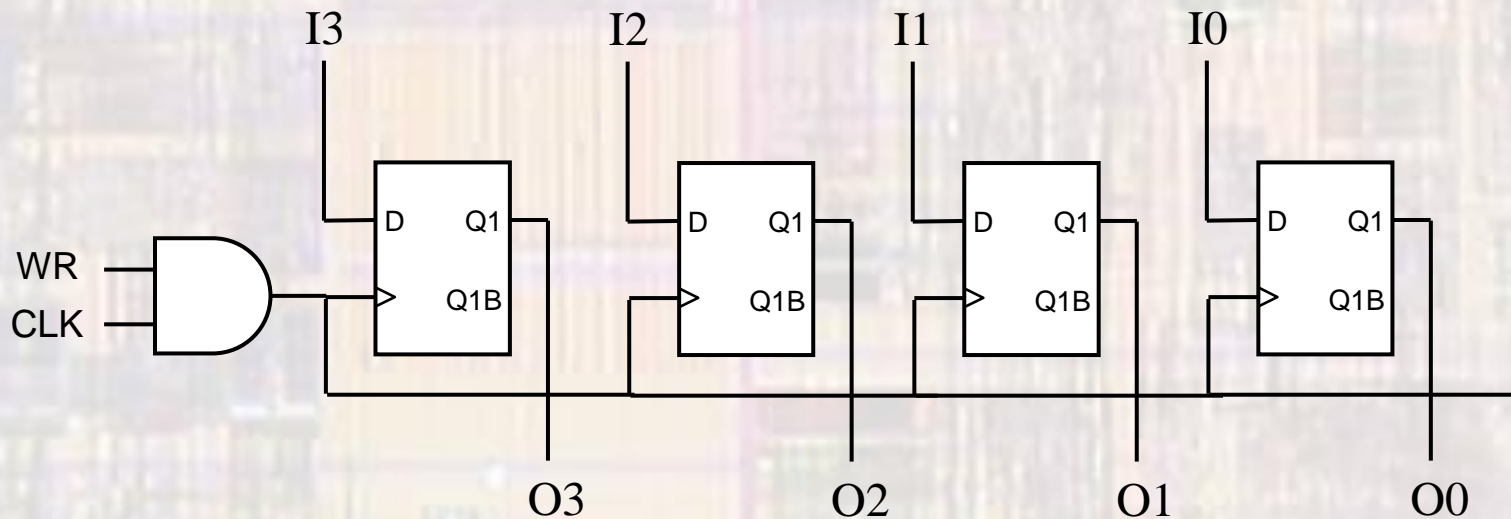

Logic Review

- Shift Register

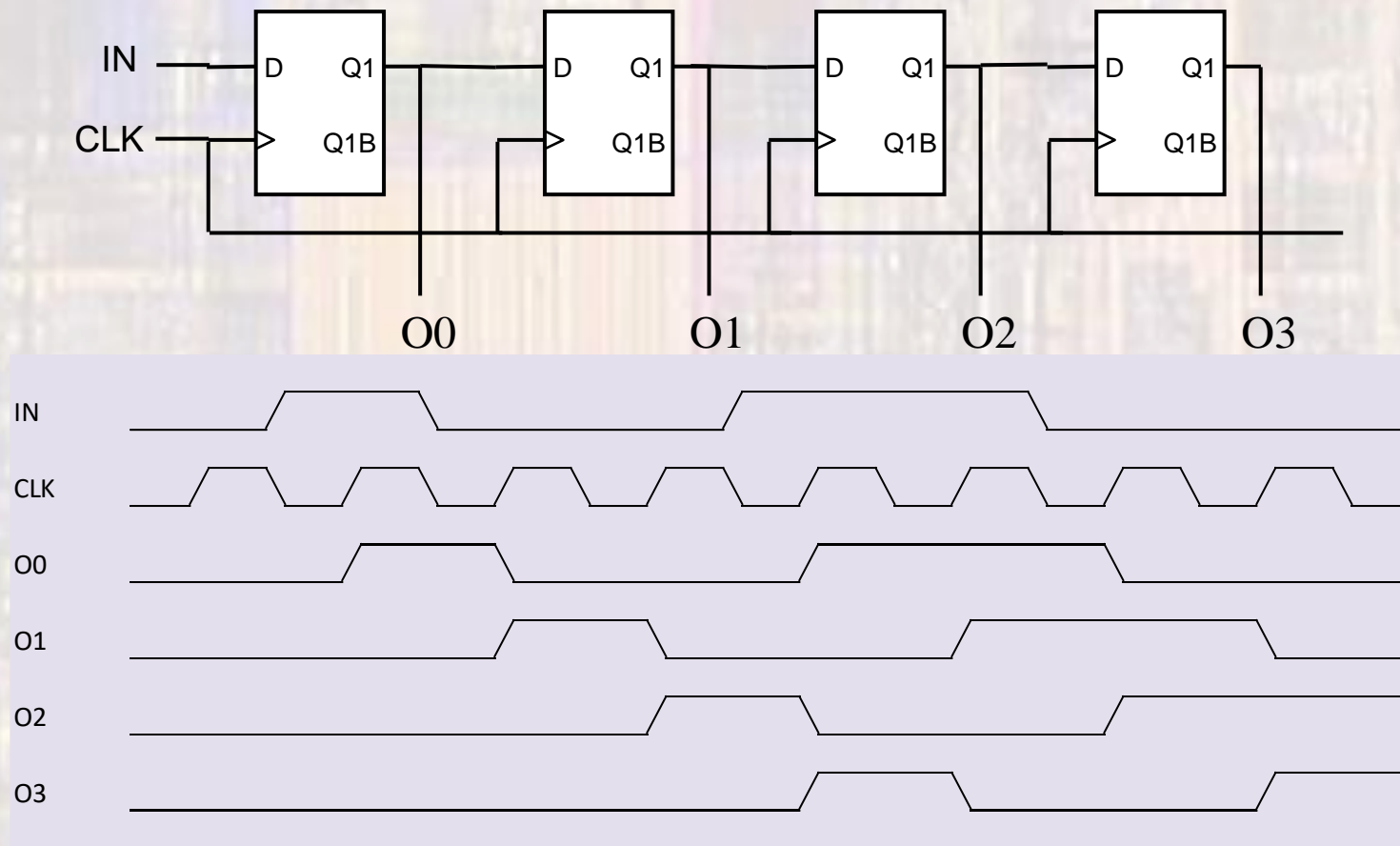

Logic Review

- Counter

