Last updated 7/18/23

ALU Control

Basic ALU control mapping

Operation	invA	negB	ctl[1]	ctl[0]
AND	0	0	1	1
OR	0	0	1	0
NOR	1	1	1	1
NAND	1	1	1	0
ADD	0	0	0	1
SUB	0	1	0	1
SLT	0	1	0	0


ALU Control

Full ALU control mapping


Operation	invA	negB	ctl[1]	ctl[0]
AND	0	0	1	1
OR	0	0	1	0
NOR	1	1	1	1
NAND	1	1	1	0
ADD	0	0	0	1
SUB	0	1	0	1
SLT	0	1	0	0
LD	0	0	0	1
ST	0	0	0	1
LDI	0	0	0	1

adding 0 from instruction adding 0 from instruction adding 0 from mux


ALU Control Signals

 

 - Data Memory Control Signals
 - mem_to_reg
 - Selects between the ALU output and the RAM read data value to pass to the Write data input of the register file
 - "1" only on LD instructions
 - ram_write
 - Enable writing to the Data RAM
 - "1" only on ST instructions




Data Memory Control Signals

 


ALU Input Control Signals

 
- alu_src_B
 - Selects between the Read data 2 output of the register file and the sign extended immediate signal to pass to ALU input B
 - "0" for arithmetic and logical instructions
 - "1" for LD, ST and LDI instructions
- alu_src_A
 - Selects between the Read data 1 output of the register file and 0 to pass to ALU input A
 - "1" only on LDI commands



ALU Input Control Signals

 

 - Register File Control Signals
 - reg_write
 - Enable writing to the Register File
 - "0" only on ST and SLT instructions



Register File Control Signals

