


# State Diagrams

Last updated 7/18/23

# State Diagrams

- State Diagram Elements


- State

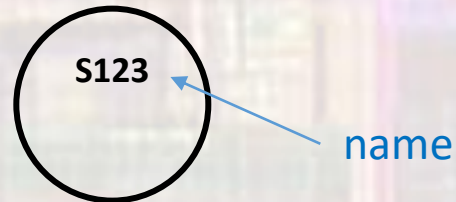

- Outputs



- Inputs

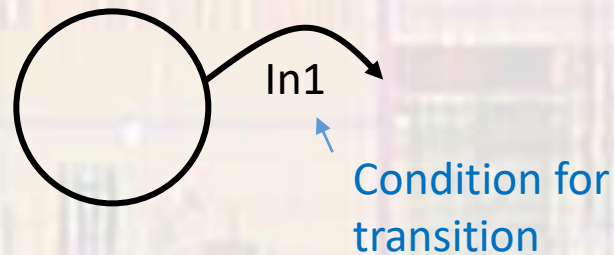

# State Diagrams

- Transition Rules
  - Transitions ONLY occur on clock edges (rising)
  - Transitions occur on EVERY clock edge (rising)
  - Only 1 path out of a state can be valid at a time
  - Every valid state must have an input path
  - Every valid state must have an output path
    - Note that the output path may point back to the originating state


# State Diagrams

- Example 1
  - Light Switch – states





# State Diagrams

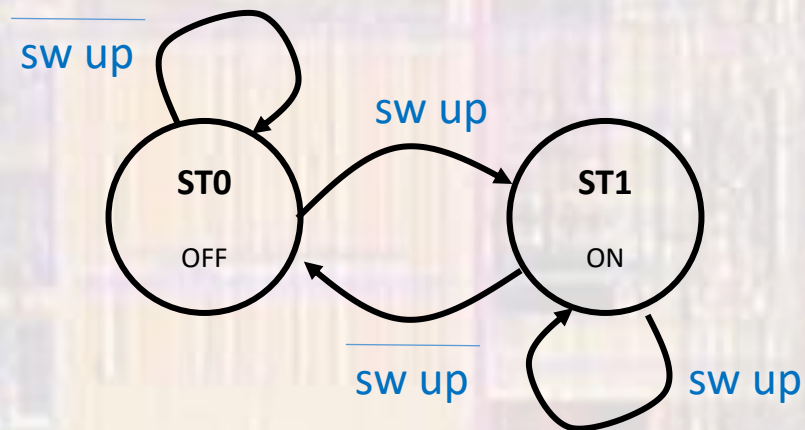- Example 1
  - Light Switch – transitions
    - Conditional – switch state is input




# State Diagrams

- Example 2
  - Stoplight - states

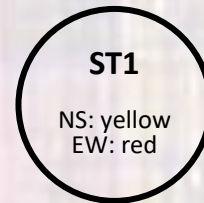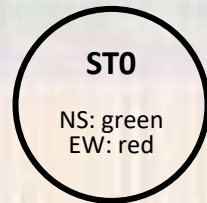


# State Diagrams

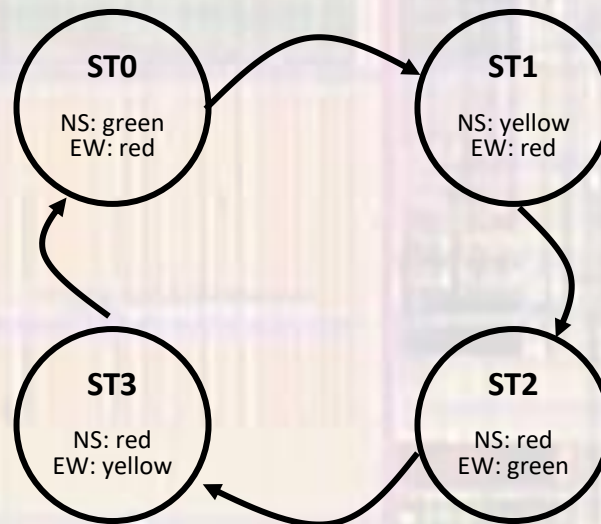- Example 2
  - Stoplight – transitions
    - Un-conditional – all signals active the same amount of time



# State Diagrams

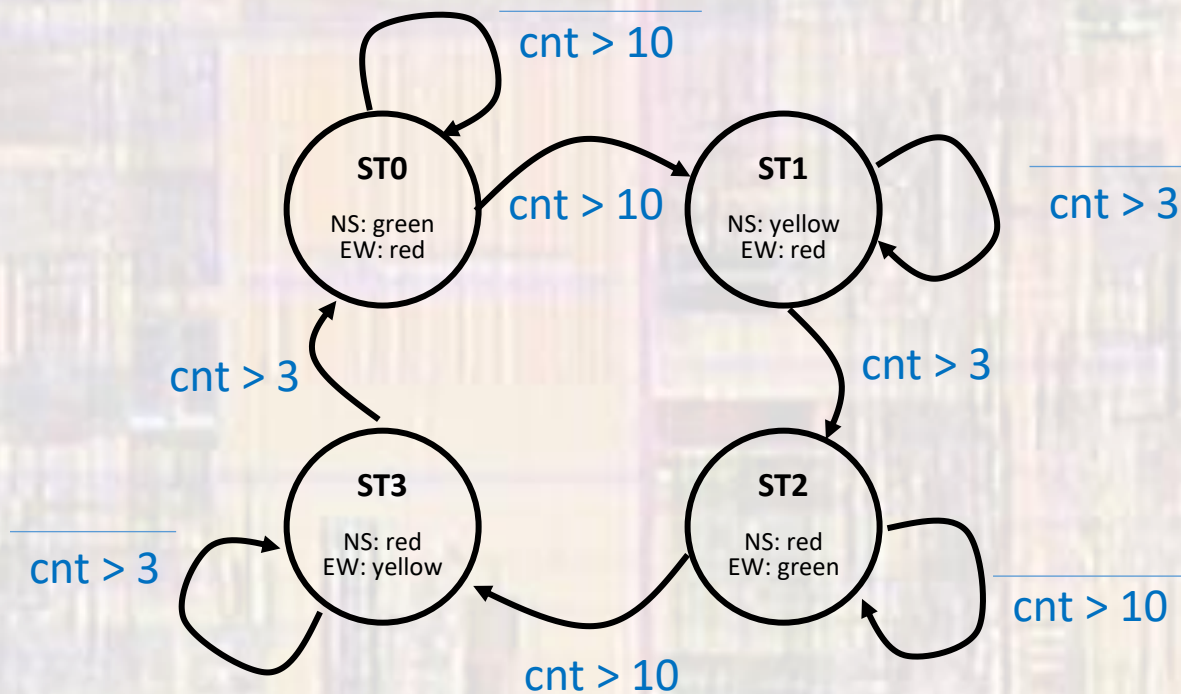
- Example 2
  - Stoplight – transitions
    - Conditional – signals active different amounts of time
      - Use a counter to delay transitions





# State Diagrams

- Types of Transitions

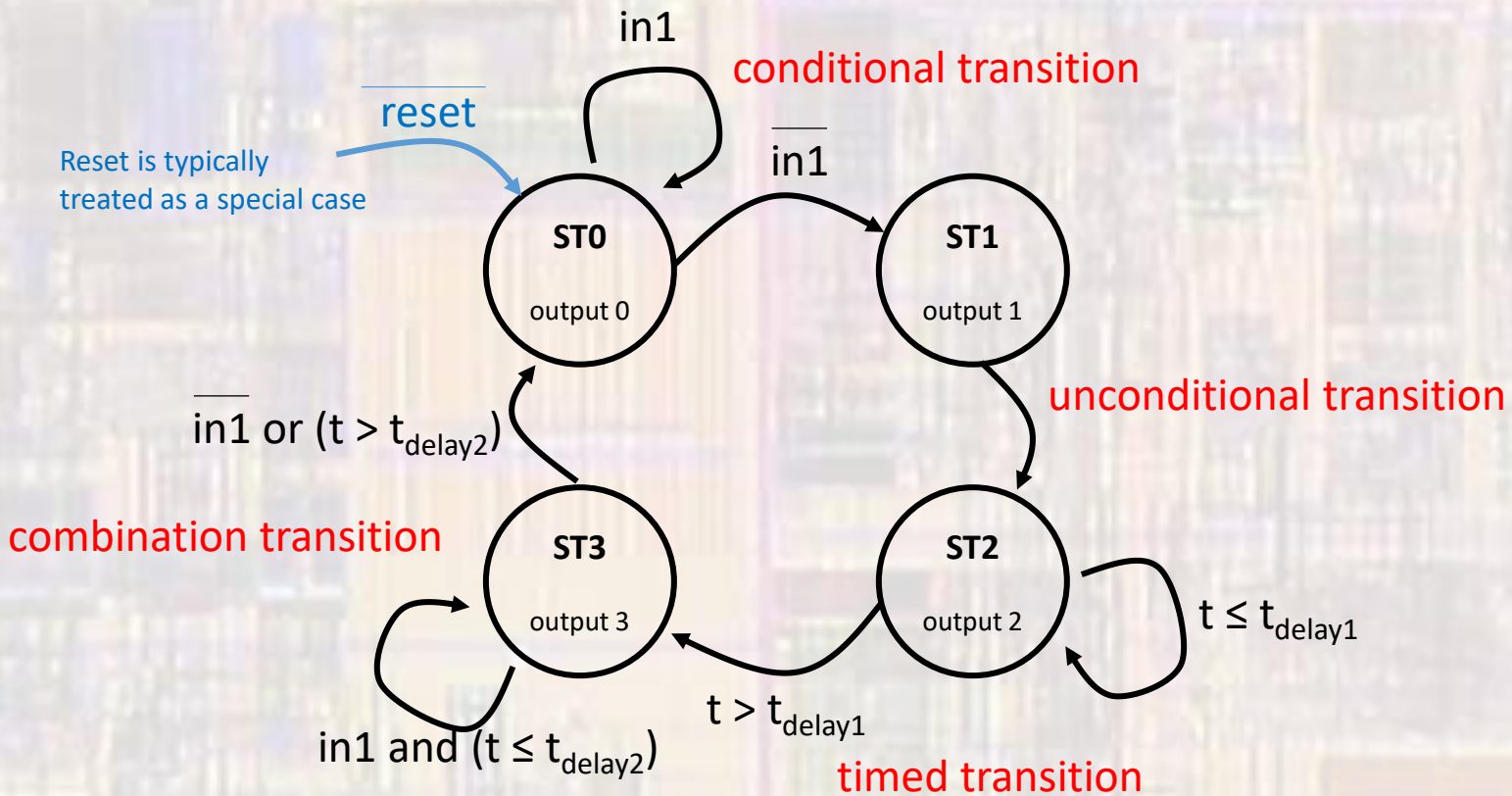


# State Diagrams

- Un-used states
  - Do we care about un-used states?
  - YES!
  - Start-up
  - Bit errors
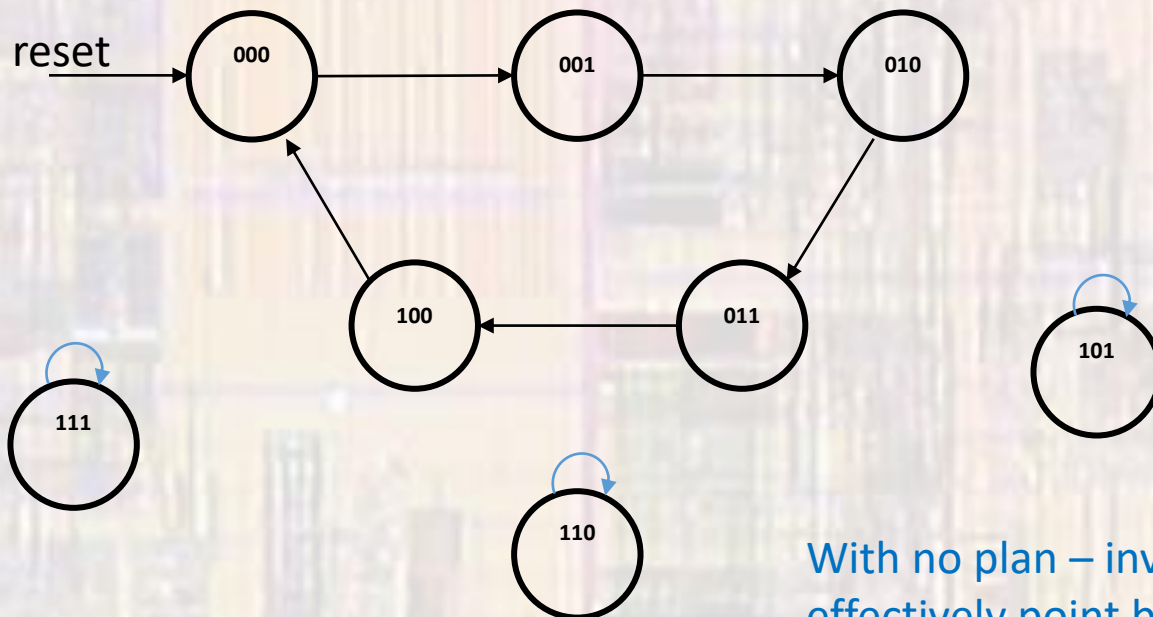
# State Diagrams

- Un-used states
  - Mod 5 counter
    - Unconditional transitions
    - What happens if some error causes the count to be invalid?



With no plan – invalid states effectively point back to themselves


# State Diagrams

- Un-used states
  - Mod 5 counter
  - Recovery solution 1


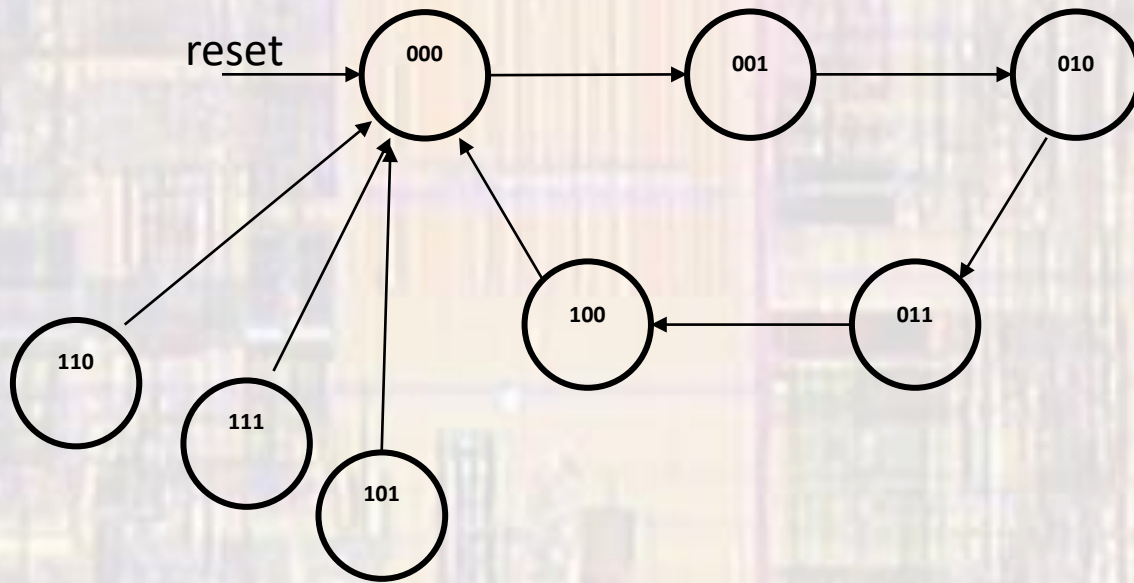
# State Diagrams

- Un-used states
  - Mod 5 counter
  - Recovery solution 2




# State Diagrams

- Redundant / Equivalent States
  - Redundant states lead to more logic than necessary
  - 2 States are equivalent if
    - Outputs are the same
    - Transition to the same next state if the inputs are the same
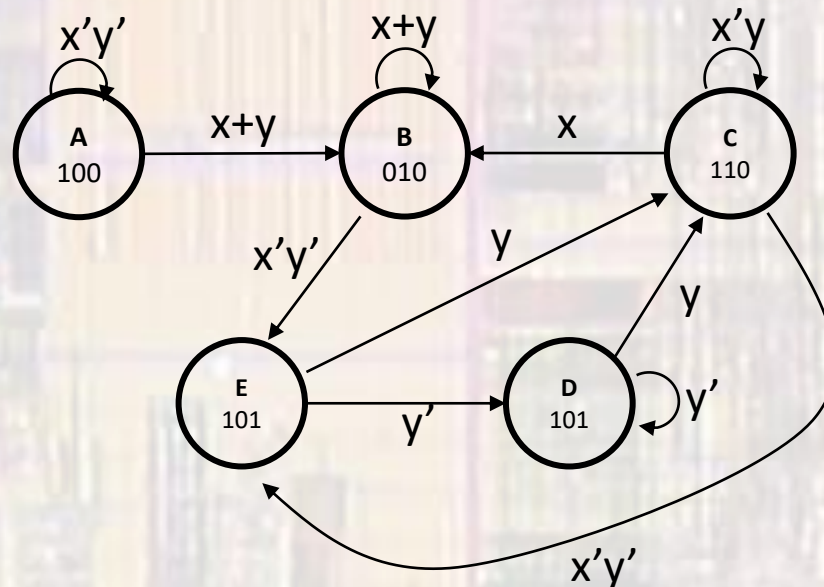
# State Diagrams

- Redundant / Equivalent States
  - Example
    - 5 states
    - 2 inputs
    - 3 outputs




# State Diagrams

- Redundant / Equivalent States

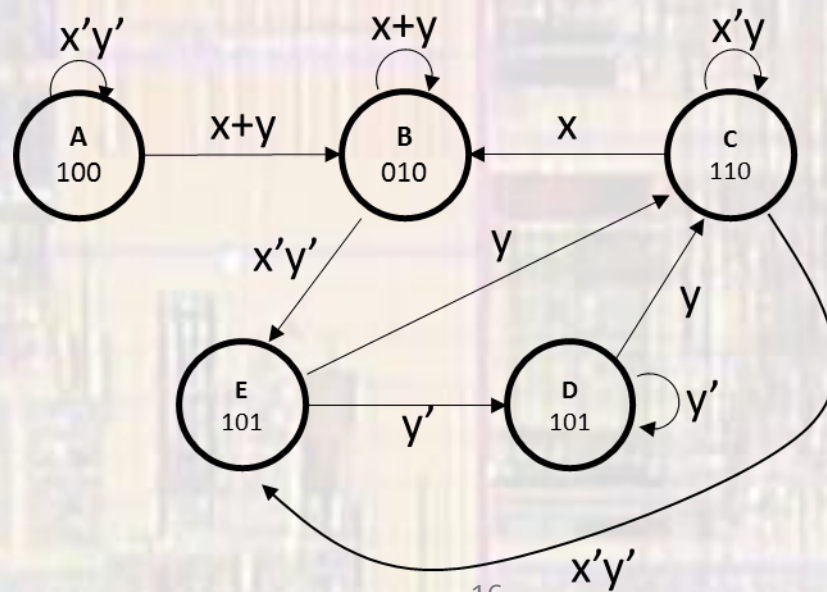- Example

- States D and E
  - have the same output (101)
  - both go to C when  $y$  is true
  - both go to D when  $y'$  is true
- Combine D and E





# State Diagrams

- Redundant / Equivalent States
  - Example
    - 4 states
    - 2 inputs
    - 3 outputs

