

# Behavioral VHDL

Last updated 8/10/24

# Behavioral VHDL

- Behavioral VHDL describes the behavior of the circuit
  - Concurrent logic
  - Sequential Logic
  - Memories
  - Finite State Machines
  - ...

# Behavioral VHDL

- Behavioral VHDL file components
  - Header
    - Description of who created the file
    - Description of the purpose of the block
    - Description of inputs and outputs
  - Inclusions
    - Any libraries that will be referenced in the design
  - Entity
    - Formal definition of the inputs and outputs
    - Any generic parameters are defined here also
  - Architecture
    - Internal signal declarations
    - HDL description of the desired functionality
      - Concurrent, sequential logic

# Behavioral VHDL

- Behavioral VHDL file components - example

```
-----  
--  
-- basic_vhdl.vhdl  
-- Created: 7/16/18  
-- By: johnsontimoj  
-- For: EE3921  
  
--  
  
-- File Overview ---  
--  
-- This file demonstrates basic VHDL file structure  
  
-- File Details ---  
-----
```

Header  
Information

Document  
who, when, what and how

Should be sufficient to allow a  
co-worker to use/modify the design

# Behavioral VHDL

- Behavioral VHDL file components - example

```
-----  
--  
-- basic_vhdl.vhdl  
-- Created: 7/16/18  
-- By: johnsontimoj  
-- For: EE3921  
  
--  
  
-- File Overview ---  
--  
-- This file demonstrates basic VHDL file structure  
  
-- File Details ---  
-----
```

Header Information

```
-- Library inclusions  
library IEEE;  
use ieee.std_logic_1164.all;  
use ieee.numeric_std.all;
```

Library Inclusions

Companies may have their own libraries  
- we will use the IEEE standard library

Only include the portions of the library you need  
- ieee.std\_logic\_1164.all provides:  
    std\_logic  
    std\_logic\_vector  
    9 logic levels  
- ieee.numeric\_std.all provides  
    Signed vectors – signed, unsigned

# Behavioral VHDL

- Behavioral VHDL file components - example

```
--  
-- basic_vhdl.vhdl  
-- Created: 7/16/18  
-- By: johnsontimoj  
-- For: EE3921  
  
--  
  
-- File Overview ---  
--  
-- This file demonstrates basic VHDL file structure  
  
-- File Details ---  
-----
```

Header Information

```
-- Library inclusions  
library IEEE;  
use ieee.std_logic_1164.all;  
use ieee.numeric_std.all;
```

Library Inclusions

Generic

```
-- Entity definition  
entity basic_vhdl is
```

generic( N:

port(

i\_a:

i\_b:

i\_c :

i\_p:

i\_q:

i\_r :


o\_x:

o\_y;

);

end entity;

Entity

 

The Entity is the external view of the block

Generics indicate 'adjustable' aspects of the block

Ports are the i/o connections of the block

Ports have a direction but no interpretation

Wires

Limited to std\_logic or std\_logic\_vector for us

# Behavioral VHDL

- Behavioral VHDL file components - example

```
--  
-- basic_vhdl.vhdl  
-- Created: 7/16/18  
-- By: johnsontimoj  
-- For: EE3921  
--
```

## Header Information

The Architecture is the operational description of the block

Behavioral  
Structural  
Testbench

...

Before the begin

Internal signals

Constants used for readability

After the begin

HDL for the specific application

```
i_q: in  std_logic_vector(N-1 downto 0);  
i_r : in  std_logic_vector(N-1 downto 0);  
o_x: out std_logic;  
o_y: out std_logic_vector(N-1 downto 0)  
);  
end entity;
```

```
-- Behavioral Architecture Definition  
architecture behavioral of basic_vhdl is  
    signal e: std_logic;  
    signal f: std_logic;  
    signal g: std_logic;  
    signal t: unsigned(N-1 downto 0);  
    signal u: signed(N-1 downto 0);
```

Begin

```
e <= i_a and i_b;  
f <= i_c nor i_a;  
g <= e xor f;  
o_x <= g and not i_p(3);
```

```
t <= unsigned(i_p xor i_q);  
u <= signed("11" & i_a & t(4) & i_r(3 downto 2) & i_a & g);  
o_y <= (7 => '1' , 4 => u(5), 1 => i_a , 5 => t(4) , others => '1' ); -- array assignment  
end architecture;
```

## Architecture

Internal signals

Architectural Definition

# Behavioral VHDL

- Behavioral VHDL file components - example

```
--  
-- basic_vhdl.vhdl  
-- Created: 7/16/18  
-- By: johnsontimoj  
-- For: EE3921  
  
--  
  
-- File Overview ---  
--  
-- This file demonstrates basic VHDL file structure  
  
-- File Details ---
```

Header Information

```
-- Library inclusions  
library IEEE;  
use ieee.std_logic_1164.all;  
use ieee.numeric_std.all;
```

Library Inclusions

```
-- Entity definition  
entity basic_vhdl is  
    generic( N:      positive := 8);  
    port(     i_a:  in   std_logic;  
             i_b:  in   std_logic;  
             i_c :  in   std_logic;  
             i_p:  in   std_logic_vector(N-1 downto 0);  
             i_q:  in   std_logic_vector(N-1 downto 0);  
             i_r :  in   std_logic_vector(N-1 downto 0);  
             o_x:  out  std_logic;  
             o_y:  out  std_logic_vector(N-1 downto 0)  
);  
end entity;
```


Entity

```
-- Behavioral Architecture Definition  
architecture behavioral of basic_vhdl is  
    signal e:  std_logic;  
    signal f:  std_logic;  
    signal g:  std_logic;  
    signal t:  unsigned(N-1 downto 0);  
    signal u:  signed(N-1 downto 0);
```

Begin

```
    e <= i_a and i_b;  
    f <= i_c nor i_a;  
    g <= e xor f;  
    o_x <= g and not i_p(3);  
  
    t <= unsigned(i_p xor i_q);  
    u <= signed("11" & i_a & t(4) & i_r(3 downto 2) & i_a & g);  
    o_y <= (7 => '1', 4 => u(5), 1 => i_a , 5 => t(4) others => '1' ); -- array assignment
```

end architecture;

 

Architecture