

# VHDL Memories

Last updated 9/19/23

# VHDL Memories

- Four major VHDL memory solutions
  - Mux based
    - Only applicable for ROMs
  - FlipFlop based
    - Very large – only acceptable for very small memories
  - Inferred
    - Memory is implemented in a pre-built memory block
      - Memory block must exist in the platform
      - Tightly coupled memory – small but very fast
      - General memory – large and not as fast
  - External
    - The memory interface is implemented
    - The memory itself is a separate chip

# VHDL Memories

N words x M bits/word  
N array elements x SLV

- VHDL solution for memories
  - An array of `std_logic_vectors`
  - Coded just like the non-optimized long array of data words
- Array construct
  - New type, that has array type as its basis  
`type my_new_type is array (0 to depth) of some_vhdl_type`
- Memory construct
  - Uses `std_logic_vector`
    - No understanding of the values (signed/unsigned) is assumed, just bits

```
type my_memory is array (0 to depth) of std_logic_vector((wordwidth - 1) downto 0);
```

# VHDL Memories

- ROM – mux based
  - Read only
  - Memory values stored as constants

16 word, 16b/w (2B/w) ROM

```
-- rom_muxbased_constants.vhdl
-- created 4/25/17
-- tj
--
-- rev 0
-----
-- Mux based rom with constants for values
-----
-- inputs: addr
-- outputs: data
-----

library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
use ieee.math_real.all;

entity rom_muxbased_constants is
  generic(
    mem_width:  positive := 16;
    mem_depth:  positive := 16
  );
  port(
    i_addr:  in   std_logic_vector(((integer(ceil(log2(real(mem_depth)))) - 1) downto 0);
    o_data:  out  std_logic_vector((mem_width - 1) downto 0)
  );
end entity;
```

```
architecture behavioral of rom_muxbased_constants is
  -- ROM structure
  type rom_type is array (0 to (mem_depth - 1)) of std_logic_vector ((mem_width - 1) downto 0);
  -- ROM contents
  constant my_ROM: rom_type := (
    0 => X"C010",
    1 => X"C04A",
    2 => X"5180",
    3 => X"02C0",
    4 => X"4640",
    8 => X"2E40",
    9 => X"6B00",
    10 => X"F000",
    others => X"F000"
  );
begin
  o_data <= my_ROM(to_integer(unsigned(i_addr)));
end architecture;
```

Special exception to “no initialization”

notice the frowny face :=(

We can assign values := because they are constant – just tying a wire high or low in the hardware

Calculating the # of address bits based on the mem-depth - see next slide

# VHDL Memories

- ROM – mux based
  - Address bit calculation

```
i_addr: in std_logic_vector(((integer(ceil(log2(real(mem_depth)))) - 1) downto 0));
```

`mem_depth`

only makes sense to be an integer

`real(mem_depth)`

turns it into a real number (not an int)

`log2(real(mem_depth))`

calculates the log base 2

requires a real input

provides a real output

`ceil(log2(real(mem_depth)))`

rounds up (next largest whole real number)

provides support for non- $2^N$  sizes

24 → 4.585 → 5.0

`integer(ceil(log2(real(mem_depth))))`



converts the real to an integer

must be integer to use as index

# VHDL Memories

- ROM – mux based
  - Memory values stored as constants

Modelled as 1 mux per bit in the word

  

# VHDL Memories

- SRAM – flipflop based
  - Using flipflops as our memory storage element
  - The inferred memories on **our FPGA** all require synchronous read paths
    - **To force a flipflop based memory the read path must be asynchronous**
  - Since we want flipflops, we must have some clock controlling the memory
    - Make the write path synchronous
    - Outputs of the flipflops are always available

# VHDL Memories

- SRAM – flipflop based
  - 64 x 32b

64 word, 32b/w (4B/w) FF based SRAM

```
-----  
-- sram_regbased.vhd1  
-- created 4/25/17  
-- tj  
-- rev 0  
-----  
-- synchronous RAM built with registers  
-----  
-- Inputs: clk, addr, we_b, data_in  
-- Outputs: data_out  
-----  
library ieee;  
use ieee.std_logic_1164.all;  
use ieee.numeric_std.all;  
use ieee.math_real.all;  
entity sram_regbased is  
  generic(  
    mem_width: positive := 32;  
    mem_depth: positive := 64  
  );  
  port(  
    i_clk: in std_logic;  
    i_we_b: in std_logic;  
    i_addr: in std_logic_vector(((integer(ceil(log2(real(mem_depth)))) - 1) downto 0));  
    i_data_in: in std_logic_vector((mem_width - 1) downto 0);  
    o_data_out: out std_logic_vector((mem_width - 1) downto 0)  
  );  
end entity;
```

```
architecture behavioral of sram_regbased is  
  --  
  -- create type  
  --  
  type sram_type is array (0 to (mem_depth - 1)) of std_logic_vector ((mem_width - 1) downto 0);  
  -- create memory  
  --  
  signal mySRAM: sram_type;  
  begin  
    --  
    -- SRAM write process  
    --  
    process(i_clk)  
    begin  
      if (rising_edge(i_clk)) then  
        -- write logic  
        if(i_we_b = '0') then  
          mySRAM(to_integer(unsigned(i_addr))) <= i_data_in;  
        end if;  
      end if;  
    end process;  
    --  
    -- SRAM asynchronous read  
    --  
    o_data_out <= mySRAM(to_integer(unsigned(i_addr)));  
  end behavioral;
```

Synchronous write to force FFs

Asynchronous read to prevent inferred memory


64 words X 32 bits  
64 words X 4 Bytes  
64x4x8 bits = 2048 flipflops



# VHDL Memories

- SRAM – register based
  - 64x32b

There is an RTL model for this memory

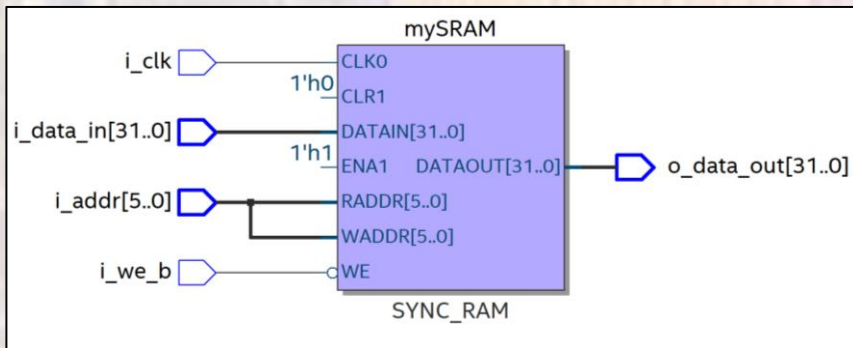

The implementation is in flipflops

Flow Summary	
Search <<Filter>>	
Flow Status	Successful - Fri May 15 11:1
Quartus Prime Version	19.1.0 Build 670 09/22/201
Revision Name	Class_Examples
Top-level Entity Name	sram_regbased
Family	MAX 10
Device	10M50DAF484C7G
Timing Models	Final
Total logic elements	3,472
Total registers	2048
Total pins	72
Total virtual pins	0
Total memory bits	0
Embedded Multiplier 9-bit elements	0
Total PLLs	0
UFM blocks	0
ADC blocks	0

# VHDL Memories

- SRAM – register based – test bench
- 64x32b

```



-- Run Process
run: Process      -- note - no sensitivity list allowed
begin
  -- Initialize values
  ADDR <= (others => '0');
  DATA_IN <= (others => '0');
  WE_B <= '1';

  -- Read from a few addresses
  for i in 0 to 9 loop
    wait for 2*PER;
    ADDR <= std_logic_vector(to_unsigned(i*250,(integer(ceil(log2(real(mem_depth)))))));
  end loop;

  -- Write to a few addresses
  for i in 0 to 9 loop
    wait for 1*PER;
    ADDR <= std_logic_vector(to_unsigned(i*250,(integer(ceil(log2(real(mem_depth)))))));
    DATA_IN <= std_logic_vector(to_unsigned(i*5, mem_width));
    WE_B <= '0';
    wait for 1*PER;
    WE_B <= '1';
  end loop;

  -- Read from a few addresses
  for i in 0 to 9 loop
    wait for 2*PER;
    ADDR <= std_logic_vector(to_unsigned(i*250,(integer(ceil(log2(real(mem_depth)))))));
  end loop;
end process run;
  
```

  Not all addresses tested  
Not all bit values tested



# VHDL Memories

- Memory Test Benches
  - A proper memory testbench would test:
    - All addresses
    - All bits 0 and 1
    - Read ROMs, R/W for RAMs
    - Write\_enable\_bar functionality