

VHDL Memories Flip-Flop Based

Last updated 2/19/25

VHDL Memories – Flip-Flop Based

- Four major VHDL memory solutions
 - Mux based
 - Only applicable for ROMs
 - FlipFlop based
 - Very large – only acceptable for very small memories
 - Inferred
 - Memory is implemented in a pre-built memory block
 - Memory block must exist in the platform
 - Tightly coupled memory – small but very fast
 - General memory – large and not as fast
 - External
 - The memory interface is implemented
 - The memory itself is a separate chip

VHDL Memories – Flip-Flop Based

N words x M bits/word
N array elements x SLV

- VHDL solution for memories
 - An array of `std_logic_vectors`
 - Coded just like the non-optimized long array of data words
- Array construct
 - New type, that has array type as its basis
`type my_new_type is array (0 to depth) of some_vhdl_type`
- Memory construct
 - Uses `std_logic_vector`
 - No understanding of the values (signed/unsigned) is assumed, just bits

```
type my_memory is array (0 to depth) of std_logic_vector((wordwidth - 1) downto 0);
```

VHDL Memories – Flip-Flop Based

- SRAM – flipflop based
 - Using flipflops as our memory storage element
 - The inferred memories on **our FPGA** all require synchronous read paths
 - **To force a flipflop based memory the read path must be asynchronous**
 - Since we want flipflops, we must have some clock controlling the memory
 - Make the write path synchronous
 - Outputs of the flipflops are always available

VHDL Memories – Flip-Flop Based

- SRAM – flipflop based
 - 64 x 32b

64 word, 32b/w (4B/w) FF based SRAM

```
-----  
-- sram_regbased.vhd1  
-- created 4/25/17  
-- tj  
-- rev 0  
-----  
-- synchronous RAM built with registers  
-----  
-- Inputs: clk, addr, we_b, data_in  
-- Outputs: data_out  
-----  
library ieee;  
use ieee.std_logic_1164.all;  
use ieee.numeric_std.all;  
use ieee.math_real.all;  
  
entity sram_regbased is  
  generic(  
    mem_width: positive := 32;  
    mem_depth: positive := 64  
  );  
  port(  
    i_clk: in std_logic;  
    i_we_b: in std_logic;  
    i_addr: in std_logic_vector(((integer(ceil(log2(real(mem_depth)))) - 1) downto 0));  
    i_data_in: in std_logic_vector((mem_width - 1) downto 0);  
    o_data_out: out std_logic_vector((mem_width - 1) downto 0)  
  );  
end entity;
```

```
architecture behavioral of sram_regbased is  
  --  
  -- create type  
  --  
  type sram_type is array (0 to (mem_depth - 1)) of std_logic_vector ((mem_width - 1) downto 0);  
  -- create memory  
  --  
  signal mySRAM: sram_type;  
  
  begin  
  
    -- SRAM write process  
    --  
    process(i_clk)  
    begin  
      if (rising_edge(i_clk)) then  
        -- write logic  
        if(i_we_b = '0') then  
          mySRAM(to_integer(unsigned(i_addr))) <= i_data_in;  
        end if;  
      end if;  
    end process;  
  
    -- SRAM asynchronous read  
    --  
    o_data_out <= mySRAM(to_integer(unsigned(i_addr)));  
  
  end behavioral;
```

Synchronous write
to force FFs


Asynchronous read
to prevent inferred memory

64 words X 32 bits
64 words X 4 Bytes
64x4x8 bits = 2048 flipflops

VHDL Memories – Flip-Flop Based

- SRAM – register based
 - 64x32b

There is an RTL model for this memory

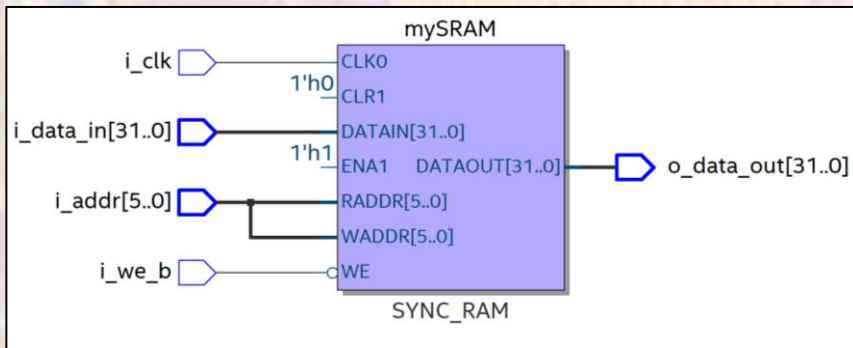

The implementation is in flipflops

Flow Summary	
Search <<Filter>>	
Flow Status	Successful - Fri May 15 11:1
Quartus Prime Version	19.1.0 Build 670 09/22/201
Revision Name	Class_Examples
Top-level Entity Name	sram_regbased
Family	MAX 10
Device	10M50DAF484C7G
Timing Models	Final
Total logic elements	3,472
Total registers	2048
Total pins	72
Total virtual pins	0
Total memory bits	0
Embedded Multiplier 9-bit elements	0
Total PLLs	0
UFM blocks	0
ADC blocks	0

VHDL Memories – Flip-Flop Based

- SRAM – register based – test bench
 - 64x32b



```
-- Run Process
run: Process      -- note - no sensitivity list allowed
begin
  -- Initialize values
  ADDR <= (others => '0');
  DATA_IN <= (others => '0');
  WE_B <= '1';

  -- Read from a few addresses
  for i in 0 to 9 loop
    wait for 2*PER;
    ADDR <= std_logic_vector(to_unsigned(i*250,(integer(ceil(log2(real(mem_depth)))))));
  end loop;

  -- Write to a few addresses
  for i in 0 to 9 loop
    wait for 1*PER;
    ADDR <= std_logic_vector(to_unsigned(i*250,(integer(ceil(log2(real(mem_depth)))))));
    DATA_IN <= std_logic_vector(to_unsigned(i*5, mem_width));
    WE_B <= '0';
    wait for 1*PER;
    WE_B <= '1';
  end loop;

  -- Read from a few addresses
  for i in 0 to 9 loop
    wait for 2*PER;
    ADDR <= std_logic_vector(to_unsigned(i*250,(integer(ceil(log2(real(mem_depth)))))));
  end loop;
end process run;
```

  Not all addresses tested
Not all bit values tested



VHDL Memories – Flip-Flop Based

- Memory Test Benches
 - A proper memory testbench would test:
 - All addresses
 - All bits 0 and 1
 - Read ROMs, R/W for RAMs
 - Write_enable_bar functionality