

VHDL Memories Inferred

Last updated 2/19/25

VHDL Memories – Inferred

- Four major VHDL memory solutions
 - Mux based
 - Only applicable for ROMs
 - FlipFlop based
 - Very large – only acceptable for very small memories
 - **Inferred**
 - Memory is implemented in a pre-built memory block
 - Memory block must exist in the platform
 - Tightly coupled memory – small but very fast
 - General memory – large and not as fast
 - External
 - The memory interface is implemented
 - The memory itself is a separate chip

VHDL Memories – Inferred

N words x M bits/word
N array elements x SLV

- VHDL solution for memories
 - An array of `std_logic_vectors`
 - Coded just like the non-optimized long array of data words
- Array construct
 - New type, that has array type as its basis
`type my_new_type is array (0 to depth) of some_vhdl_type`
- Memory construct
 - Uses `std_logic_vector`
 - No understanding of the values (signed/unsigned) is assumed, just bits

```
type my_memory is array (0 to depth) of std_logic_vector((wordwidth - 1) downto 0);
```

VHDL Memories – Inferred

- ROM – Inferred
 - Using SRAM integrated on the FPGA as our memory storage element – configured with no write path
 - The inferred memories on **our FPGA** all require synchronous read paths
 - **To force an inferred memory the read path must be synchronous**

VHDL Memories – Inferred

- ROM - Inferred
 - Fixed values in the Memory signal
 - Synchronous read path
 - No write path

```
-----  
--  
-- rom_inferred_constants.vhdl  
-- created 4/25/17  
-- tj  
--  
-- rev 0  
-----  
-- Inferred rom with constants for values  
-----  
-- inputs: clk, addr  
-- outputs: data  
-----  
  
library ieee;  
use ieee.std_logic_1164.all;  
use ieee.numeric_std.all;  
use ieee.math_real.all;  
  
entity rom_inferred_constants is  
  generic(  
    mem_width: positive := 16;  
    mem_depth: positive := 16  
  );  
  port(  
    i_clk: in std_logic;  
    i_addr: in std_logic_vector(((integer(ceil(log2(real(mem_depth)))) - 1) downto 0));  
    o_data: out std_logic_vector((mem_width - 1) downto 0)  
  );  
end entity;
```

```
architecture behavioral of rom_inferred_constants is  
  
  -- ROM structure  
  type rom_type is array (0 to (mem_depth - 1)) of std_logic_vector ((mem_width - 1) downto 0);  
  
  -- ROM contents  
  signal my_ROM: rom_type:=(  
    0 => X"C010",  
    1 => X"C04A",  
    2 => X"5180",  
    3 => X"02C0",  
    4 => X"4640",  
  
    8 => X"2E40",  
    9 => X"6B00",  
    10 => X"F000",  
  
    others => X"F000"  
  );  
  
begin  
  
  process (i_clk)  
    begin  
      if (rising_edge(i_clk)) then  
        o_data <= my_ROM(to_integer(unsigned(i_addr)));  
      end if;  
    end process;  
  
end architecture;
```

VHDL Memories – Inferred

- SRAM – Inferred
 - Using SRAM integrated on the FPGA as our memory storage element
 - The inferred memories on **our FPGA** all require synchronous read paths
 - **To force an inferred memory the read path must be synchronous**

VHDL Memories – Inferred

- SRAM – inferred
 - 4K x 8

4K word, 1B/w inferred SRAM

```
-----  
-- sram_inferred.vhdl  
-- created 4/25/17  
-- tj  
-- rev 0  
-----  
-- synchronous RAM using inferred memories  
-----  
--  
-- Inputs: clk, addr, we_b, data_in  
-- Outputs: data_out  
-----  
library ieee;  
use ieee.std_logic_1164.all;  
use ieee.numeric_std.all;  
use ieee.math_real.all;  
entity sram_inferred is  
  generic(  
    mem_width: positive := 8;  
    mem_depth: positive := 4096  
  );  
  port(  
    i_clk: in std_logic;  
    i_we_b: in std_logic;  
    i_addr: in std_logic_vector(((integer(ceil(log2(real(mem_depth)))))) - 1) downto 0);  
    i_data_in: in std_logic_vector((mem_width - 1) downto 0);  
    o_data_out: out std_logic_vector((mem_width - 1) downto 0)  
  );  
end entity;
```

```
architecture behavioral of sram_inferred is  
  -- create type  
  type sram_type is array (0 to (mem_depth - 1)) of std_logic_vector ((mem_width - 1) downto 0);  
  -- create memory  
  signal mySRAM: sram_type;  
begin  
  --  
  -- SRAM write process  
  process (i_clk)  
  begin  
    if (rising_edge(i_clk)) then  
      -- read logic  
      if (i_we_b = '0') then  
        mySRAM(to_integer(unsigned(i_addr))) <= i_data_in;  
      end if;  
      --registered output  
      o_data_out <= mySRAM(to_integer(unsigned(i_addr)));  
    end if;  
  end process;  
end behavioral;
```


Synchronous read
to create inferred memory

VHDL Memories – Inferred

- SRAM – inferred
 - 4K x 8

The implementation used inferred SRAM on the FPGA

There is an RTL model for this memory

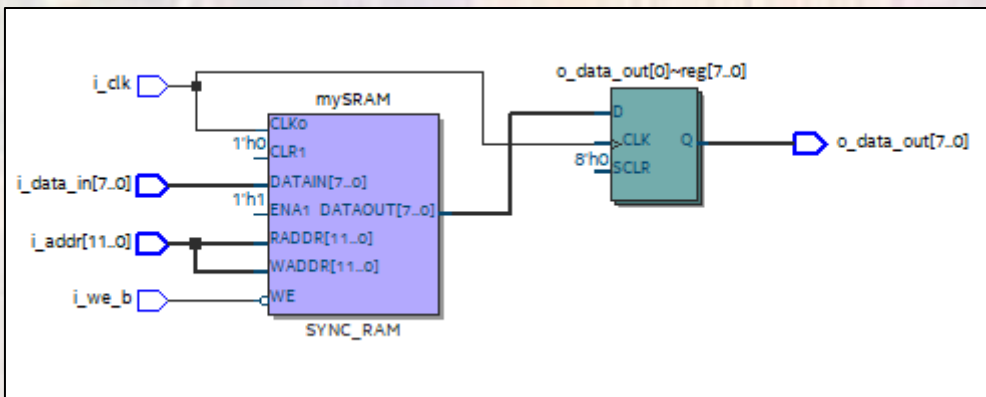

Flow Summary	
Flow Status	Successful - Wed Feb 19 11:43:46 2025
Quartus Prime Version	18.1.0 Build 625 09/12/2018 SJ Lite Edition
Revision Name	Class_examples
Top-level Entity Name	sram_inferred
Family	MAX 10
Device	10M50DAF484C7G
Timing Models	Final
Total logic elements	1 / 49,760 (< 1 %)
Total registers	0
Total pins	30 / 360 (8 %)
Total virtual pins	0
Total memory bits	32,768 / 1,677,312 (2 %)
Embedded Multiplier 9-bit elements	0 / 288 (0 %)
Total PLLs	0 / 4 (0 %)
UFM blocks	0 / 1 (0 %)
ADC blocks	0 / 2 (0 %)

VHDL Memories – Inferred

- SRAM – Inferred – test bench
 - 4K x 8



```
-- Run Process
run: Process      -- note - no sensitivity list allowed
begin
  -- Initialize values
  ADDR <= (others => '0');
  DATA_IN <= (others => '0');
  WE_B <= '1';

  -- Read from a few addresses
  for i in 0 to 9 loop
    wait for 2*PER;
    ADDR <= std_logic_vector(to_unsigned(i*250,(integer(ceil(log2(real(mem_depth)))))));
  end loop;

  -- Write to a few addresses
  for i in 0 to 9 loop
    wait for 1*PER;
    ADDR <= std_logic_vector(to_unsigned(i*250,(integer(ceil(log2(real(mem_depth)))))));
    DATA_IN <= std_logic_vector(to_unsigned(i*5, mem_width));
    WE_B <= '0';
    wait for 1*PER;
    WE_B <= '1';
  end loop;

  -- Read from a few addresses
  for i in 0 to 9 loop
    wait for 2*PER;
    ADDR <= std_logic_vector(to_unsigned(i*250,(integer(ceil(log2(real(mem_depth)))))));
  end loop;
end process run;
```

  Not all addresses tested
Not all bit values tested



VHDL Memories – Inferred

- Memory Test Benches
 - A proper memory testbench would test:
 - All addresses
 - All bits 0 and 1
 - Read ROMs, R/W for RAMs
 - Write_enable_bar functionality