

# VHDL Memories MUX Based

Last updated 2/19/25

# VHDL Memories – Mux Based

- Four major VHDL memory solutions
  - Mux based
    - Only applicable for ROMs
  - FlipFlop based
    - Very large – only acceptable for very small memories
  - Inferred
    - Memory is implemented in a pre-built memory block
      - Memory block must exist in the platform
      - Tightly coupled memory – small but very fast
      - General memory – large and not as fast
  - External
    - The memory interface is implemented
    - The memory itself is a separate chip

# VHDL Memories – Mux Based

N words x M bits/word  
N array elements x SLV

- VHDL solution for memories
  - An array of `std_logic_vectors`
  - Coded just like the non-optimized long array of data words
- Array construct
  - New type, that has array type as its basis  
`type my_new_type is array (0 to depth) of some_vhdl_type`
- Memory construct
  - Uses `std_logic_vector`
    - No understanding of the values (signed/unsigned) is assumed, just bits

```
type my_memory is array (0 to depth) of std_logic_vector((wordwidth - 1) downto 0);
```

# VHDL Memories – Mux Based

- ROM – mux based
  - Read only
  - Memory values stored as constants

16 word, 16b/w (2B/w) ROM

```
-- rom_muxbased_constants.vhdl
-- created 4/25/17
-- tj
--
-- rev 0
-----
-- Mux based rom with constants for values
-----
-- inputs: addr
-- outputs: data
-----

library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
use ieee.math_real.all;

entity rom_muxbased_constants is
  generic(
    mem_width:  positive := 16;
    mem_depth:  positive := 16
  );
  port(
    i_addr:  in   std_logic_vector(((integer(ceil(log2(real(mem_depth)))) - 1) downto 0));
    o_data:  out  std_logic_vector((mem_width - 1) downto 0)
  );
end entity;
```

```
architecture behavioral of rom_muxbased_constants is
  -- ROM structure
  type rom_type is array (0 to (mem_depth - 1)) of std_logic_vector ((mem_width - 1) downto 0);
  -- ROM contents
  constant my_ROM: rom_type := (
    0 => X"C010",
    1 => X"C04A",
    2 => X"5180",
    3 => X"02C0",
    4 => X"4640",
    8 => X"2E40",
    9 => X"6B00",
    10 => X"F000",
    others => X"F000"
  );
begin
  o_data <= my_ROM(to_integer(unsigned(i_addr)));
end architecture;
```

Special exception to "no initialization"

notice the frowny face :=(

We can assign values := because they are constant – just tying a wire high or low in the hardware

Calculating the # of address bits based on the mem-depth - see next slide

# VHDL Memories – Mux Based

- ROM – mux based
  - Address bit calculation

```
i_addr: in std_logic_vector(((integer(ceil(log2(real(mem_depth)))) - 1) downto 0));
```

`mem_depth`

only makes sense to be an integer

`real(mem_depth)`

turns it into a real number (not an int)

`log2(real(mem_depth))`

calculates the log base 2

requires a real input

provides a real output

`ceil(log2(real(mem_depth)))`

rounds up (next largest whole real number)

provides support for non- $2^N$  sizes

24  $\rightarrow$  4.585  $\rightarrow$  5.0

`integer(ceil(log2(real(mem_depth))))`



converts the real to an integer

must be integer to use as index

# VHDL Memories – Mux Based

- ROM – mux based
  - Memory values stored as constants

Modelled as 1 mux per bit in the word

  

# VHDL Memories – Mux Based

- Memory Test Benches
  - A proper memory testbench would test:
    - All addresses