

VHDL Review

Last updated 2/1/24

VHDL Review

- VHDL
- VHSIC Hardware Description Language
- Very High Speed Integrated Circuit

VHDL Review

- Synthesizable constructs
 - Code that can be converted to hardware
 - Concurrent logic
 - Sequential logic (processes with edge detection)
 - Structural logic
 - with-select, when-else, ...
 - if-else, case, ...
- Un-synthesizable constructs
 - Code that cannot be converted to hardware
 - Allowed for simulation, descriptive or compilation purposes
 - Time – wait, delay
 - Loops – while, for, ...
 - Initial conditions
 - Variables
 - Strictly speaking variables can be used in synthesis – but it is very dangerous

VHDL Review

- Concurrent Logic in HDL
 - Concurrent activities are happening all the time (in parallel)
 - Assignment: `<=`
 - with-select
 - when-else
 - ...

`z <= (b or c) when (d = '0') else (e and f);`

z can change if any value changes, immediately

VHDL Review

- Sequential Logic in HDL
 - Sequential activities only happen in certain situations
 - E.g. Rising edge of clock
 - Sequential activities are identified by placing them in a “process” block
 - Process blocks are only executed when a signal in the blocks “sensitivity list” changes
 - Sequential Signals are ONLY updated at the end of the process block
 - Process blocks themselves are concurrent activities

VHDL Review

- Process block format

```
process (sensitivity list)
begin
    actions
end process;
```

```
label process (sensitivity list)
begin
    actions
end process;
```

VHDL Review

- VHDL file components
 - Header
 - Description of who created the file
 - Description of the purpose of the block
 - Description of inputs and outputs
 - Inclusions
 - Any libraries that will be referenced in the design
 - Entity
 - Formal definition of the inputs and outputs
 - Any generic parameters are defined here also
 - Architecture
 - Internal signal declarations
 - Component declarations for hierarchical blocks used in the design
 - Instantiation (hook-up) of any hierarchical blocks used in the design
 - HDL description of the desired functionality
 - Concurrent, sequential, structural logic

VHDL Review

- VHDL file components - example

```
-----  
--  
-- basic_vhdl.vhdl  
-- Created: 7/16/18  
-- By: johnsontimoj  
-- For: EE3921  
--  
  
-- File Overview ---  
--  
-- This file demonstrates basic VHDL file structure  
  
-- File Details ---  
-----
```

Header
Information

Document
who, when, what and how

Should be sufficient to allow a
co-worker to use/modify the design

VHDL Review

- VHDL file components - example

```
-----  
--  
-- basic_vhdl.vhdl  
-- Created: 7/16/18  
-- By: johnsontimoj  
-- For: EE3921  
--  
  
-- File Overview ---  
--  
-- This file demonstrates basic VHDL file structure  
  
-- File Details ---  
-----
```

Header
Information

```
-- Library inclusions  
library IEEE;  
use ieee.std_logic_1164.all;  
use ieee.numeric_std.all;
```

Library
Inclusions

Companies may have their own libraries
- we will use the IEEE standard library

Only include the portions of the library you need
- ieee.std_logic_1164.all provides:

- std_logic
- std_logic_vector
- 9 logic levels

- ieee.numeric_std.all provides

- Signed vectors – signed, unsigned

VHDL Review


• VHDL file components - example

```
-----  
--  
-- basic_vhdl.vhdl  
-- Created: 7/16/18  
-- By: johnsontimoj  
-- For: EE3921  
--  
-- File Overview ---  
--  
-- This file demonstrates basic VHDL file structure  
--  
-- File Details ---  
-----
```

Header Information

```
-- Library inclusions  
library IEEE;  
use ieee.std_logic_1164.all;  
use ieee.numeric_std.all;
```

Library Inclusions

 

The Entity is the external view of the block

Generics indicate 'adjustable' aspects of the block

Ports are the i/o connections of the block
Ports have a direction but no interpretation

Wires
Limited to `std_logic` or `std_logic_vector` for us

```
-- Entity definition  
entity basic_vhdl is  
  generic( N: positive := 8);  
  port(  
    i_a: in std_logic;  
    i_b: in std_logic;  
    i_c: in std_logic;  
    i_p: in std_logic_vector(N-1 downto 0);  
    i_q: in std_logic_vector(N-1 downto 0);  
    i_r: in std_logic_vector(N-1 downto 0);  
    o_x: out std_logic;  
    o_y: out std_logic_vector(N-1 downto 0)  
  );  
end entity;
```

Entity

Generic

Ports

VHDL Review

• VHDL file components - example

```
-----  
--  
-- basic_vhdl.vhdl  
-- Created: 7/16/18  
-- By: johnsontimoj  
-- For: EE3921  
--
```

Header
Information

The Architecture is the operational
description of the block

Behavioral
Structural
Testbench

...

Before the begin

Internal signals

Constants used for readability

After the begin

HDL for the specific application

```
-- Behavioral Architecture Definition  
architecture behavioral of basic_vhdl is  
    signal e: std_logic;  
    signal f: std_logic;  
    signal g: std_logic;  
    signal t: unsigned(N-1 downto 0);  
    signal u: signed(N-1 downto 0);
```

Architecture

Internal
signals

Begin

```
e <= i_a and i_b;  
f <= i_c nor i_a;  
g <= e xor f;  
o_x <= g and not i_p(3);
```

Architectural
Definition

```
t <= unsigned(i_p xor i_q);  
u <= signed("11" & i_a & t(4) & i_r(3 downto 2) & i_a & g);  
o_y <= (7 => '1', 4 => u(5), 1 => i_a, 5 => t(4), others => '1'); -- array assignment
```

```
end architecture;
```

```
    i_q: in std_logic_vector(N-1 downto 0);  
    i_r : in std_logic_vector(N-1 downto 0);  
    o_x: out std_logic;  
    o_y: out std_logic_vector(N-1 downto 0)  
);  
end entity;
```

VHDL Review

• VHDL file components - example

```
-----  
--  
-- basic_vhdl.vhdl  
-- Created: 7/16/18  
-- By: johnsontimoj  
-- For: EE3921  
--  
  
-- File Overview ---  
--  
-- This file demonstrates basic VHDL file structure  
  
-- File Details ---  
-----
```

Header
Information

```
-- Library inclusions  
library IEEE;  
use ieee.std_logic_1164.all;  
use ieee.numeric_std.all;
```

Library
Inclusions

```
-- Entity definition  
entity basic_vhdl is  
  generic( N:          positive := 8);  
  port( i_a: in        std_logic;  
        i_b: in        std_logic;  
        i_c : in        std_logic;  
        i_p: in        std_logic_vector(N-1 downto 0);  
        i_q: in        std_logic_vector(N-1 downto 0);  
        i_r : in        std_logic_vector(N-1 downto 0);  
        o_x: out        std_logic;  
        o_y: out        std_logic_vector(N-1 downto 0)  
  );  
end entity;
```

Entity

```
-- Behavioral Architecture Definition  
architecture behavioral of basic_vhdl is  
  signal e: std_logic;  
  signal f: std_logic;  
  signal g: std_logic;  
  signal t: unsigned(N-1 downto 0);  
  signal u: signed(N-1 downto 0);
```


Architecture

Begin

```
e <= i_a and i_b;  
f <= i_c nor i_a;  
g <= e xor f;  
o_x <= g and not i_p(3);
```

```
t <= unsigned(i_p xor i_q);  
u <= signed("11" & i_a & t(4) & i_r(3 downto 2) & i_a & g);  
o_y <= (7 => '1', 4 => u(5), 1 => i_a, 5 => t(4), others => '1'); -- array assignment
```



end architecture;

 


VHDL Review

- Concurrent / Sequential constructs
 - Concurrent logic can be created with either the concurrent logic constructs **with-select** and **when-else** or the process constructs **if-else**, **case**
 - The process construct versions of concurrent logic are more flexible

with-select
and/or
case

  


when-else
and/or
if-else

 

VHDL Review

- Structural VHDL
 - Explicitly build the logic from hierarchical blocks

- Example
 - Full Adder block

 

```
-----
--
-- full_adder.vhdl
--
-- by: johnsontimoj
--
-- created: 7/5/2017
--
-- version: 0.0
--
-----
--
-- 1 bit full adder
--
-- inputs: a, b, cin
--
-- outputs: s, cout
--
-----
library IEEE;
use ieee.std_logic_1164.all;
```

```
entity full_adder is
    port( i_a:    in std_logic;
          i_b:    in std_logic;
          i_cin:  in std_logic;
          o_s:    out std_logic;
          o_cout: out std_logic
    );
end entity;

architecture behavioral of full_adder is

    signal p: std_logic;
    signal g: std_logic;

begin

    p <= i_a xor i_b;
    g <= i_a and i_b;

    o_s <= p xor i_cin;
    o_cout <= g or (p and i_cin);

end;
```

VHDL Review

- Structural VHDL
 - 4 bit adder example

```
-----  
--  
-- adder_4bit.vhdl  
--  
-- by: tj  
--  
-- created: 7/5/2017  
--  
-- version: 0.0  
--  
-----  
--  
-- 4 bit adder to show cell instantiation  
--  
-- inputs: - a, b, cin  
--  
-- outputs: - sum, cout  
--  
-----  
library IEEE;  
use ieee.std_logic_1164.all;  
  
entity adder_4bit is  
  port( i_A: in std_logic_vector(3 downto 0);  
        i_B: in std_logic_vector(3 downto 0);  
        i_CIN: in std_logic;  
        o_SUM: out std_logic_vector(3 downto 0);  
        o_COUT: out std_logic  
  );  
end entity;  
  
architecture structural of adder_4bit is
```

Top Level
Entity

```
-----  
-- 1 bit full adder prototype  
-----  
component full_adder is  
  port( i_a: in std_logic;  
        i_b: in std_logic;  
        i_cin: in std_logic;  
        o_s: out std_logic;  
        o_cout: out std_logic  
  );  
end component;
```

Component
Prototype

```
-----  
-- intermediate carrys mapped to co  
-- with 1st stage Cout mapped to co(0) and 4th stage cout mapped to co(3)  
-----  
signal co: STD_LOGIC_VECTOR(3 downto 0); -- intermediate carrys  
-- no vector interpretation
```

```
begin  
  
  add_0: full_adder port map( i_a => i_A(0),  
                             i_b => i_B(0),  
                             i_cin => i_CIN,  
                             o_s => o_SUM(0),  
                             o_cout => co(0)  
  );  
  
  add_1: full_adder port map( i_a => i_A(1),  
                             i_b => i_B(1),  
                             i_cin => co(0),  
                             o_s => o_SUM(1),  
                             o_cout => co(1)  
  );  
  
  add_2: full_adder port map( i_a => i_A(2),  
                             i_b => i_B(2),  
                             i_cin => co(1),  
                             o_s => o_SUM(2),  
                             o_cout => co(2)  
  );  
  
  add_3: full_adder port map( i_a => i_A(3),  
                             i_b => i_B(3),  
                             i_cin => co(2),  
                             o_s => o_SUM(3),  
                             o_cout => co(3)  
  );  
  
  o_COUT <= co(3);  
  
end architecture;
```

Instantiations

Explicit
Port
Mapping

VHDL Review

- Structural VHDL
 - 4 bit adder example

