

VHDL Signals

Last updated 8/20/24

VHDL Signals


This is not a programming language
It is a hardware description language

VHDL Signals

- A VHDL **signal** represents a wire
 - A single wire is identified as a **std_logic signal**

Declaration
 
```
signal in1: std_logic;  
signal in2: std_logic;  
signal out1: std_logic;
```



Behavior

```
out1 <= in1 AND in2;
```



VHDL Signals

- A VHDL **signal** represents a wire
 - A bus (collection of wires) is identified as a **std_logic_vector signal**
 - Includes the dimension of the bus – in wire order – 7 6 5 4 3 2 1 0
 - Format: **std_logic_vector((n-1) downto 0)**


Declaration

```
signal inA:      std_logic_vector(7 downto 0);  
signal inB:      std_logic_vector(7 downto 0);  
signal out_AB:   std_logic_vector(7 downto 0);
```

inA 8/
inB 8/
out_AB 8/

Behavior

```
out_AB <= inA OR inB;
```

 

VHDL Signals

- Individual wires in a bus can be identified
 - `signal_name(wire number)`

Declaration

```
signal inA:    std_logic_vector(7 downto 0);  
signal out1:  std_logic;
```



Behavior

```
out1 <= NOT inA(3);
```



VHDL Signals


- Contiguous wires in a bus can be identified
 - `signal_name(wire range)`
 - Format: `signal_name(n downto m)`

Declaration

```
signal inA:    std_logic_vector(7 downto 0);  
signal out1:  std_logic_vector(3 downto 0);
```

Behavior

```
out1 <= NOT inA(6 downto 3);
```

 

VHDL Signals



- Wires and buses can be combined to create a new signal (bus) name
- No new wires are created – just connected to an additional name
- Concatenation operator &

Declaration

```
signal in1:      std_logic;  
signal inA:      std_logic_vector(7 downto 0);  
signal inB:      std_logic_vector(3 downto 0);  
signal new_bus:  std_logic_vector(12 downto 0);
```

Behavior

```
new_bus <= inA & in1 & inB;
```

  

new_bus: inA(7), inA(6), ... inA(0), in1, inB(3), ...inB(0)