

Structural VHDL

Last updated 8/19/24

Structural VHDL

- Structural VHDL implements hierarchical designs
 - Instantiates blocks into a more complex design
 - Complex Designs
 - Test Benches
 - Can include behavioral VHDL content

Structural VHDL

- Structural VHDL file components
 - Header
 - Description of who created the file
 - Description of the purpose of the block
 - Description of inputs and outputs
 - Inclusions
 - Any libraries that will be referenced in the design
 - Entity
 - Formal definition of the inputs and outputs
 - Any generic parameters are defined here also
 - Architecture
 - Internal signal declarations
 - Required for connecting structural blocks
 - Component declarations for hierarchical blocks used in the design
 - Instantiation (hook-up) of any hierarchical blocks used in the design
 - HDL description of the desired additional functionality
 - Concurrent, sequential, structural logic

Structural VHDL

- Structural VHDL file components - example

```
-----  
--  
-- adder_4bit.vhdl  
--  
-- by: tj  
--  
-- created: 7/5/2017  
--  
-- version: 0.0  
--  
-----  
--  
-- 4 bit adder to show cell instantiation  
--  
-- inputs: - a, b, cin  
--  
-- outputs: - sum, cout  
--  
-----
```

Header
Information

Document
who, when, what and how

Should be sufficient to allow a
co-worker to use/modify the design

Structural VHDL

- Structural VHDL file components - example

```
-----  
--  
-- adder_4bit.vhdl  
--  
-- by: tj  
--  
-- created: 7/5/2017  
--  
-- version: 0.0  
--  
-----  
--  
-- 4 bit adder to show cell instantiation  
--  
-- inputs: - a, b, cin  
--  
-- outputs: - sum, cout  
--  
-----
```

Header
Information

```
library IEEE;  
use ieee.std_logic_1164.all;  
use ieee.numeric_std.all;
```

Library
Inclusions

Companies may have their own libraries
- we will use the IEEE standard library

Only include the portions of the library you need
- ieee.std_logic_1164.all provides:

- std_logic
- std_logic_vector
- 9 logic levels


- ieee.numeric_std.all provides

- Signed vectors – signed, unsigned

Structural VHDL

- Structural VHDL file components - example
 - Explicitly build the logic from hierarchical blocks

- Example
 - 1-bit Full Adder block

 

```
-----  
--  
-- full_adder.vhdl  
--  
-- by: johnsontimoj  
--  
-- created: 7/5/2017  
--  
-- version: 0.0  
--  
-----  
--  
-- 1 bit full adder  
--  
-- inputs: a, b, cin  
--  
-- outputs: s, cout  
--  
-----  
  
library IEEE;  
use ieee.std_logic_1164.all;
```

```
entity full_adder is  
    port( i_a:    in std_logic;  
          i_b:    in std_logic;  
          i_cin:  in std_logic;  
          o_s:    out std_logic;  
          o_cout: out std_logic  
    );  
end entity;  
  
architecture behavioral of full_adder is  
  
    signal p: std_logic;  
    signal g: std_logic;  
  
begin  
  
    p <= i_a xor i_b;  
    g <= i_a and i_b;  
  
    o_s <= p xor i_cin;  
    o_cout <= g or (p and i_cin);  
  
end;
```

Structural VHDL

- Structural VHDL file comp
- 4 bit adder example

```
-----  
--  
-- adder_4bit.vhdl  
--  
-- by: tj  
--  
-- created: 7/5/2017  
--  
-- version: 0.0  
--  
-----  
--  
-- 4 bit adder to show cell instantiation  
--  
-- inputs: - a, b, cin  
--  
-- outputs: - sum, cout  
--  
-----  
library IEEE;  
use ieee.std_logic_1164.all;  
  
entity adder_4bit is  
    port( i_A: in std_logic_vector(3 downto 0);  
          i_B: in std_logic_vector(3 downto 0);  
          i_CIN: in std_logic;  
          o_SUM: out std_logic_vector(3 downto 0);  
          o_COUT: out std_logic  
    );  
end entity;  
  
architecture structural of adder_4bit is
```

Top Level
Entity

```
-----  
-- 1 bit full adder prototype  
-----  
component full_adder is  
    port( i_a: in std_logic;  
          i_b: in std_logic;  
          i_cin: in std_logic;  
          o_s: out std_logic;  
          o_cout: out std_logic  
    );  
end component;  
-----  
-- intermediate carries mapped to co  
-- with 1st stage Cout mapped to co(0) and 4th stage cout mapped to co(3)  
-----  
signal co: STD_LOGIC_VECTOR(3 downto 0); -- intermediate carries  
-- no vector interpretation
```

Component
Prototype

```
begin  
  
    add_0: full_adder port map( i_a => i_A(0),  
                               i_b => i_B(0),  
                               i_cin => i_CIN,  
                               o_s => o_SUM(0),  
                               o_cout => co(0)  
    );  
  
    add_1: full_adder port map( i_a => i_A(1),  
                               i_b => i_B(1),  
                               i_cin => co(0),  
                               o_s => o_SUM(1),  
                               o_cout => co(1)  
    );  
  
    add_2: full_adder port map( i_a => i_A(2),  
                               i_b => i_B(2),  
                               i_cin => co(1),  
                               o_s => o_SUM(2),  
                               o_cout => co(2)  
    );  
  
    add_3: full_adder port map( i_a => i_A(3),  
                               i_b => i_B(3),  
                               i_cin => co(2),  
                               o_s => o_SUM(3),  
                               o_cout => co(3)  
    );  
  
    o_COUT <= co(3);  
  
end architecture;
```

Instantiations

Explicit
Port
Mapping

Structural VHDL

- Structural VHDL file components - example
 - 4 bit adder example

