

Circuit Basics

Last updated 1/10/24

Circuit Basics

- Kirchhoff's Laws
 - Current Law: $\sum \text{currents}_{\text{entering a node}} = 0$
 - Voltage Law: $\sum \text{voltages}_{\text{around a loop}} = 0$
- Resistance
 - $V = IR$
 - Series Resistors: $R_{\text{series}} = \sum_{n=1}^m R_n$
 - Parallel Resistors: $1/R_{\text{parallel}} = \sum_{n=1}^m 1/R_n$

Circuit Basics

- Capacitance

- $Q = CV$

- $i = C \frac{dv}{dt}$

- Parallel Capacitors:

$$C_{series} = \sum_{n=1}^m C_n$$

- Series Capacitors:

$$1/C_{parallel} = \sum_{n=1}^m 1/C_n$$

- Inductance

- $\Phi_m = LI$

- $v = L \frac{di}{dt}$

- Series Inductors:

$$L_{series} = \sum_{n=1}^m L_n$$

- Parallel Inductors:


$$1/L_{parallel} = \sum_{n=1}^m 1/L_n$$

Circuit Basics

- RC transients
 - R
 - Output impedance of a circuit (gate)
 - Wire (trace) resistance
 - C
 - Input capacitance of a circuit (gate)
 - Wire (trace) capacitance
 - τ
 - RC time constant
 - Units is seconds

Circuit Basics

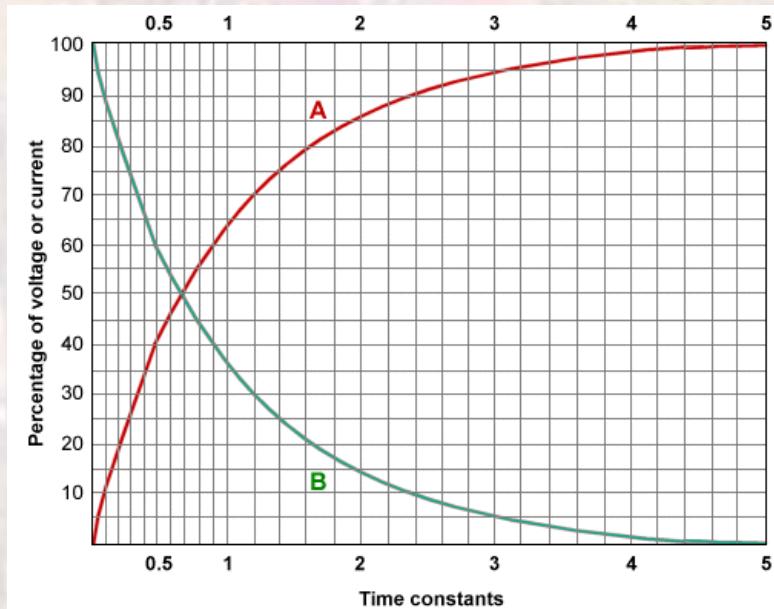- RC transients
 - Rising (charging) transient*
 - $v(t) = v_{final} (1 - e^{-t/\tau})$
 - * assuming $v_{initial} = 0v$
 - Falling (discharging) transient*
 - $v(t) = v_{initial} e^{-t/\tau}$
 - * assuming $v_{final} = 0v$
 - General transient
 - $v(t) = v_{final} + (v_{initial} - v_{final}) e^{-t/\tau}$




50% - 0.693τ

98% - 4τ

Circuit Basics

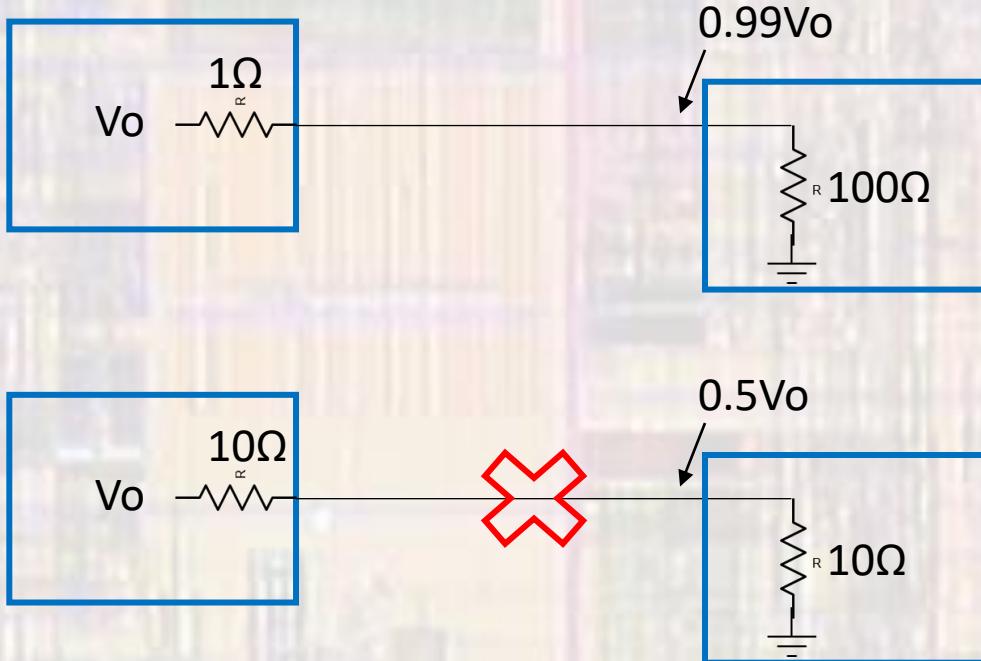
- Input / Output Impedance
 - Want low output impedance driving high input impedance




Circuit Basics

- Common Symbols

current source

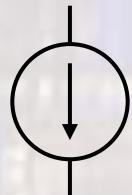

voltage source

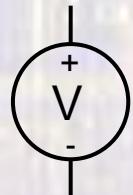

signal source




Battery
Voltage
Source



power & ground symbols




VSS

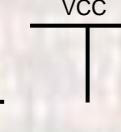


VEE




fixed
resistor

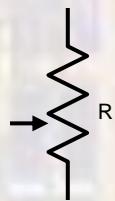

potentiometer

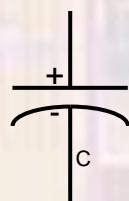

polarized
capacitor

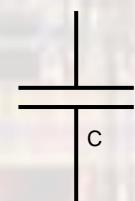

unpolarized
capacitor



inductor

