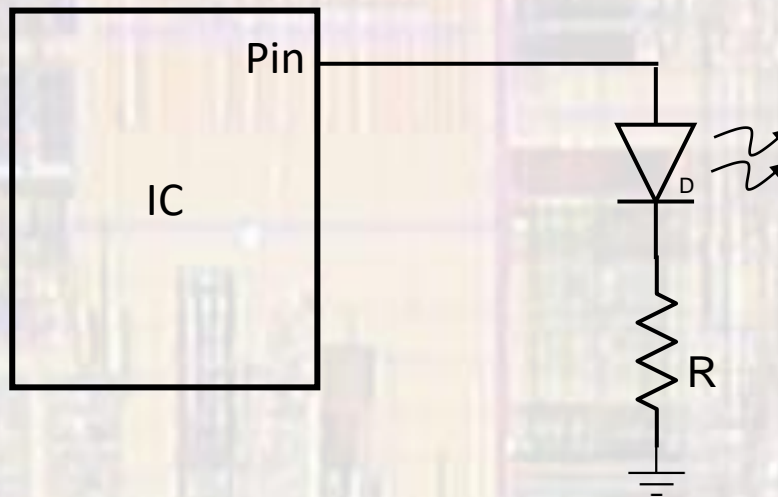


Diode Circuits

Last updated 1/10/24


LED Driver

- Determine the resistor value that will maximize the LED brightness
 - $V_D = 1.1V$
 - $V_{pin} = 0V - 3.3V$
 - $I_{pin_{max}} = +/- 10mA$




Half-wave Rectifier

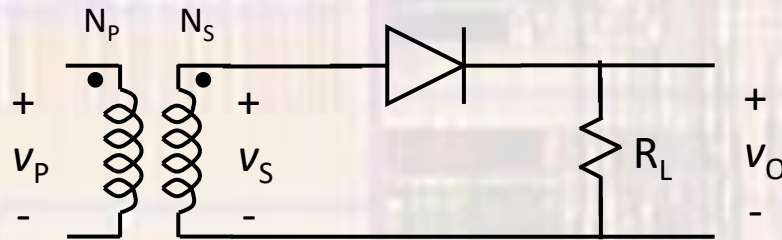- Sketch the output waveform v_O over 2 full input cycles
 - $v_p = 120\text{Vrms}$
 - $N_p = 10 \times N_s$
 - $v_D = 0.7\text{V}$
 - $R_L = 1\text{K}\Omega$



Bridge Rectifier

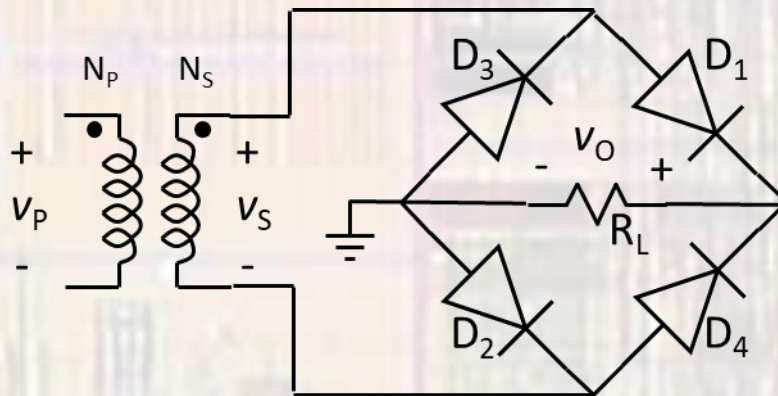- Sketch the output waveform v_O over 2 full input cycles
 - $v_p = 120\text{Vrms}$
 - $N_p = 10 \times N_s$
 - $v_D = 0.7\text{V}$
 - $R_L = 1\text{K}\Omega$



Diode Circuit

- Plot the voltage at node 1 vs V_{batt} from 0 to 12V
 - Assume $V_D = 0.7V$

