

Diodes

Last updated 1/10/24

Ideal Diode Equation

$$I_D = I_S \left[e^{\left(\frac{qV_A}{nkT} \right)} - 1 \right] = I_S \left[e^{\left(\frac{V_A}{nV_T} \right)} - 1 \right]$$

$$I_S = qA \left[\frac{D_N}{L_N} n_{p0} + \frac{D_P}{L_P} p_{n0} \right]$$

Proportional to Area (A)
Inversely proportional to Doping (n_{p0} , p_{n0})
Typically, $10^{-12}\text{A} - 10^{-18}\text{A}$

n


Accounts for non-idealities
Typically, between 1 and 2

$$V_T = \frac{q}{kT}$$

$V_T \cong 26\text{mV} @ RT$


Diode Models

- Real diode behavior

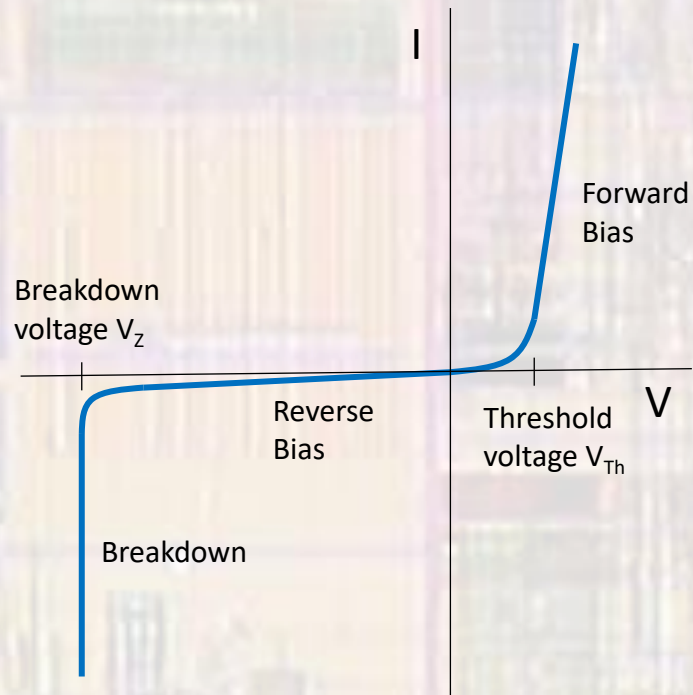

Diode Models

- Real diode behavior


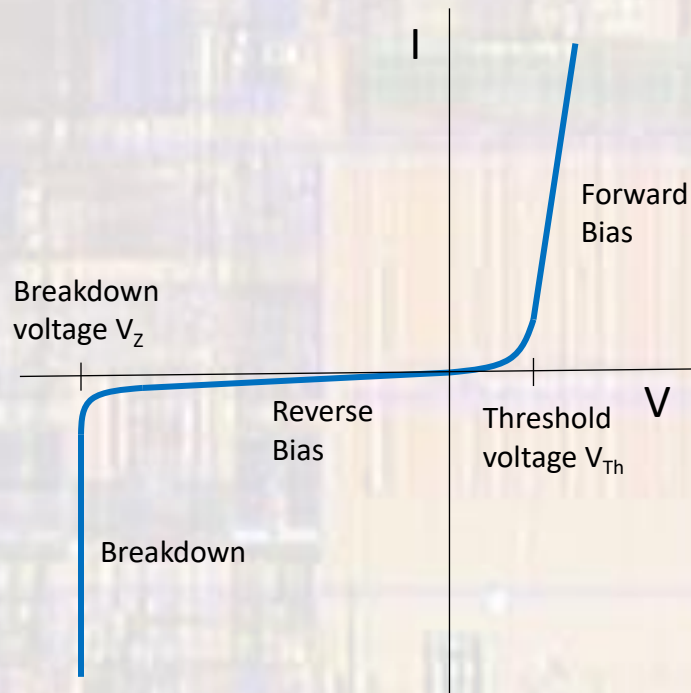


$$I_D = I_S \left(e^{\frac{V_D}{nV_T}} - 1 \right)$$

$V_D > V_Z$



Diode Models

- Ideal diode models
 - Switch model

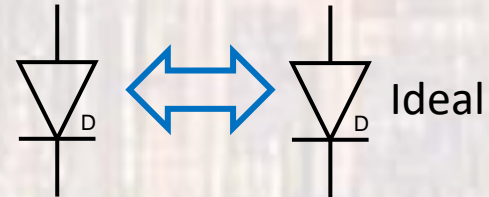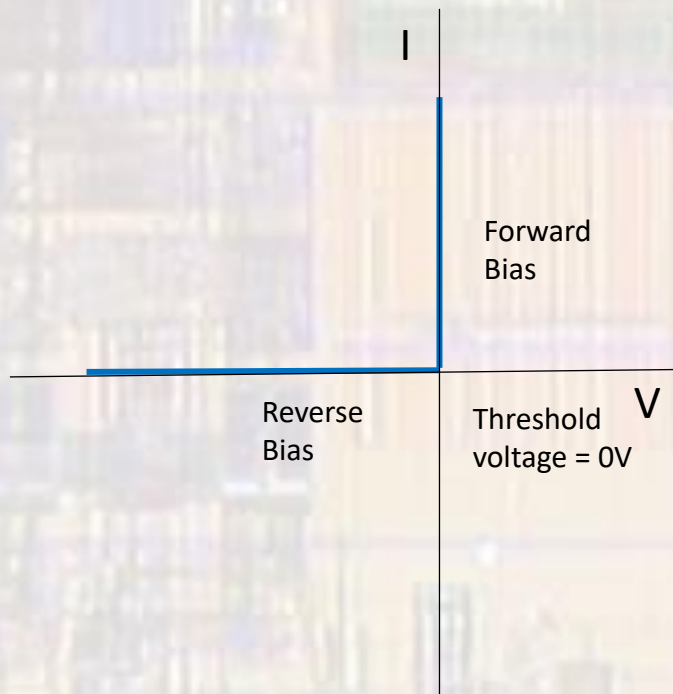



Diode Models

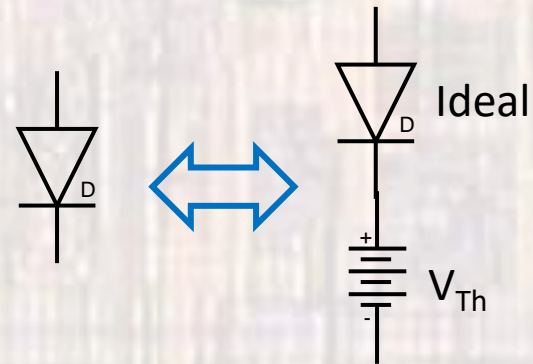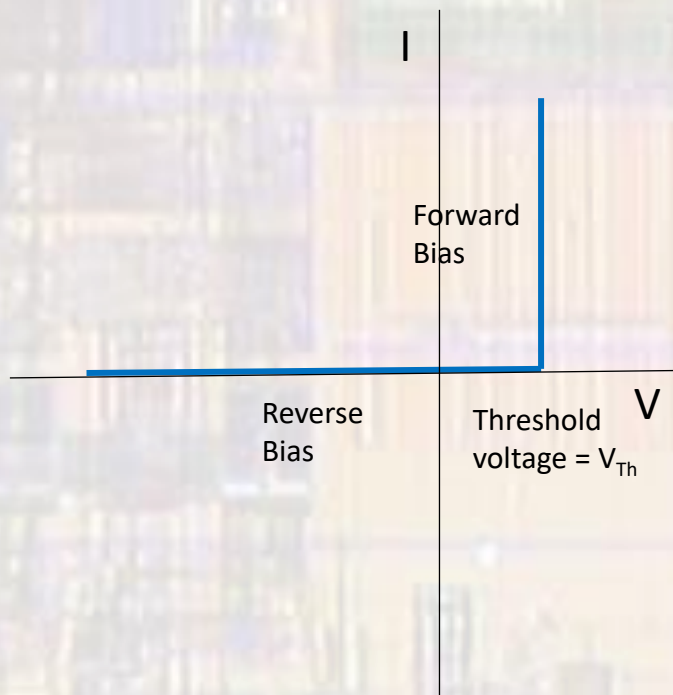- Ideal diode models
 - Switch model with Turn-on voltage




Diode Models

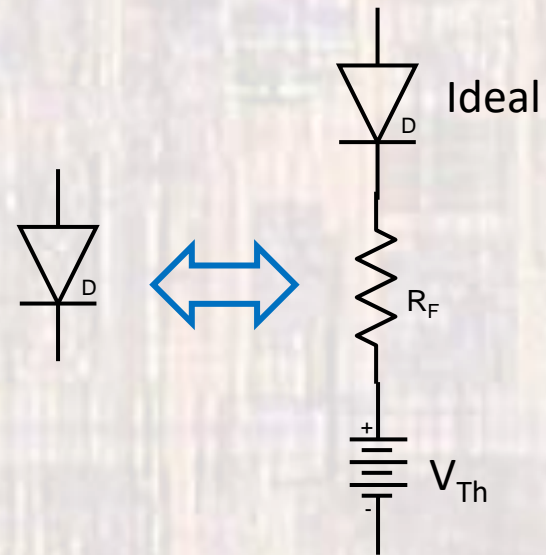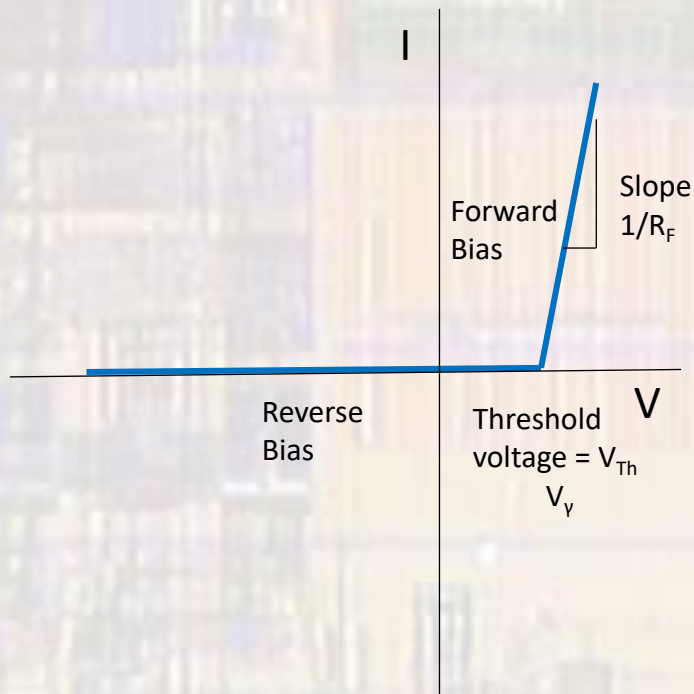- Ideal diode models
 - Piecewise Linear model





Diode Models

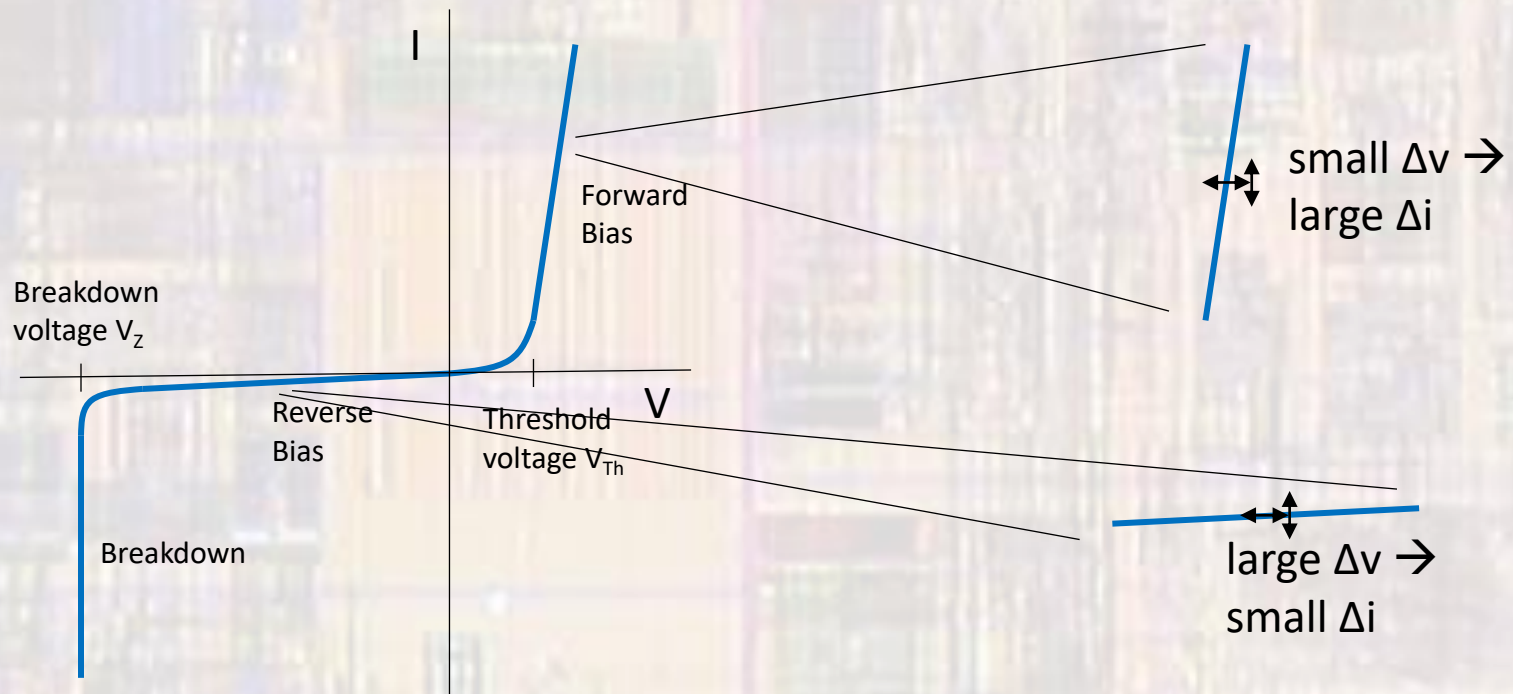- Small Signal Model
 - Consider the I-V characteristics constant



Diode Models


- Small Signal Model

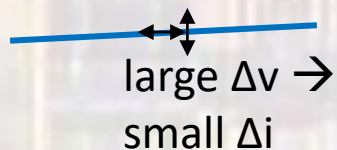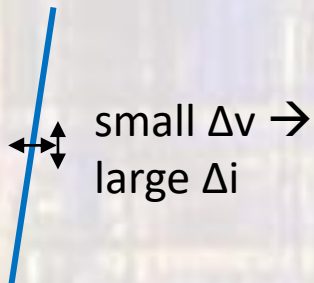

I_D – DC current
 V_D – DC voltage
 i_d – small signal current
 v_d – small signal voltage

$$i_d = \left(\frac{I_D}{V_T} \right) v_d = \left(\frac{1}{r_d} \right) v_d$$

$$r_d = \left(\frac{V_T}{I_D} \right)$$

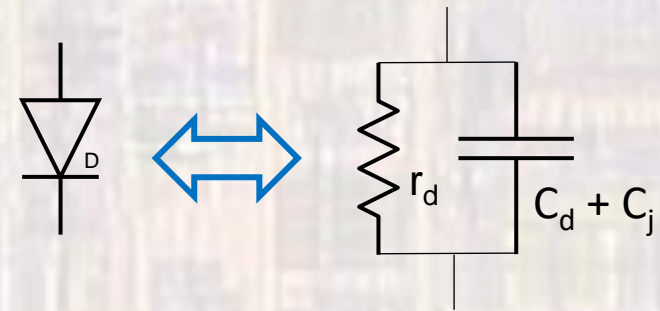


C_j – Junction Capacitance
 C_d – Diffusion Capacitance

C_j – dominant in reverse bias
 C_d – dominant in forward bias



Diode Switching

- In forward bias, carriers are traversing the depletion region and create an excess of minority carriers in the N and P regions

Reverse Bias

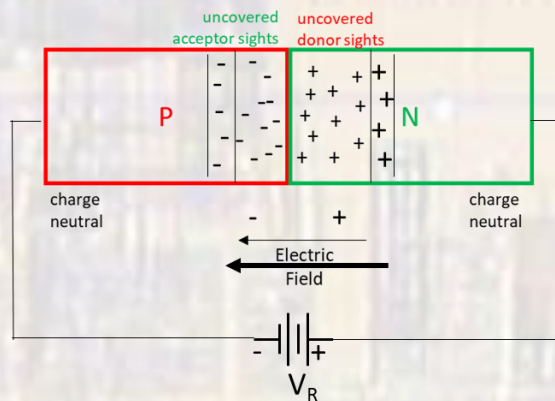


Forward Bias

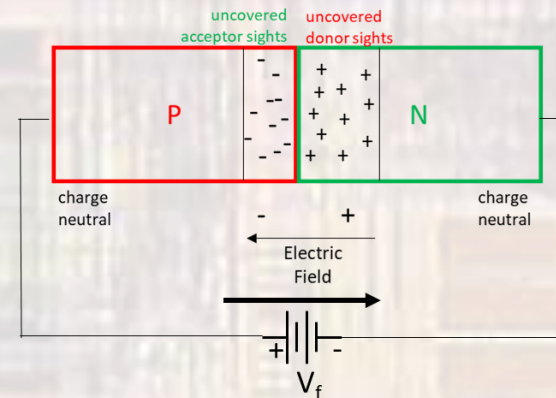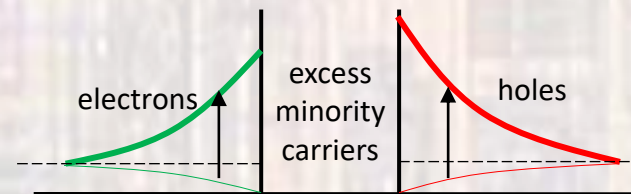


Diode Switching

- Switching from forward bias to reverse bias

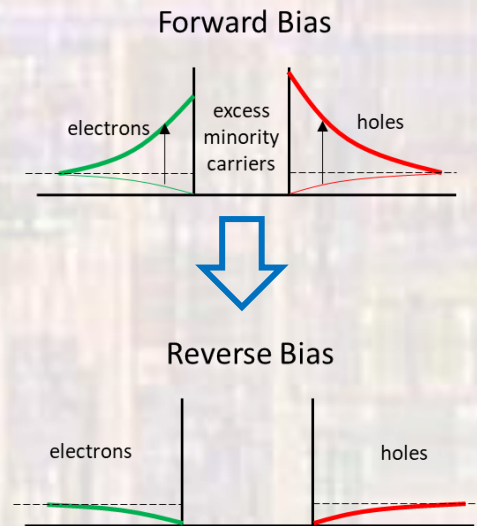- Excess minority carriers must be removed
- → reverse (negative) current flow
 - Amplitude is a function of V_F and minority carrier lifetimes
 - Storage Time – t_s
 - Time for concentrations to reach their 0V bias level
 - Recovery Time – t_r
 - Time for concentrations to reach their reverse bias level
 - Reverse Recovery Time – t_{rr}
 - Sum of t_s and t_r




Turn Off

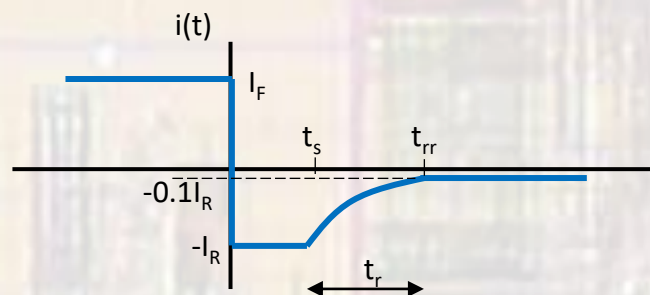





Diode Switching

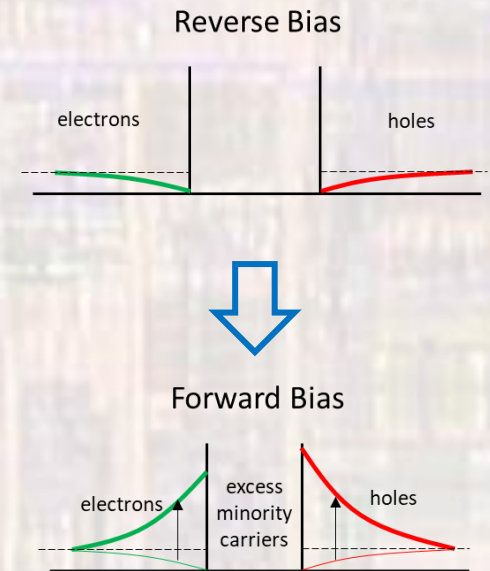- Switching from reverse bias to forward bias
 - No excess minority carriers to be removed
 - → No storage time
 - Fast transitions



Diode Switching




- Simulation Example – 5V

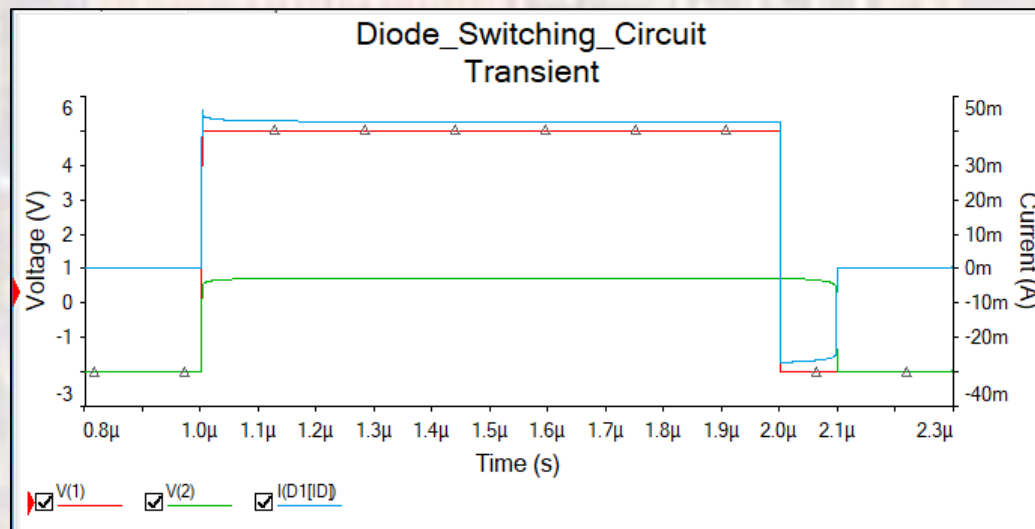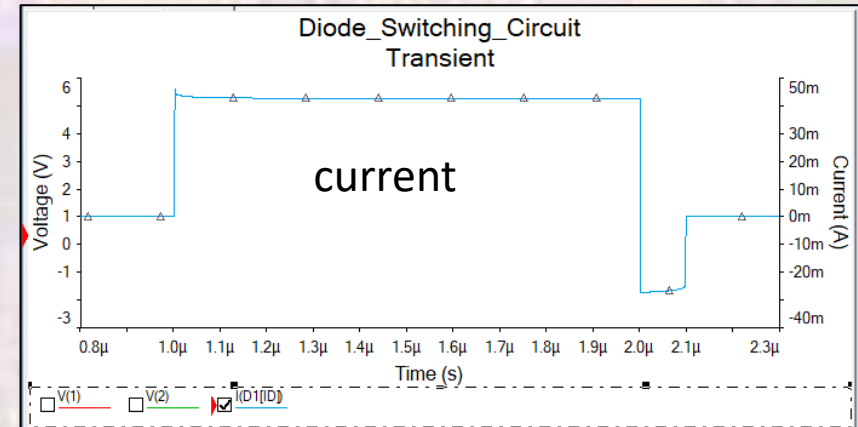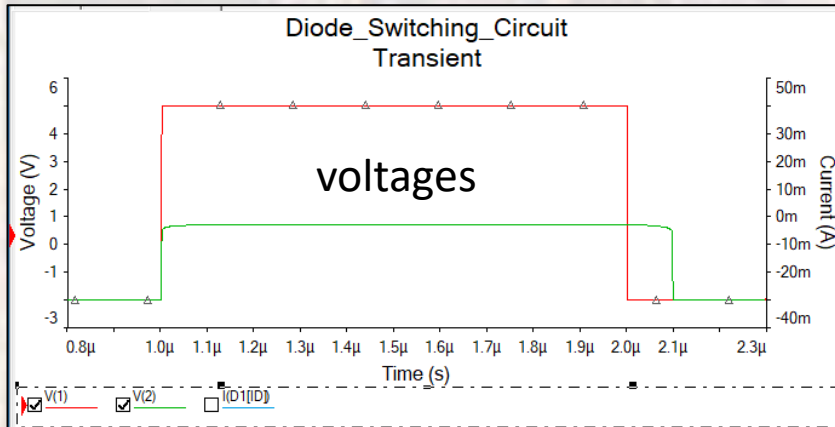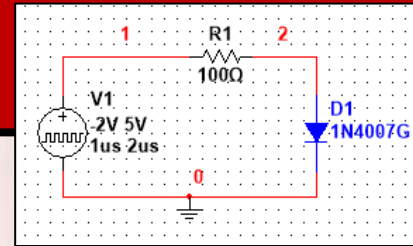


$t_{rr} = 100\text{ns}$

Diode Switching

- Simulation Example – 15V

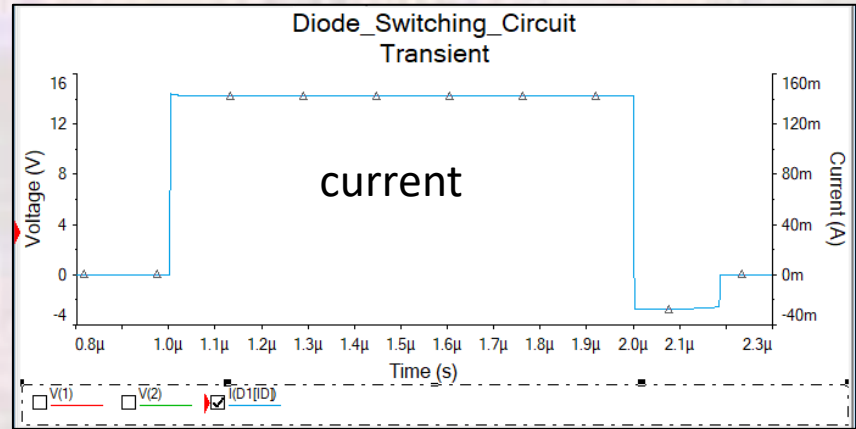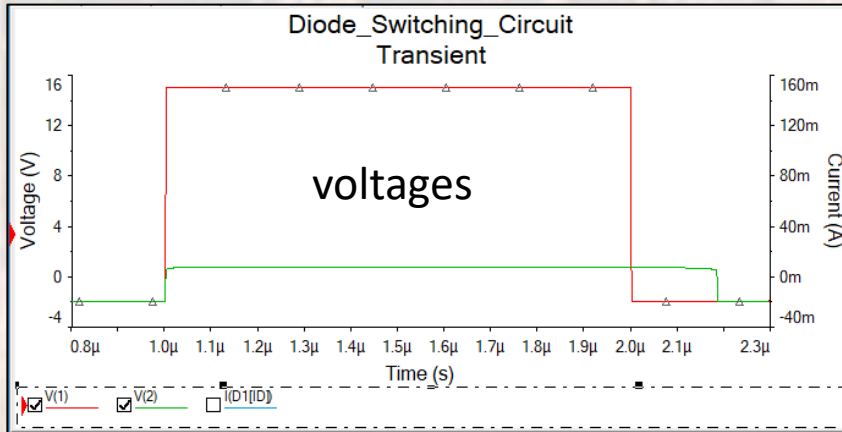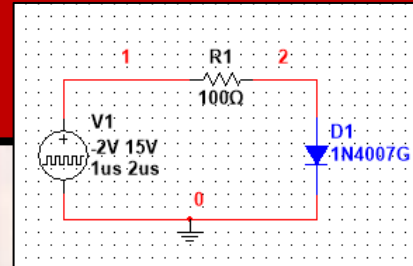


$t_{rr} = 200\text{ns}$

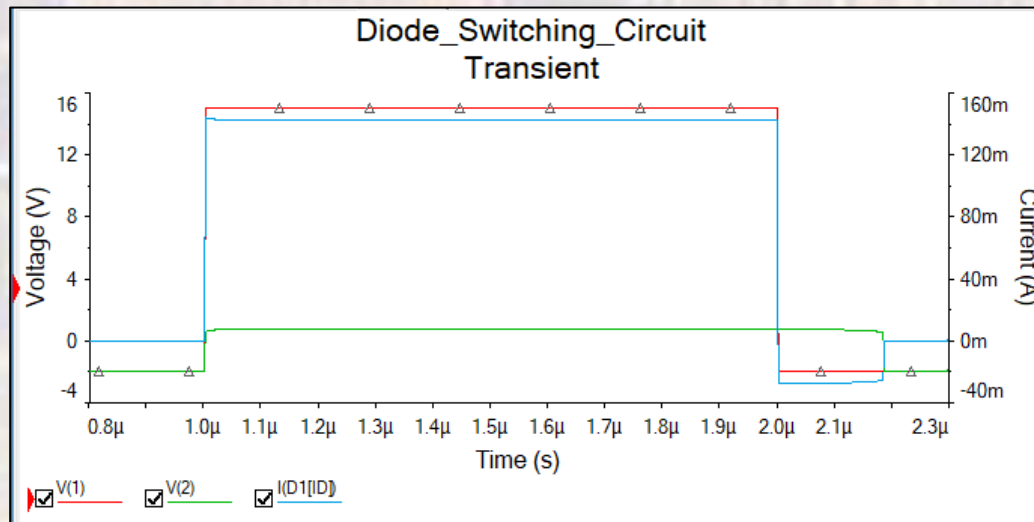

Diode Circuit Analysis

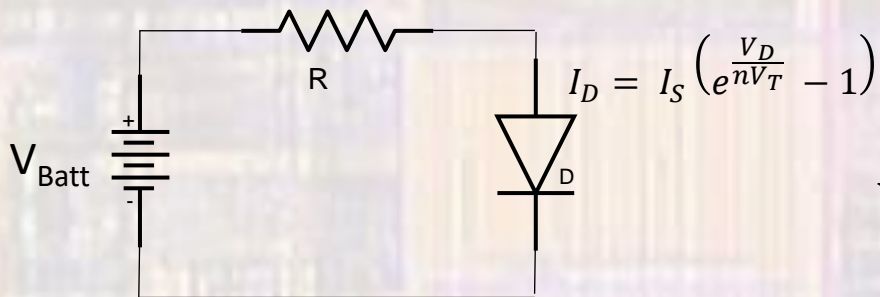- “Exact” Solution
 - Transcendental Equation
 - You have the tools to solve this



$$V_{Batt} = I_D R + V_D$$


$$V_{Batt} = I_S \left(e^{\frac{V_D}{nV_T}} - 1 \right) R + V_D$$

$$I_S = 5.3e-15, n = 1, V_{batt} = 3.3V, R = 1K\Omega$$
$$V_D = 0.6999V, I_D = 2.601mA$$

Diode Circuit Analysis

- Ideal Solution

- $V_D = V_{Th} = 0V$

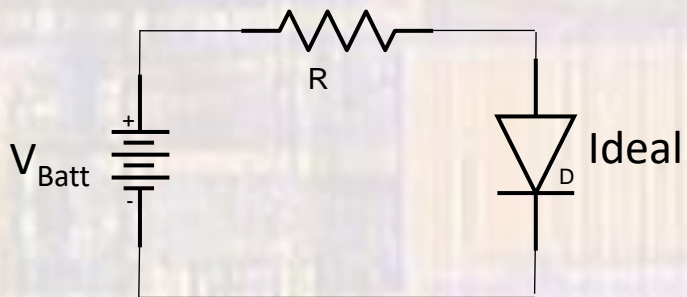

$$V_{Batt} = I_D R + V_D$$


$$V_{Batt} = I_D R$$

$$I_D = V_{Batt} / R$$

$$V_{batt} = 3.3V, R = 1K\Omega, V_{Th} = 0.7V, R_F = 5\Omega$$
$$I_D = 3.3mA$$

Diode Circuit Analysis

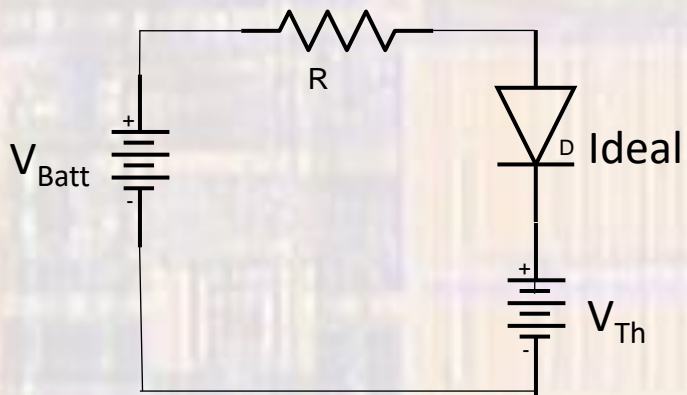- Ideal Solution (with V_{Th})
 - $V_D = V_{Th} = 0.7V$



$$V_{Batt} = I_D R + V_{Th}$$


$$I_D = (V_{Batt} - V_{Th})/R$$

$$V_{batt} = 3.3V, R = 1K\Omega, V_{Th} = 0.7V, R_F = 5\Omega$$
$$I_D = 2.60mA$$

Diode Circuit Analysis

- Piecewise Linear Solution

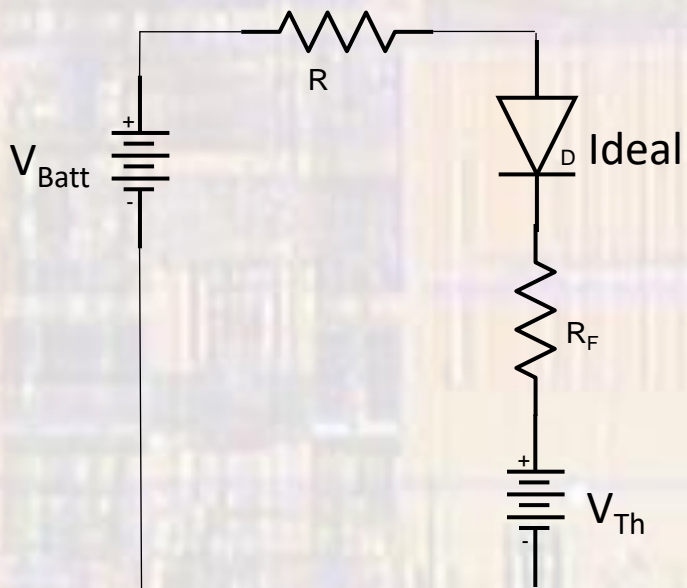- $V_{Th} = V_y = 0.7V$
- $R_F = 5\Omega$



$$V_{Batt} = I_D R + I_D R_F + V_{Th}$$

$$I_D = (V_{Batt} - V_{Th}) / (R + R_F)$$

$$V_{batt} = 3.3V, R = 1K\Omega, V_{TH} = 0.7V, R_F = 5\Omega$$
$$I_D = 2.587mA$$

Diode Circuit Analysis

- Comparison

Exact

Simulate instead

$$V_{Batt} = I_S \left(e^{\frac{V_D}{nV_T}} - 1 \right) R + V_D$$

$$I_S = 5.3e-15, n = 1, V_{batt} = 3.3V, R = 1K\Omega$$

$$V_D = 0.6999V, I_D = 2.601mA$$

Ideal

Only acceptable for determining functionality

$$V_{Batt} = I_D R$$

$$V_{batt} = 3.3V, R = 1K\Omega, V_{TH} = 0.7V, R_F = 5\Omega$$

$$I_D = 3.3mA$$

Ideal w/ V_{Th}

The best choice for almost all situations

$$V_{Batt} = I_D R + V_{Th}$$

$$V_{batt} = 3.3V, R = 1K\Omega, V_{TH} = 0.7V, R_F = 5\Omega$$

$$I_D = 2.60mA$$

Piecewise linear


$$V_{Batt} = I_D R + I_D R_F + V_{Th}$$

$$V_{batt} = 3.3V, R = 1K\Omega, V_{TH} = 0.7V, R_F = 5\Omega$$

$$I_D = 2.587mA$$



Other Diodes

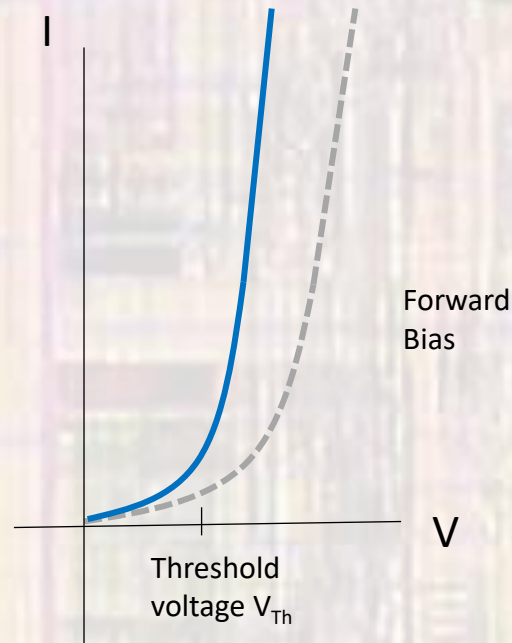- Schottky Barrier Diode
 - Metal – Semiconductor junction
 - Lower turn on voltage (0.2V to 0.3V)




Other Diodes

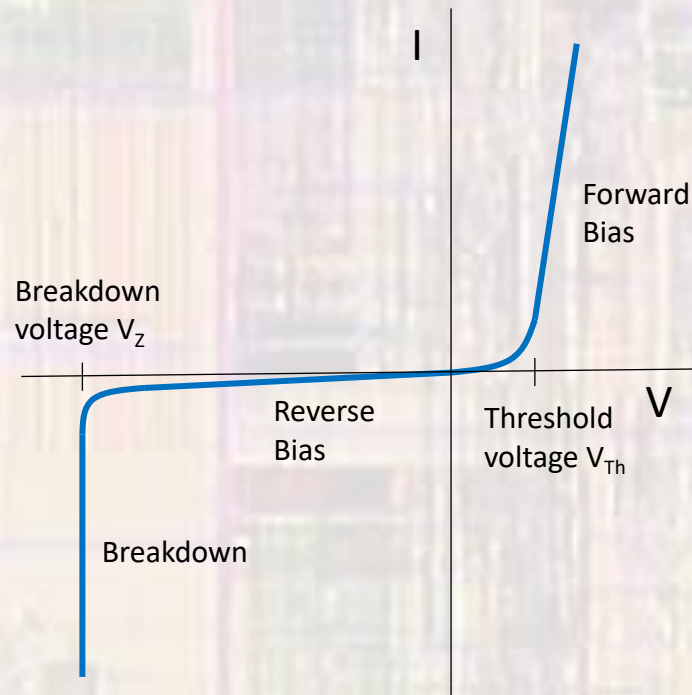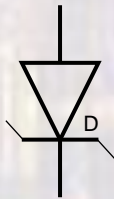- Zener Diode
 - Well managed breakdown voltage




Other Diodes

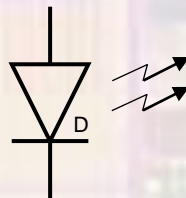- Light Emitting Diode
 - Direct bandgap semiconductor
 - When holes and electrons recombine in the bulk region photons are emitted
 - Typically higher turn on voltages (1.2V – 1.8V)



Other Diodes

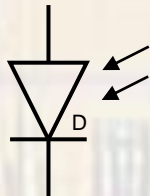- Photo Diode
 - P-I-N Diode
 - I is an intrinsic layer
 - Light applied to the intrinsic layer creates hole-electron pairs
 - These holes and electrons are swept away due to the electric field → current



Solar Cell

