
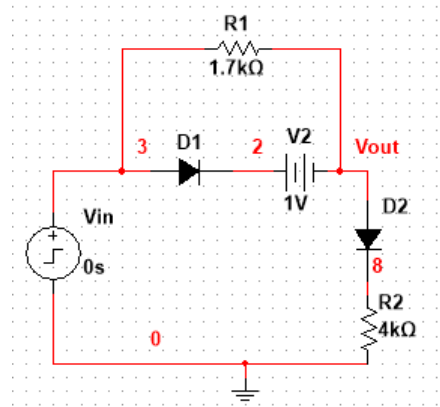


- 1 – Sketch out the transfer characteristic of this circuit V_{out} vs V_{in} for V_{in} ranging from 0V to 5V. Assume $V_{D_{on}} = 0.7V$. Be sure to identify notable voltages and slopes.

20pts

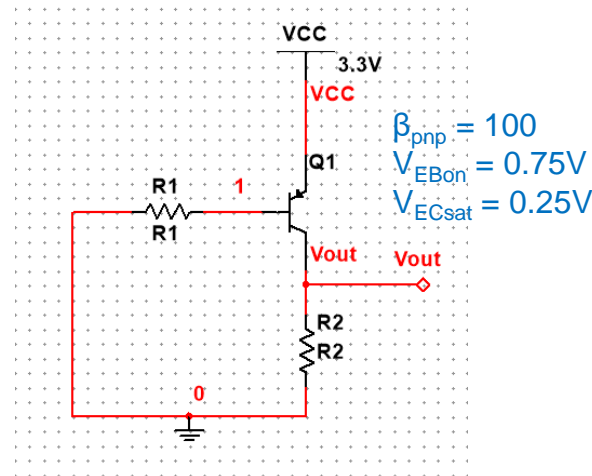

- 2 – Select values for R1 and R2 in the circuit below. The output voltage should be 1.6V with a < 10% error to loads greater than 15K Ω 20pts



- 3 – Design a first order active low pass filter with a cutoff frequency of 30KHz and $Z_{in} > 20K\Omega$, use industry standard common components (listed on the website) 30pts

4 – Provide the LSB size for each of the following:

30pts

10bit ADC with $V_{ref} = 2.5V$ _____

12bit DAC with $V_{dd} = 3.3V$ _____

Provide the expected output value (hex) for the 10bit ADC above with $V_{in} = 1.8V$

Provide the expected output value (V) for the 12bit DAC above with the input set to 0x7A3

Briefly describe what Quantization Error is: