


Memory Topology Physical

Last updated 2/4/24


Memory Topology - Physical

- Direct implementation of the Logical view

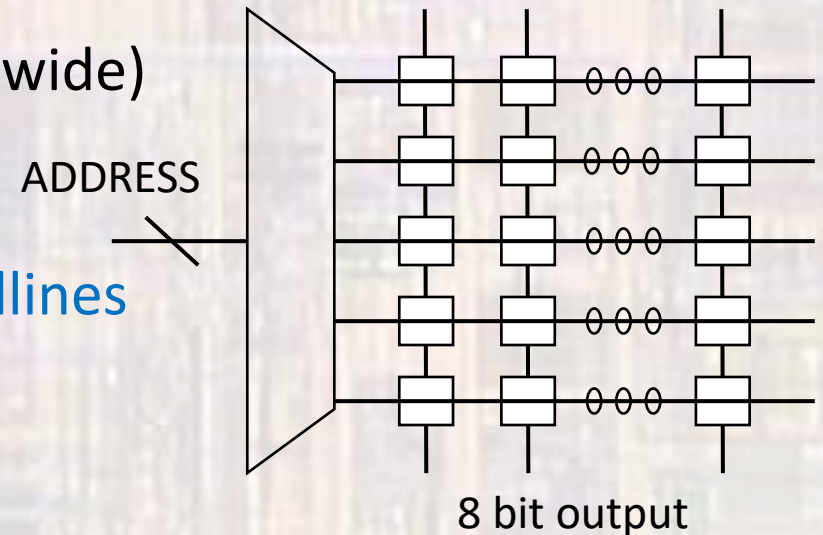- Array of single bit cells (8 bits wide)
- Row decoder chooses 1 row
- Rows are typically called **wordlines**
- Bit Cell Columns are typically called **bitlines**



 
- Non optimal
 - Physical implementation
 - Non-practical die dimensions
 - Speed
 - Long lines → slow speeds



Memory Topology - Physical

- Practical Physical Structure

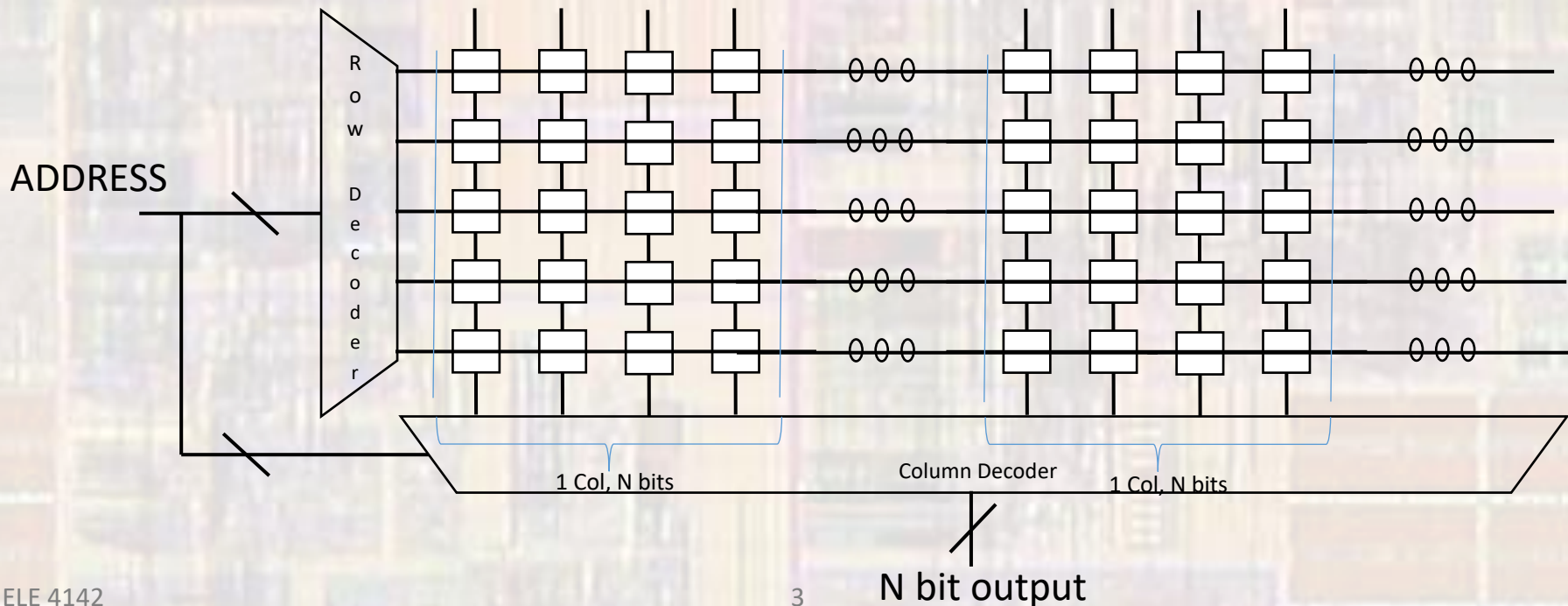- Array of single bit cells
 - Typically, square \leftrightarrow 1::2 ratio
 - Grouped as N bit **columns**
 - $N = 1, 4, 8, 16, 32, 64, 128, \dots$ bits/column
- Row decoder chooses 1 row
- Column decoder chooses 1 column




Memory Topology - Physical

- Practical Physical Structure

- 1Mb array, with square bit cells, in a x1 (col = 1bit) architecture

- 1K rows X 1K columns

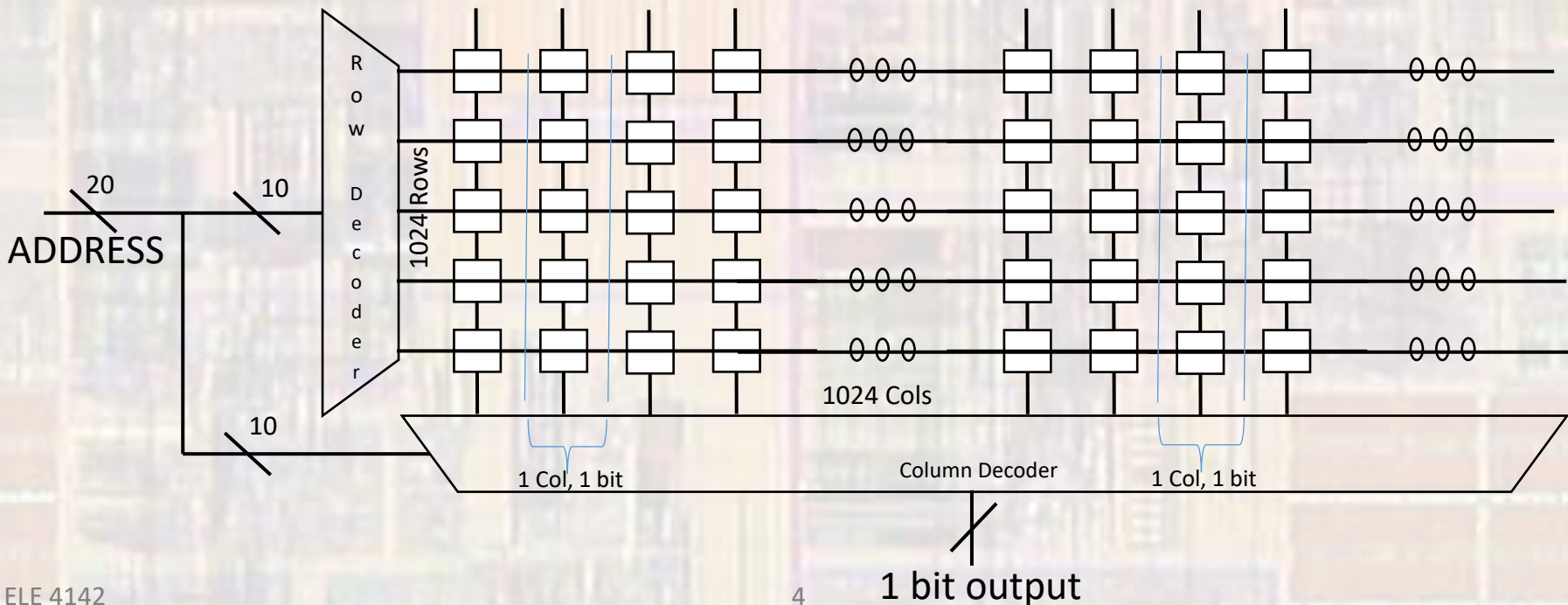
- 10 row address lines, 10 col address lines → 20 total address lines



Memory Topology - Physical

- Practical Physical Structure

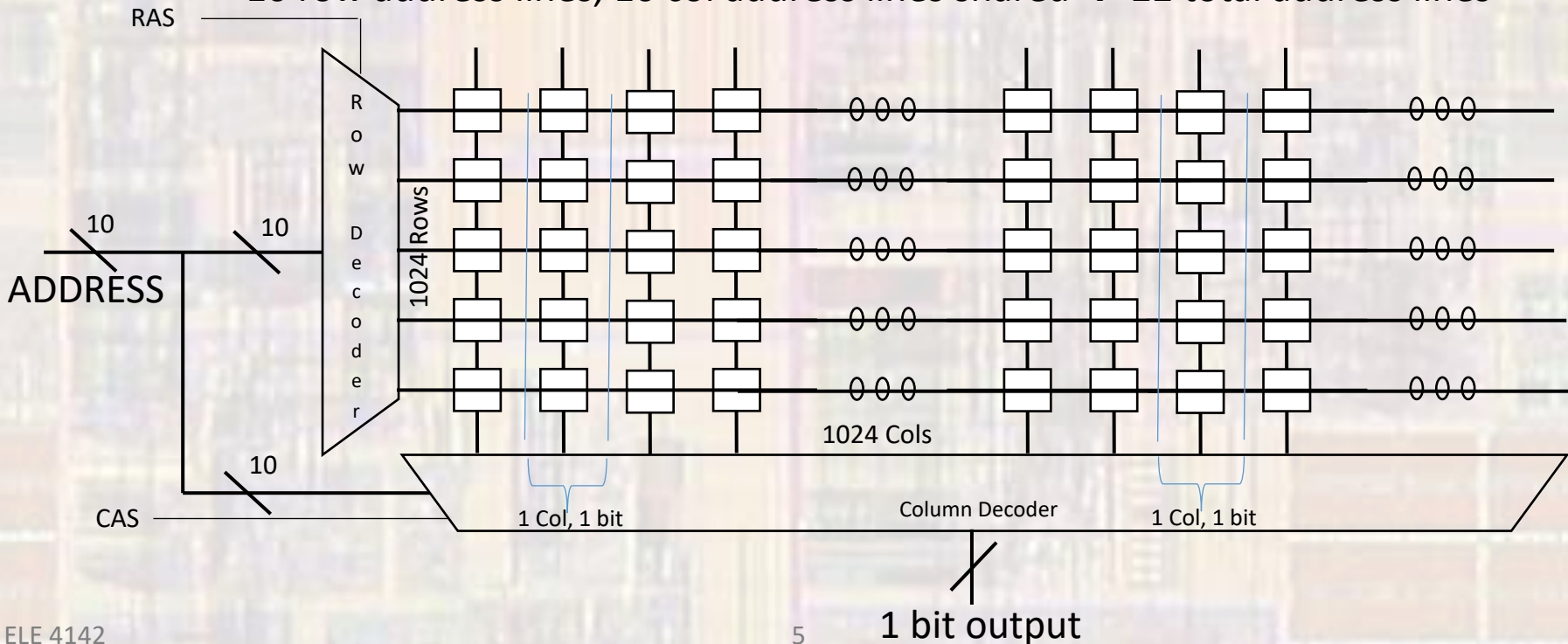- 1Mb array, with square bit cells, in a x1 (col = 1bit) architecture – **with shared address lines**
 - 1K rows X 1K columns
 - Add a Row Address Strobe (RAS) and Column Address Strobe (CAS)
 - Row decode is active when RAS high, Col decode is active when CAS high
 - 10 row address lines, 10 col address lines shared → 22 total address lines



Memory Topology - Physical

- Memory Descriptive Terminology
 - 16Mb in a x4
 - 16Mb total memory, each memory address provides 4 bits
 - 16Mb x 4
 - 64Mb total memory, each memory address provides 4 bits
 - Could be configured as 4 16MB memories, each providing 1b to the output

Memory Topology - Physical

- Memory Descriptive Terminology
 - Example – 16Mb in a x4 configuration
 - address sharing

16Mb total \rightarrow 16,777,216 bits
x4 means each column is 4 bits
or each address points to 4 bits

16Mb in a x4 configuration \rightarrow 4 bits / address \rightarrow 4,194,304 - individual addresses
 \rightarrow 22 total address bits


Assuming a square memory array and a square bit cell \rightarrow 4 times as many rows as columns
4 times as many rows as columns \rightarrow 2 more row address bits than column address bits

22 address bits \rightarrow 12 bits for row addresses and 10 bits for column addresses

IF sharing address bits \rightarrow 12 address bits + RAS + CAS = 14 total address signals

16 rows \rightarrow
4 bit address

4 cols \rightarrow 2 bit address

 

Memory Topology - Physical

- Memory Packaging
 - Single chip
 - DIP, SOP, BGA
 - SIMM
 - Single In-line Memory Module
 - 4Mb Module → 8, 256Kb x 1 chips
 - 32b processor would require 4 SIMMs
 - DIMM
 - Dual In-line Memory Module
 - 2 sided version of a SIMM, thicker but shorter
 - DDRx
 - Double Data rate (SDRAM)
 - DIMM with registration slots tied to DDRx type

