


OpAmp Circuits

Last updated 1/11/24


OpAmps

- Operational Amplifier (OpAmp)
 - High Gain difference amplifier

$$V_o = A_{od} (V_+ - V_-)$$

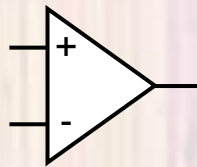

Implied power connections

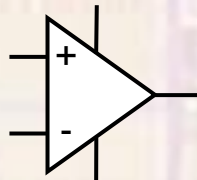





Explicit power connections

OpAmps

- Ideal OpAmp
 - High Gain difference amplifier

$$V_o = A_{od}(V_+ - V_-)$$

$$A_{od} = 100,000$$

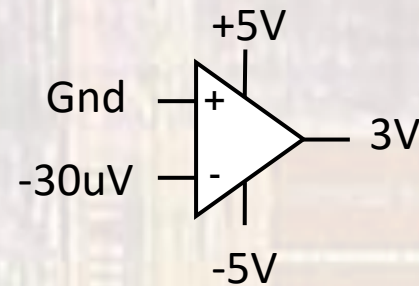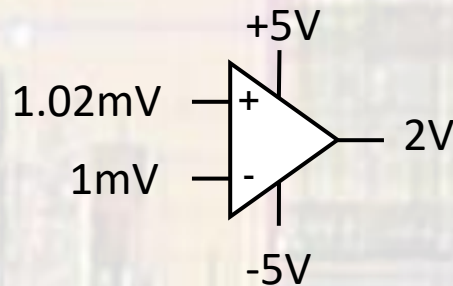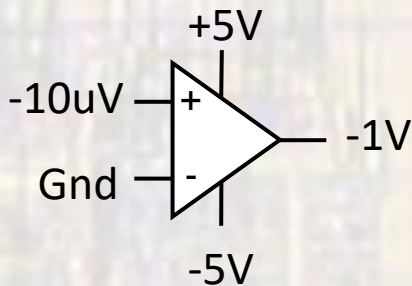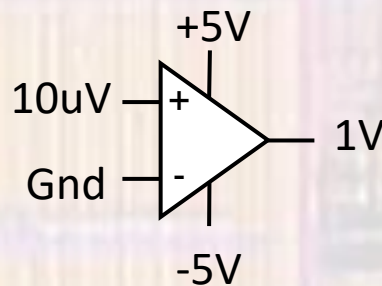



OpAmps

- OpAmp Limitations


- Output Swing

- Common opamps can only swing the output to about 1V from the positive or negative voltage rails
 - Rail-to-rail opamps can get to within 10s of mv of the rails

$$A_{od} = 100,000$$

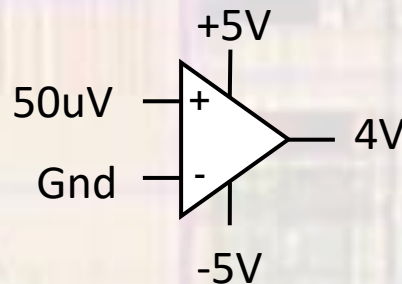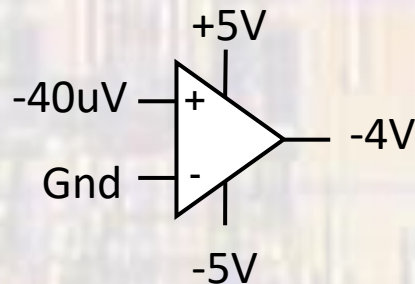

Output Saturated
(clipped, limited)

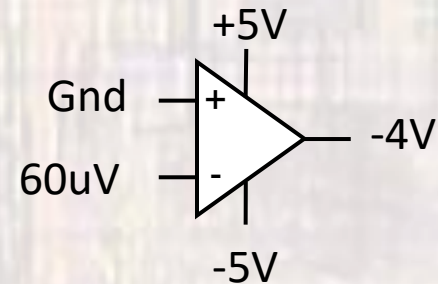

Output Saturated
(clipped, limited)



OpAmps

- OpAmp Limitations

- Slew Rate

- Limit on how fast the output can change
- Limits large signal rise and fall times at the output
 - Typically between 1V/us and 100V/us
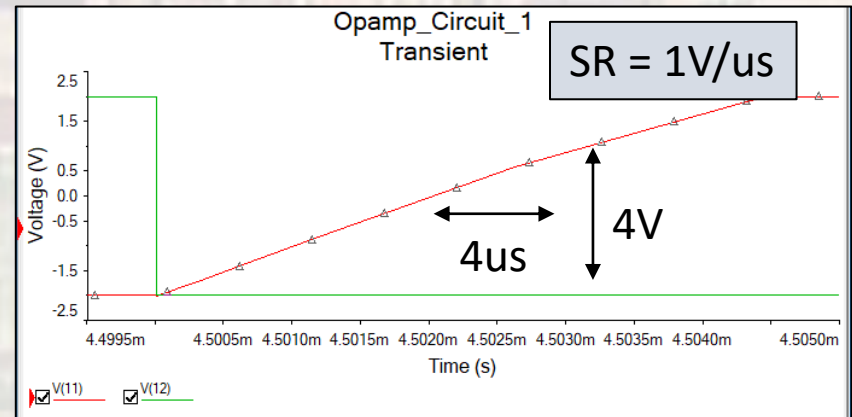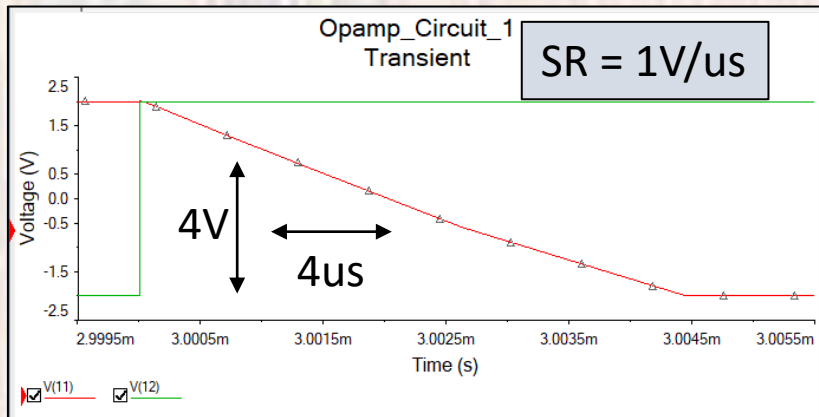
$$\left(\frac{dV_o}{dt}\right)_{max} = SR$$






OpAmps

- OpAmp Limitations

- Input Offset

- This represents a built-in error between the + and – inputs
 - Bipolar: < 20mV
 - CMOS: < 1mV
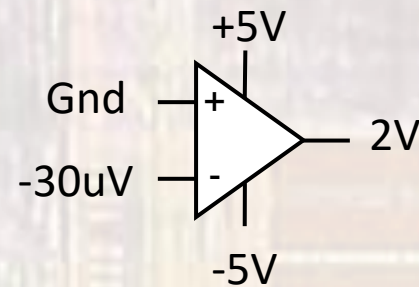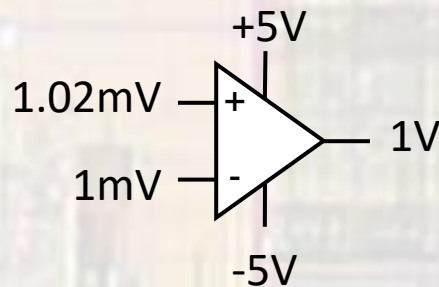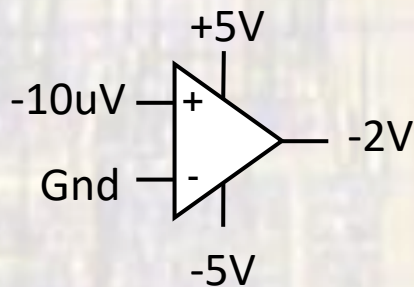
$$V_o = A_{od}(V_+ - V_- - V_{offset}) \quad A_{od} = 100,000$$
$$V_{os} = 10\mu\text{V}$$



OpAmps

- OpAmp Limitations
 - Input bias current / input bias current offset
 - The required input current to operate the opamp
 - The offset from + to – for the input bias currents
 - Bipolar inputs
 - Bias current, typically $< 1\mu\text{A}$
 - Offset, typically 20% - 50% of bias current
 - CMOS inputs, typically $< 1\text{nA}$

OpAmps

- OpAmp Limitations
 - Input Impedance
 - The impedance looking into the inputs
 - Bipolar input opamps typically between $1\text{M}\Omega$ and $10\text{M}\Omega$
 - CMOS input opamps typically $> 10\text{G}\Omega$
 - Output Impedance
 - The impedance looking into the output
 - Typically $< 50\Omega$

OpAmps

- OpAmp Limitations

- Common Mode Rejection Ratio (CMRR)

- This represents the opamps ability to reject signals that are present on both inputs (common)
- CMRR is the ratio of the common-mode gain to differential-mode gain


$$V_o = A_{od}(V_+ - V_-) + A_{CM} \frac{(V_+ + V_-)}{2}$$

$$CMRR = \frac{A_{od}}{A_{CM}}$$

$$CMRR_{dB} = 20 \log \frac{A_{od}}{A_{CM}}$$

$$A_{od} = 100,000$$

$$A_{CM} = 80\text{dB} \\ (10,000)$$

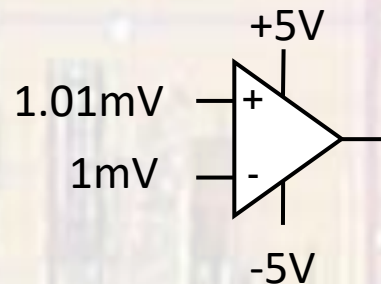

$$1V + \frac{100,000 (1.01mV + 1mV)}{10,000 \cdot 2}$$


$$1V + 10.05mV = 1.01V$$

OpAmps

- OpAmp Limitations


- Gain Bandwidth Product

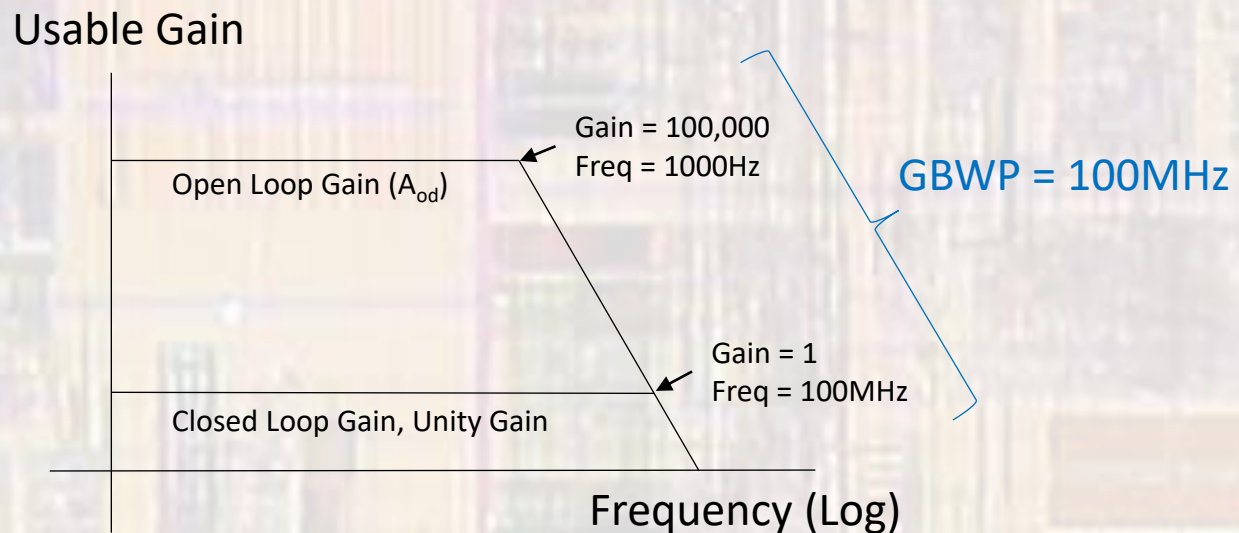- Product of the Gain at a specific frequency and the frequency
 - For most negative feedback configurations this is constant
 - Sometimes called the Unity Gain Bandwidth



OpAmps


- OpAmp Models

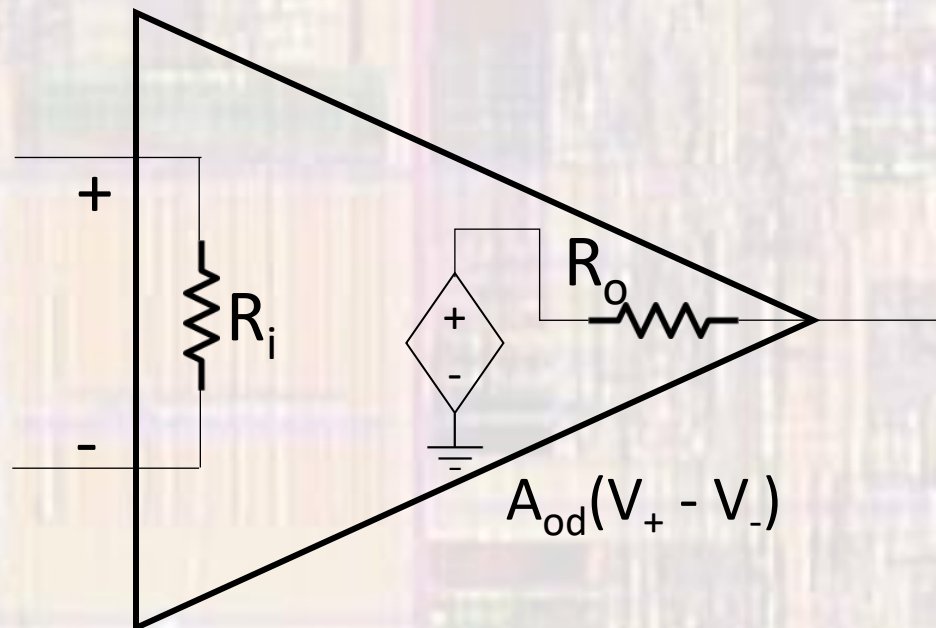

OpAmp Circuits

- Most opamps are operated in negative feedback configurations
 - Output feeds back to the - input

- Voltage Follower

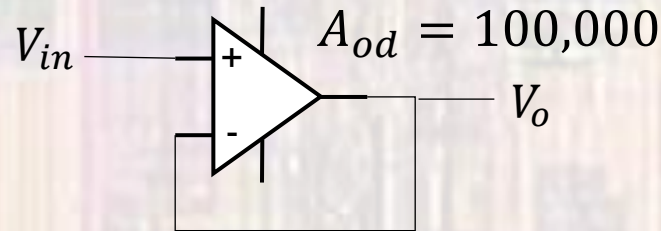

$$V_o = A_{od}(V_+ - V_-)$$

$$V_o = A_{od}(V_{in} - V_o)$$


$$V_o = \frac{A_{od}}{1 + A_{od}} V_{in} = V_{in} |_{A_{od} \gg 1}$$

$$A_v = \frac{V_o}{V_{in}} = \frac{A_{od}}{1 + A_{od}} = 1$$

OpAmp Circuits

- Fixed Gain Inverting Amplifier

- Gnd ref

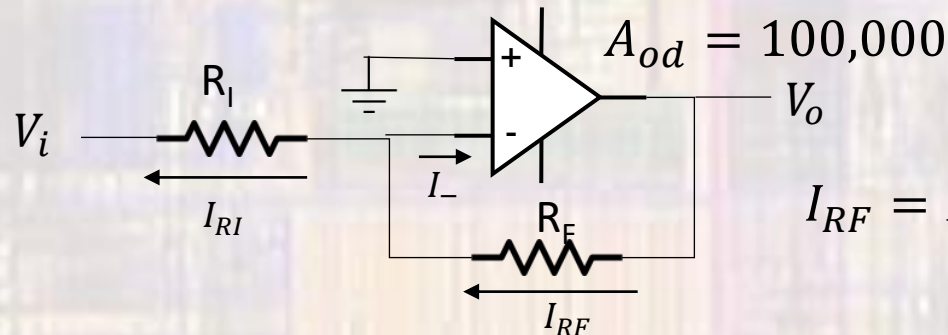

$$I_{RF} = I_{RI} + I_- = I_{RI}$$

$$I_{RF} = \frac{V_o - V_-}{R_F} = \frac{V_o - \left(V_+ - \frac{V_o}{A_{od}} \right)}{R_F}$$

$$I_{RI} = -\frac{V_i - V_-}{R_I} = -\frac{V_i - \left(V_+ - \frac{V_o}{A_{od}} \right)}{R_I}$$


$$\frac{V_o - \left(V_+ - \frac{V_o}{A_{od}} \right)}{R_F} = -\frac{V_i - \left(V_+ - \frac{V_o}{A_{od}} \right)}{R_I}$$

$$V_o = -\frac{R_F}{R_I} V_i$$

$$A_v = -\frac{R_F}{R_I}$$

OpAmp Circuits

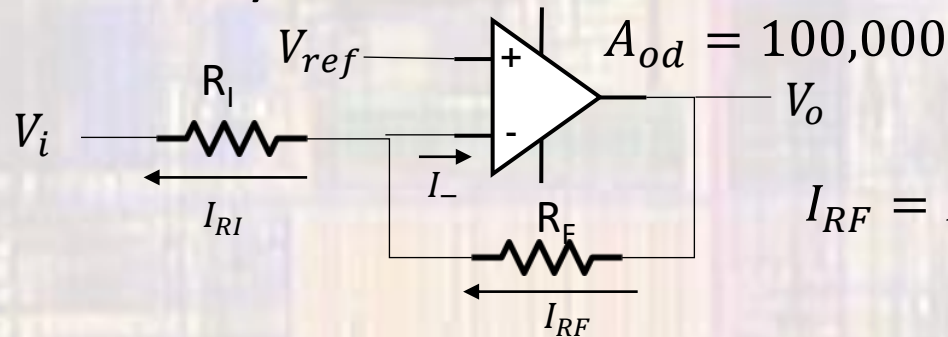- Fixed Gain Inverting Amplifier
 - Arbitrary ref



$$I_{RF} = I_{RI} + I_- = I_{RI}$$

$$I_{RF} = \frac{V_o - V_-}{R_F} = \frac{V_o - \left(V_{ref} - \frac{V_o}{A_{od}} \right)}{R_F}$$


$$I_{RI} = -\frac{V_i - V_-}{R_I} = -\frac{V_i - \left(V_{ref} - \frac{V_o}{A_{od}} \right)}{R_I}$$

$$\frac{V_o - \left(V_{ref} - \frac{V_o}{A_{od}} \right)}{R_F} = -\frac{V_i - \left(V_{ref} - \frac{V_o}{A_{od}} \right)}{R_I}$$

$$V_o = -\frac{R_F}{R_I} V_i + \left(1 + \frac{R_F}{R_I} \right) V_{ref}$$

OpAmp Circuits

- Inverting Amplifier
 - Second look

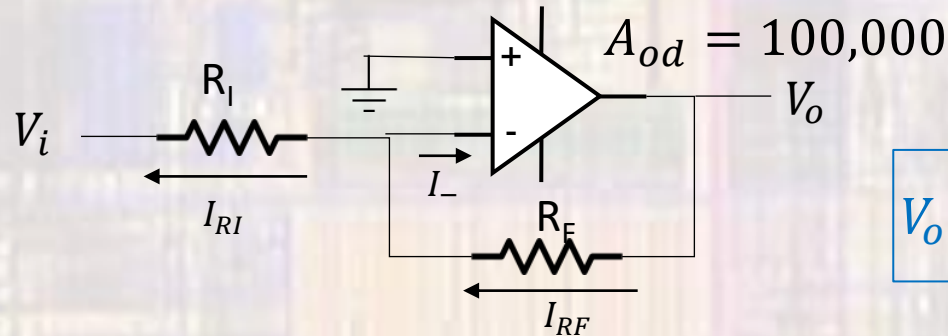

$$V_o = -\frac{R_F}{R_I} V_i$$

$$V_- = V_i + V_{R_I} = V_i + (V_o - V_i) \frac{R_I}{R_I + R_F}$$

$$V_- = \frac{V_i R_I + V_i R_F + V_o R_I - V_i R_I}{R_I + R_F} = \frac{V_i R_F + V_o R_I}{R_I + R_F} = \frac{V_i R_F - \frac{R_F}{R_I} V_i R_I}{R_I + R_F}$$




$$V_- = \frac{V_i R_F - R_F V_i}{R_I + R_F} = 0$$

V_- is called a virtual ground

OpAmp Circuits


- Inverting Amplifier

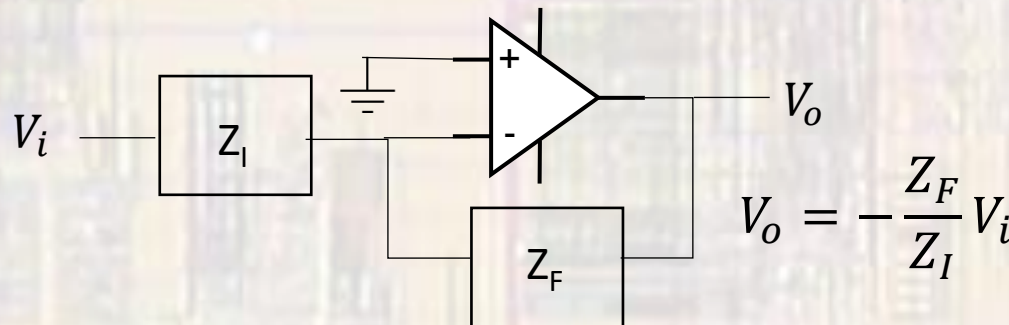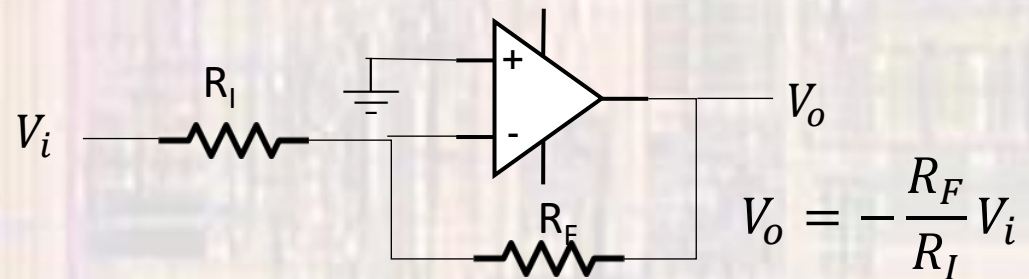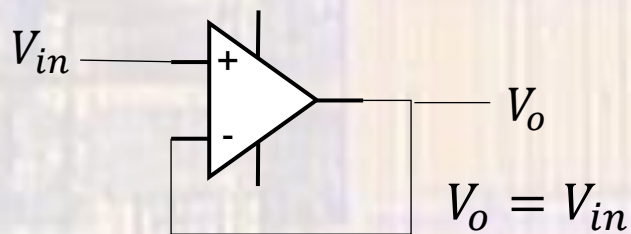An opamp in a negative feedback configuration will drive its output to force the V_+ and V_- inputs to be equal



OpAmp Circuits


- Fixed Gain Inverting Amplifier

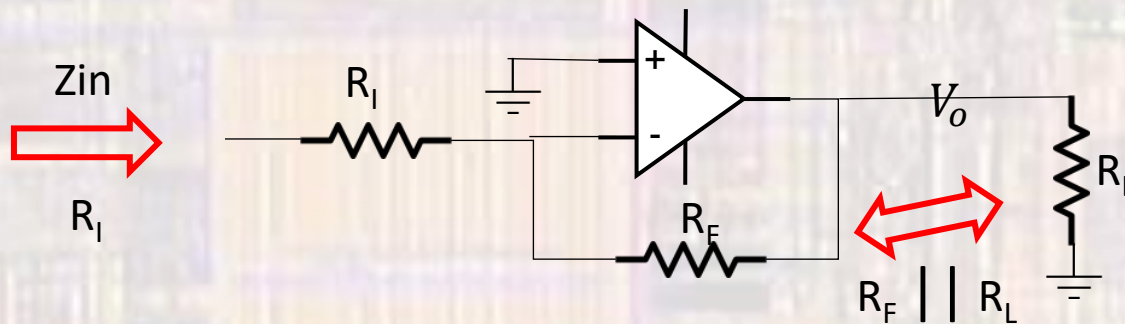

Input impedance concerns
Input current and input offset current concerns
Output impedance concerns

OpAmp Circuits

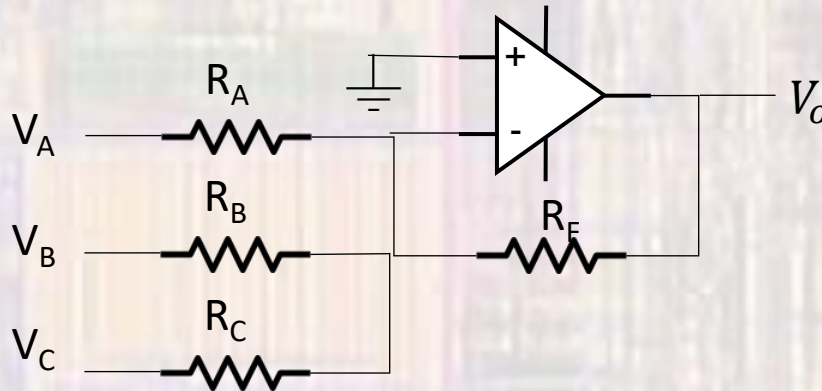
- Fixed Gain Inverting Summing Amplifier
 - By superposition



$$V_O = -\frac{R_F}{R_A} V_A - \frac{R_F}{R_B} V_B - \frac{R_F}{R_C} V_C$$

OpAmp Circuits

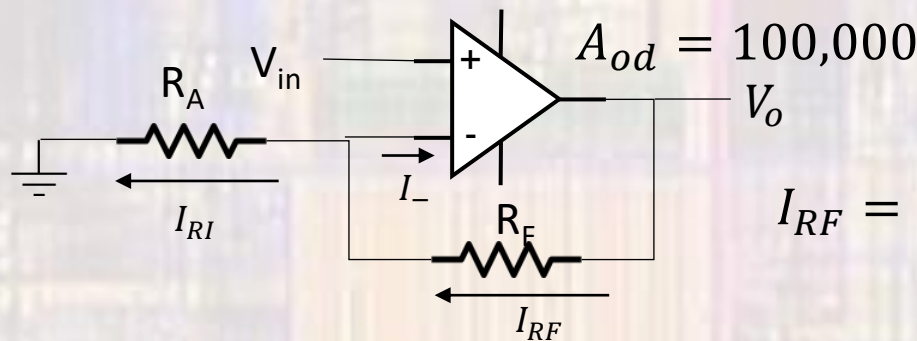- Fixed Gain Non-Inverting Summing Amplifier
 - Full Analysis



$$I_{RF} = I_{RA} + I_- = I_{RA}$$

$$I_{RF} = \frac{V_o - V_-}{R_F} = \frac{V_o - \left(V_{in} - \frac{V_o}{A_{od}} \right)}{R_F}$$

$$I_{RA} = \frac{V_- - 0}{R_A} = \frac{V_{in} - \frac{V_o}{A_{od}}}{R_A}$$


$$\frac{V_o - V_{in} + \frac{V_o}{A_{od}}}{R_F} = \frac{V_{in} - \frac{V_o}{A_{od}}}{R_A}$$

$$V_o = \left(1 + \frac{R_F}{R_A} \right) V_{in}$$

$$A_v = 1 + \frac{R_F}{R_A}$$

OpAmp Circuits

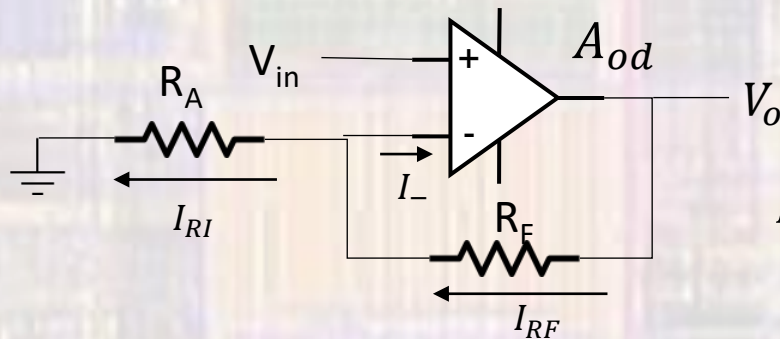- Fixed Gain Non-Inverting Summing Amplifier
 - Simplified analysis
 - Output moves to make the + and – inputs equal



$$I_{RF} = I_{RA} + I_- = I_{RA}$$

$$I_{RF} = \frac{V_O - V_-}{R_F} = \frac{V_O - V_{in}}{R_F}$$

$$I_{RA} = \frac{V_- - 0}{R_A} = \frac{V_{in}}{R_A}$$


$$\frac{V_O - V_{in}}{R_F} = \frac{V_{in}}{R_A}$$

$$V_O = \left(1 + \frac{R_F}{R_A}\right) V_{in}$$

$$A_v = 1 + \frac{R_F}{R_A}$$

OpAmp Circuits

- Difference Amplifier

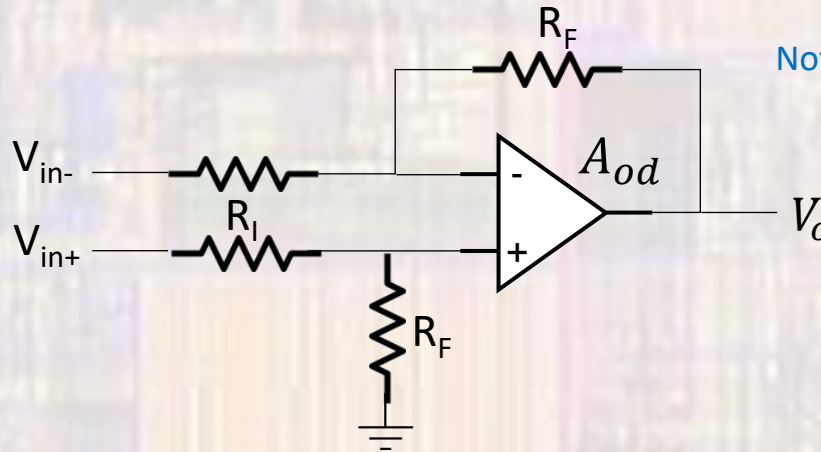


Note: no power pins
Amplifier flipped upside down

$$V_+ = V_{in+} \frac{R_F}{R_I + R_F} = V_- \quad \frac{V_{in-} - V_-}{R_I} = - \frac{V_o - V_-}{R_F}$$

$$V_o = \frac{R_F}{R_I} (V_{in+} - V_{in-})$$

OpAmp Circuits

- Current to Voltage Converter

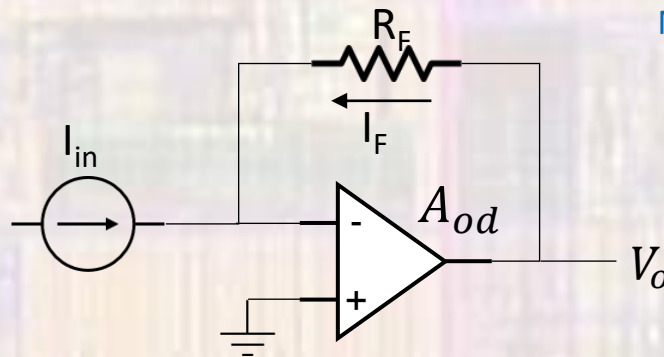


Note: no power pins
Amplifier flipped upside down

$$I_F = \frac{V_o - \overset{0}{V_-}}{R_F} = -I_{in}$$

$$V_o = -I_{in}R_F$$

OpAmp Circuits

- Voltage to Current Converter

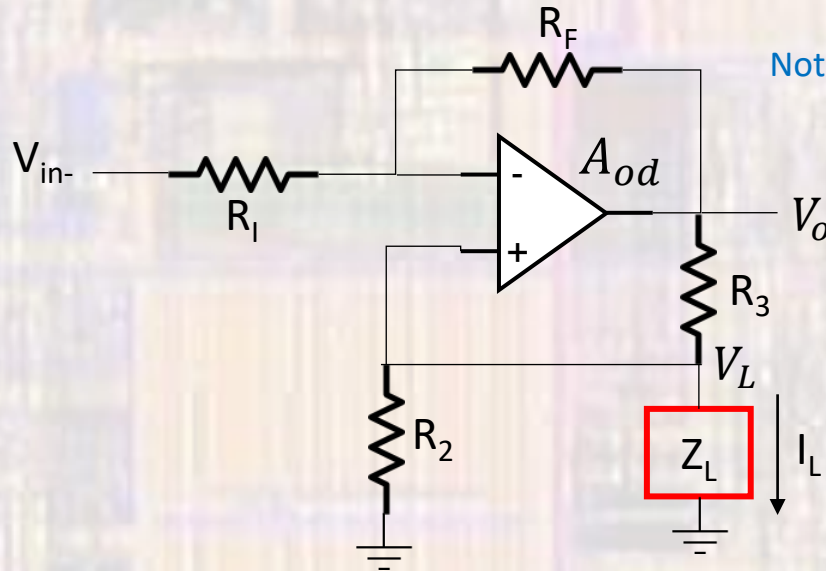


Note: no power pins
Amplifier flipped upside down

$$I_L = \frac{-V_{in}}{R_2} \left| \frac{R_F}{R_2 R_3} = \frac{1}{R_2} \right.$$

OpAmp Circuits

- Integrator

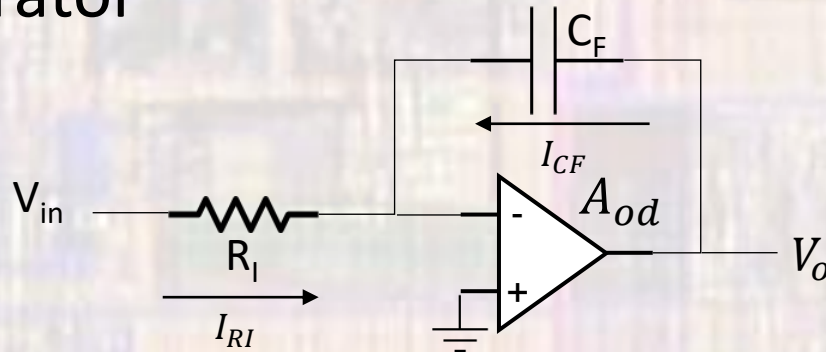


$$I_{CF} = C_F \frac{dv_o}{dt} = -\frac{V_{in}}{R_I}$$

$$dv_o = -\frac{V_{in}}{C_F R_I} dt$$

$$V_o = V_{CF0} - \frac{1}{C_F R_I} \int_0^t V_{in}(t') dt'$$

OpAmp Circuits

- Differentiator

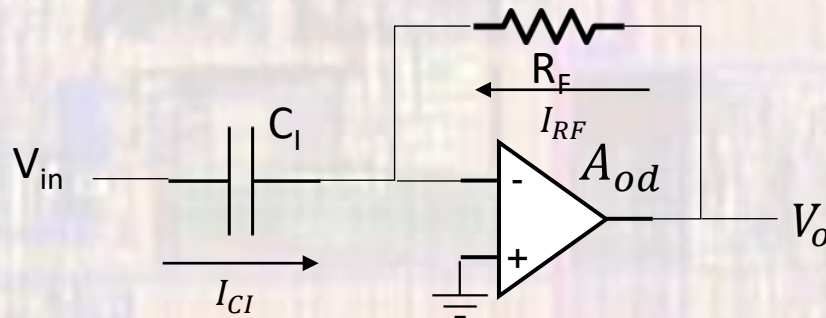


$$I_{C_I} = C_I \frac{dv_{in}}{dt} = -\frac{V_o}{R_F}$$

$$V_o = -R_F C_I \frac{dv_{in}}{dt}$$


OpAmp Circuit

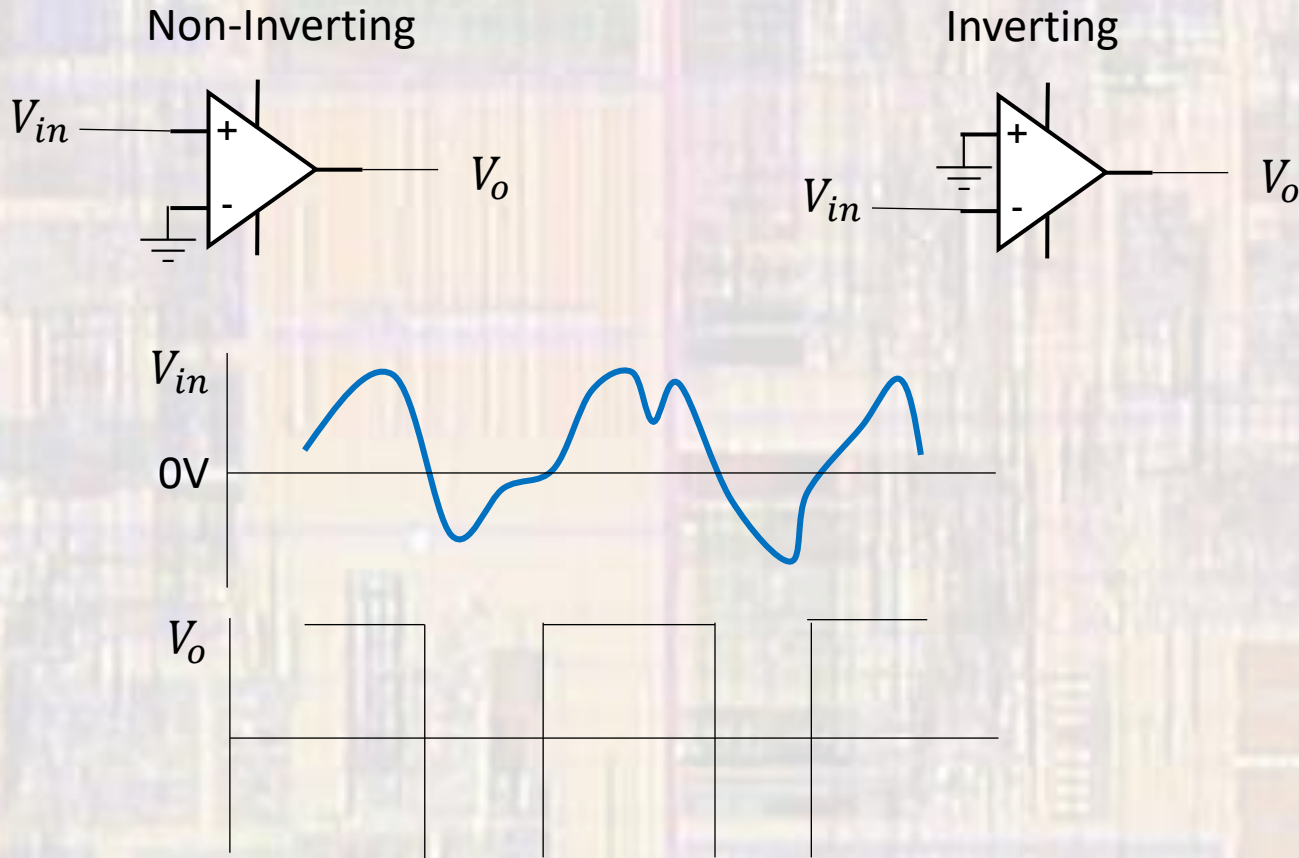- Zero Crossing Detector
 - Open Loop opamp



OpAmp Circuit

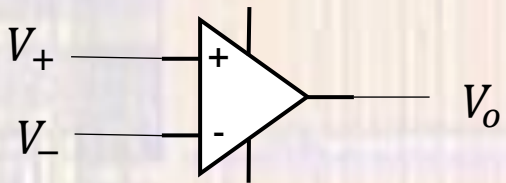
- Comparator
 - Special opamp with non-saturating outputs
 - Reduced delay in switching rail-to-rail



$$V_o = vdd \text{ or } vss$$


OpAmp Circuit

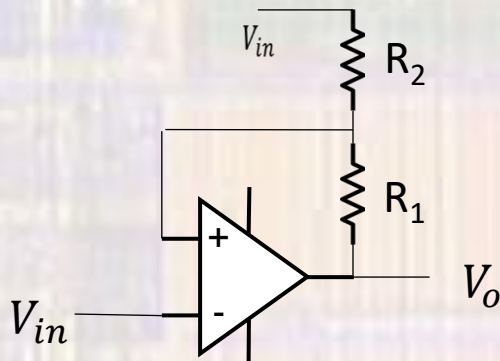- Schmitt Trigger
 - Positive feedback
 - Non-overlapping switching points



$$\text{when } V_o = v_{dd}, \text{ then } v_+ = v_{dd} \frac{R_2}{R_1 + R_2}$$
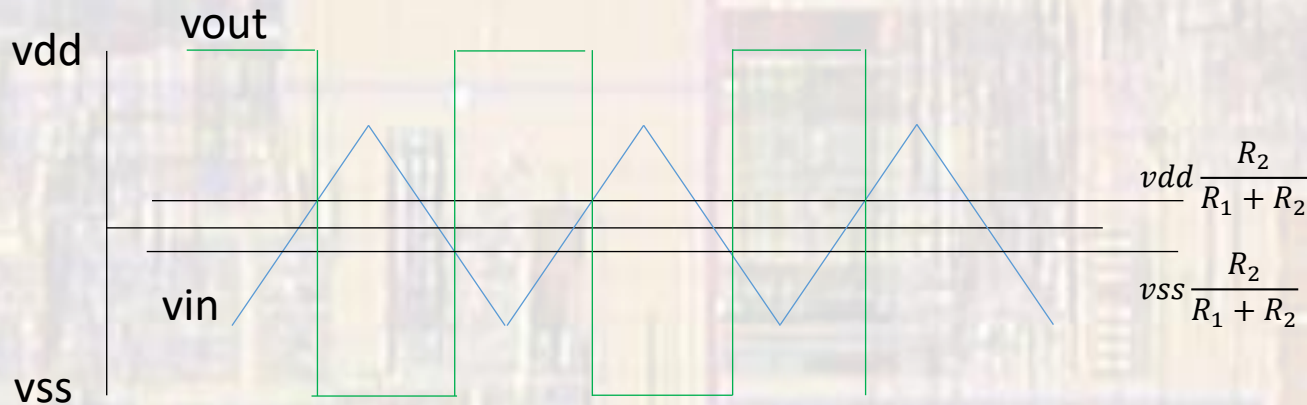
$$\text{when } V_o = v_{ss}, \text{ then } v_+ = v_{ss} \frac{R_2}{R_1 + R_2}$$



OpAmp Circuit



- Voltage Controlled Oscillator (VCO)

- Integrator

- Opamp wants $v_{+input} = v_{-input}$

- When the MOSFET is off

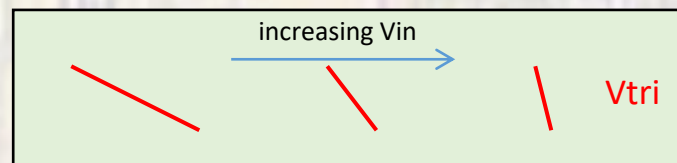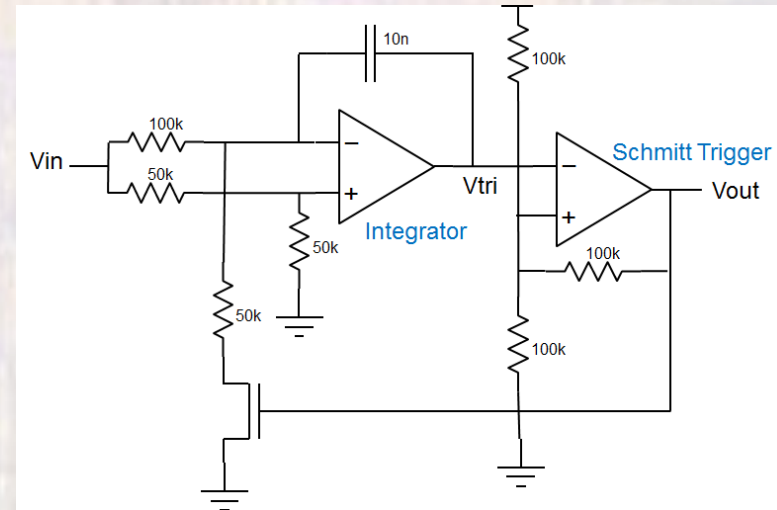- + input is $V_{in}/2$ (minus input wants to be $V_{in}/2$)
- current through 100K resistor must go through C
- current through C $I_c = -Cdv/dt$
- $-dv/dt$ is proportional to $V_{in} \rightarrow$ the opamp slews down




OpAmp Circuit

- Voltage Controlled Oscillator (VCO)

- Integrator

- Opamp wants $v_{+input} = v_{-input}$

- When the MOSFET is on

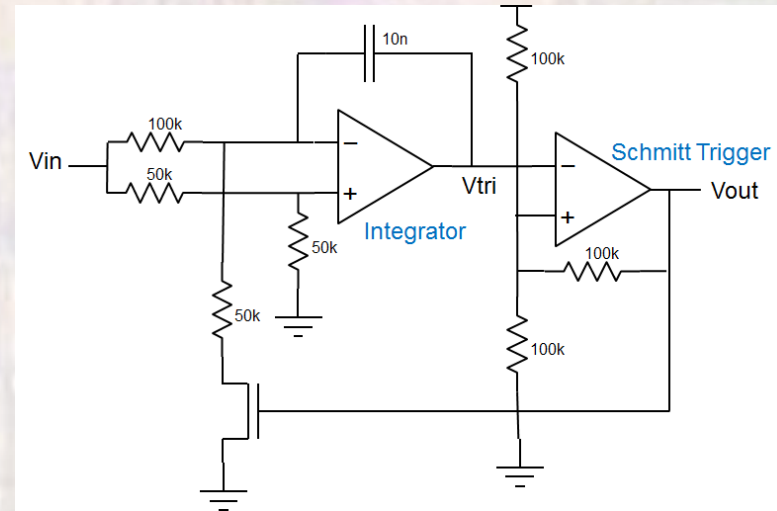


- + input is $V_{in}/2$ (minus input wants to be $V_{in}/2$)

- current through the 100K resistor is $\frac{1}{2}$ the current through 50K and MOSFET

- the other half the current through the MOSFET must come from the C

- current through C $I_c = Cdv/dt$

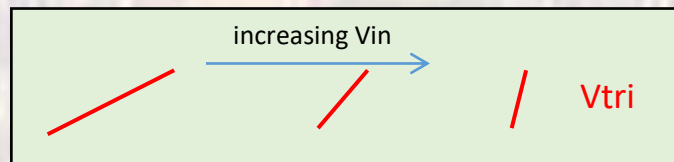- dv/dt is proportional to $V_{in} \rightarrow$ the opamp slews up



OpAmp Circuit

- Voltage Controlled Oscillator (VCO)




- Schmitt Trigger

- When V_{out} is high

- Mosfet is on $\rightarrow V_{tri}$ is slewing up
- + input is $V_{dd} * 2/3$
- When V_{tri} goes above $V_{dd} * 2/3$ the opamp switches to $V_{out} = 0$
- mosfet turns off $\rightarrow V_{tri}$ slews down

- When V_{out} is low

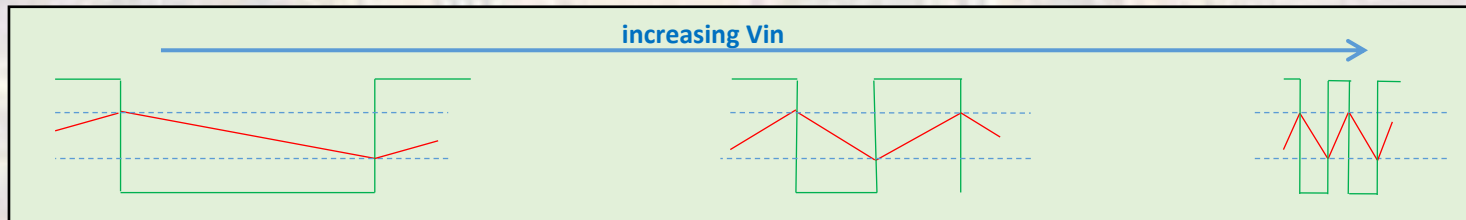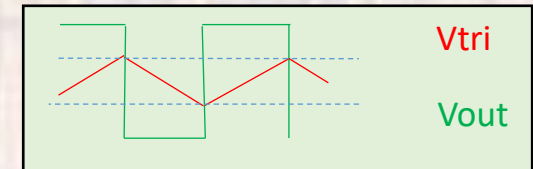
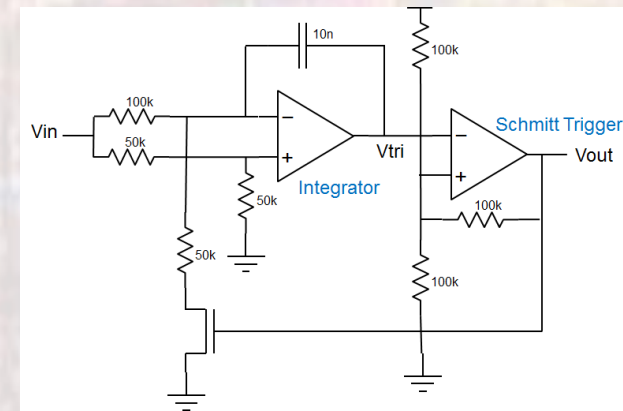
- Mosfet is off $\rightarrow V_{tri}$ is slewing down
- + input is $V_{dd} * 1/3$
- When V_{tri} goes below $V_{dd} * 1/3$ the opamp switches to $V_{out} = \text{high}$
- mosfet turns on $\rightarrow V_{tri}$ slews up



VCO



OpAmp Circuit

- Voltage Controlled Oscillator (VCO)

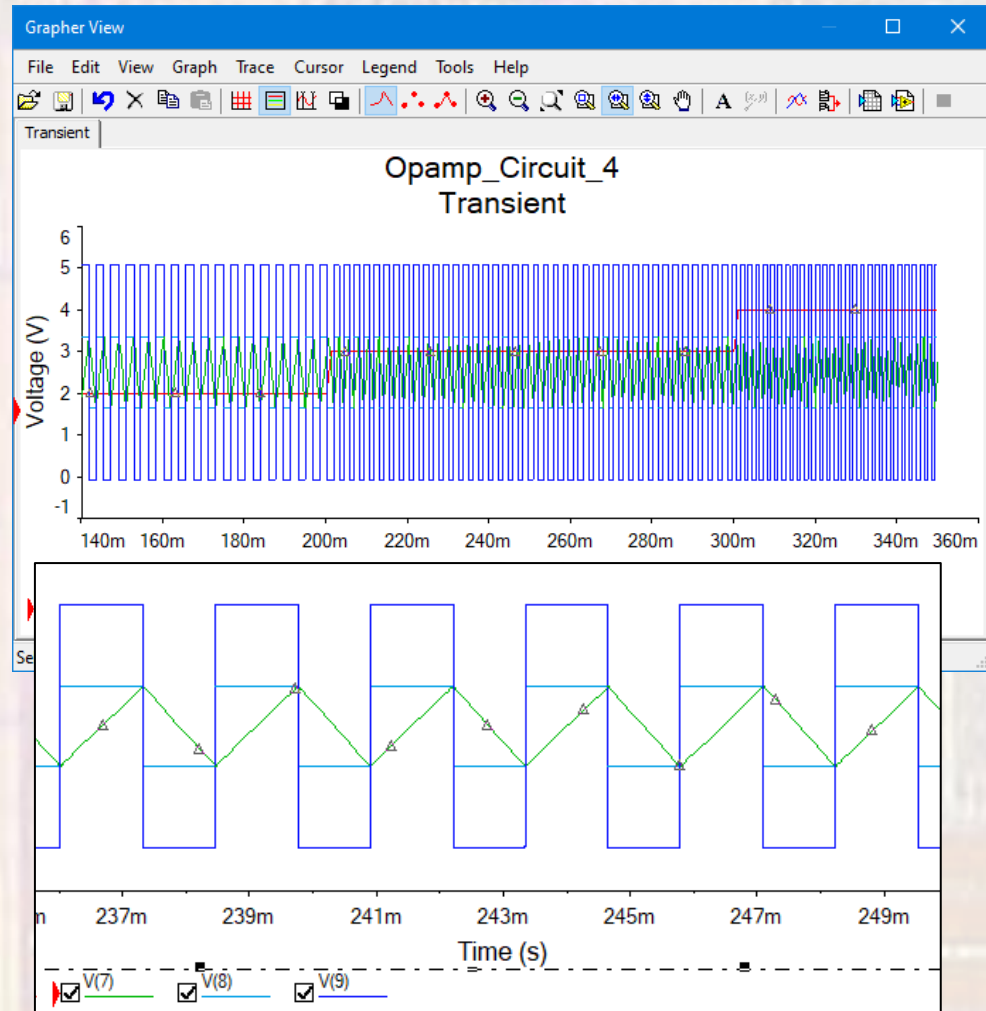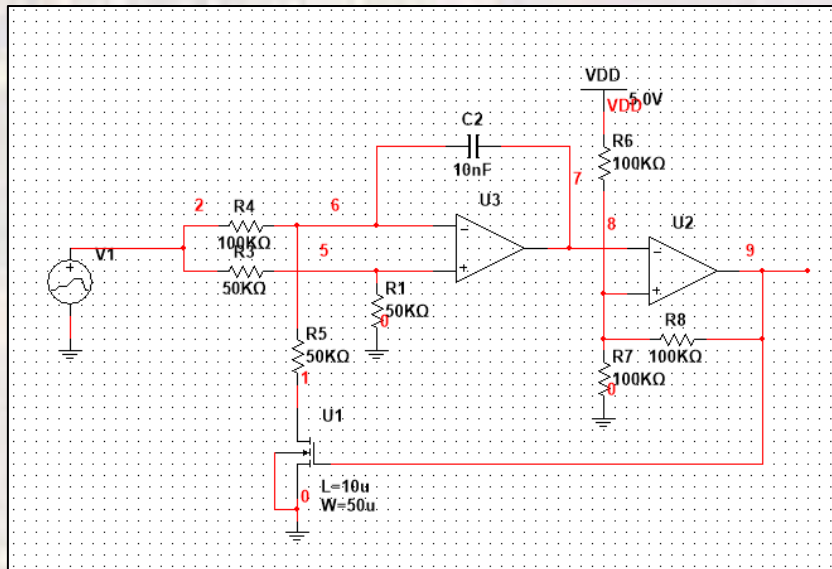



OpAmp Circuit

- Peak Detector

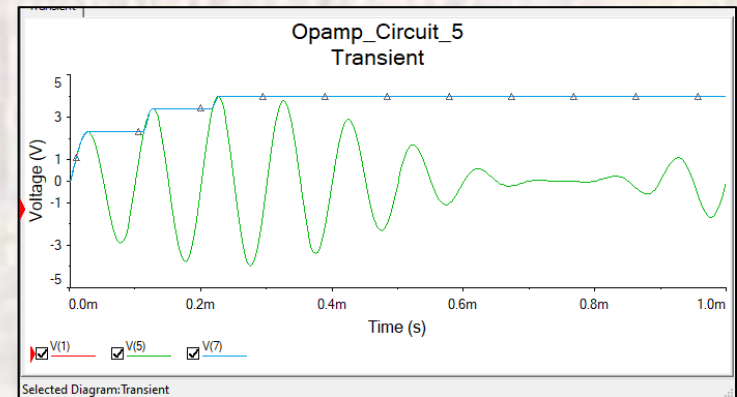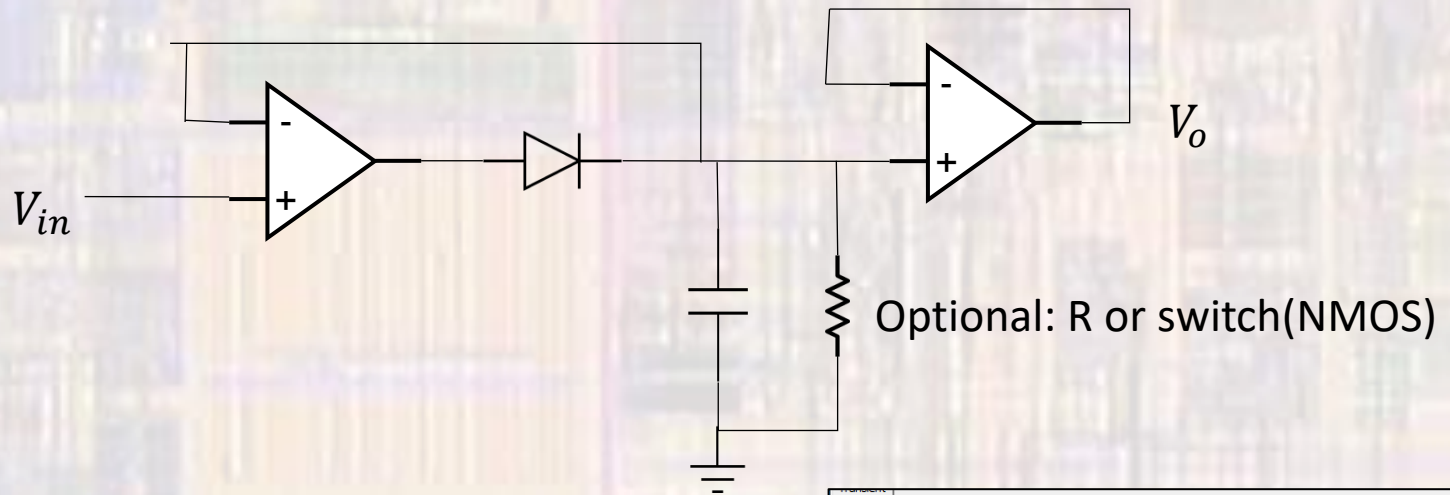


OpAmp Circuit

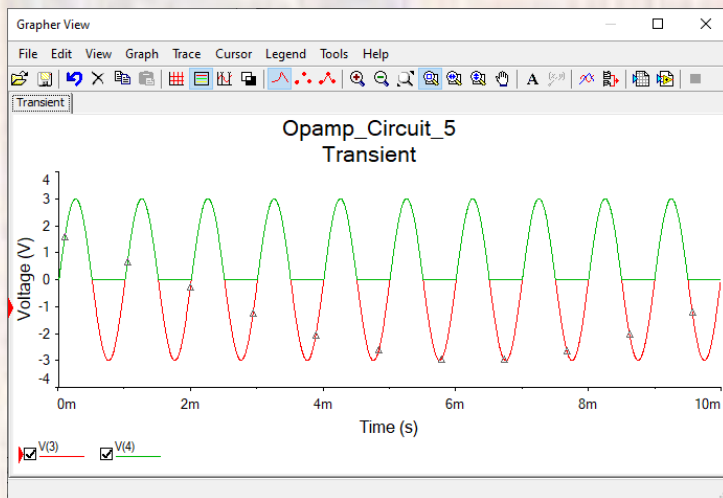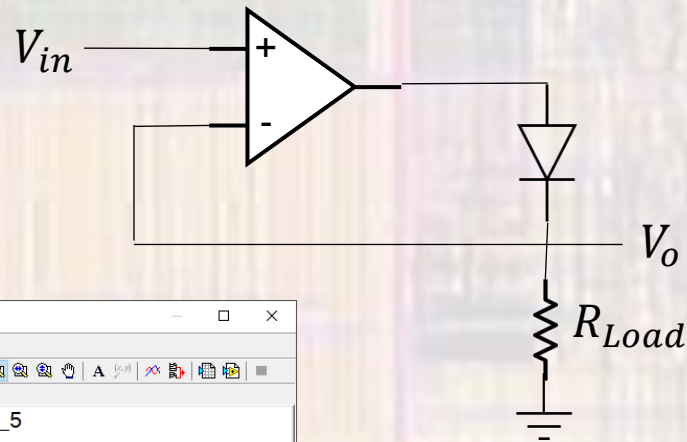- Half-Wave Precision Rectifier
 - Removes the Diode voltage drop from the output




OpAmp Circuit

- Log Amplifier

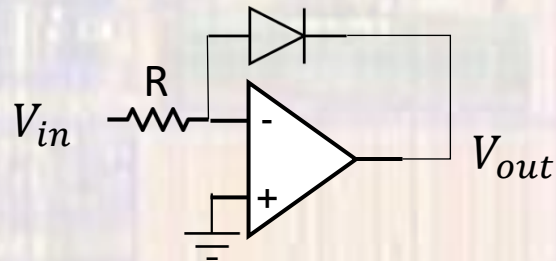


$$V_{in}/R = I_D = I_S e^{\frac{V_D}{nV_T}} = I_S e^{\frac{-V_{out}}{nV_T}}$$
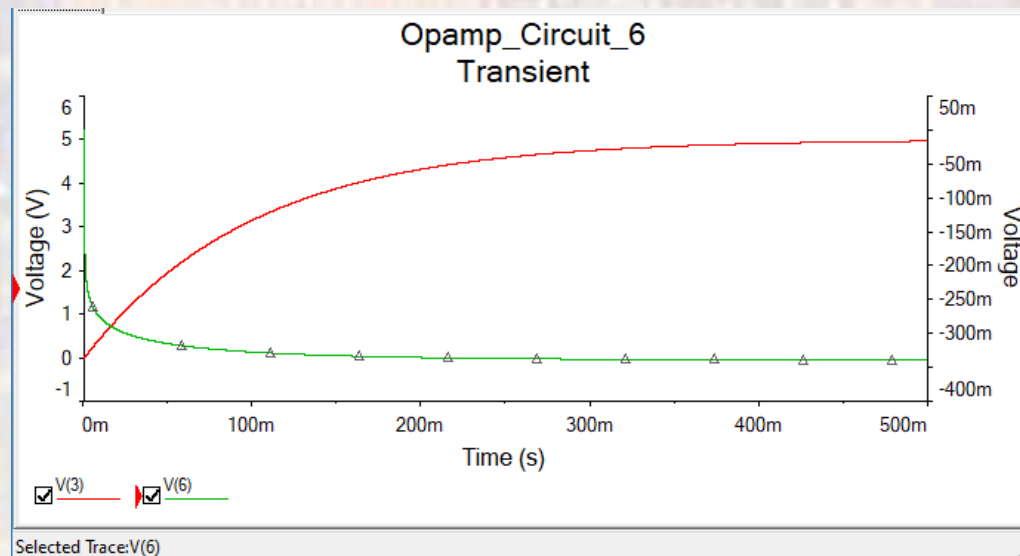
$$V_{out} = -nV_T \ln\left(\frac{V_{in}}{I_S R}\right)$$




OpAmp Circuit

- Exponential Amplifier

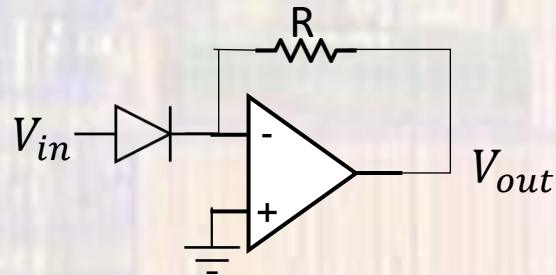


$$V_{out}/R = I_D = I_S e^{\frac{V_D}{nV_T}} = I_S e^{\frac{V_{in}}{nV_T}}$$
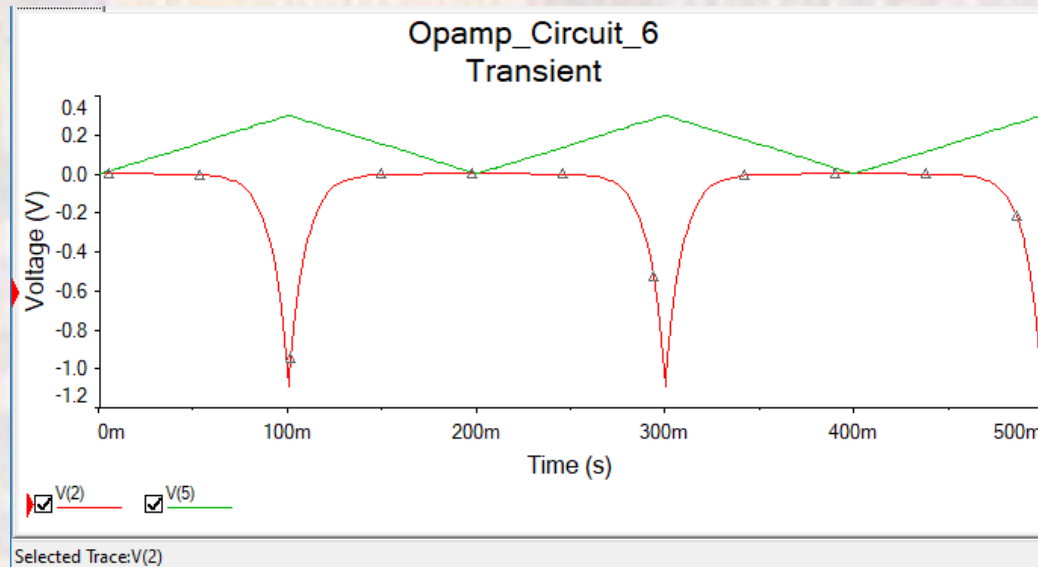
$$V_{out} = -RI_S e^{\frac{V_{in}}{nV_T}}$$




OpAmp Circuit

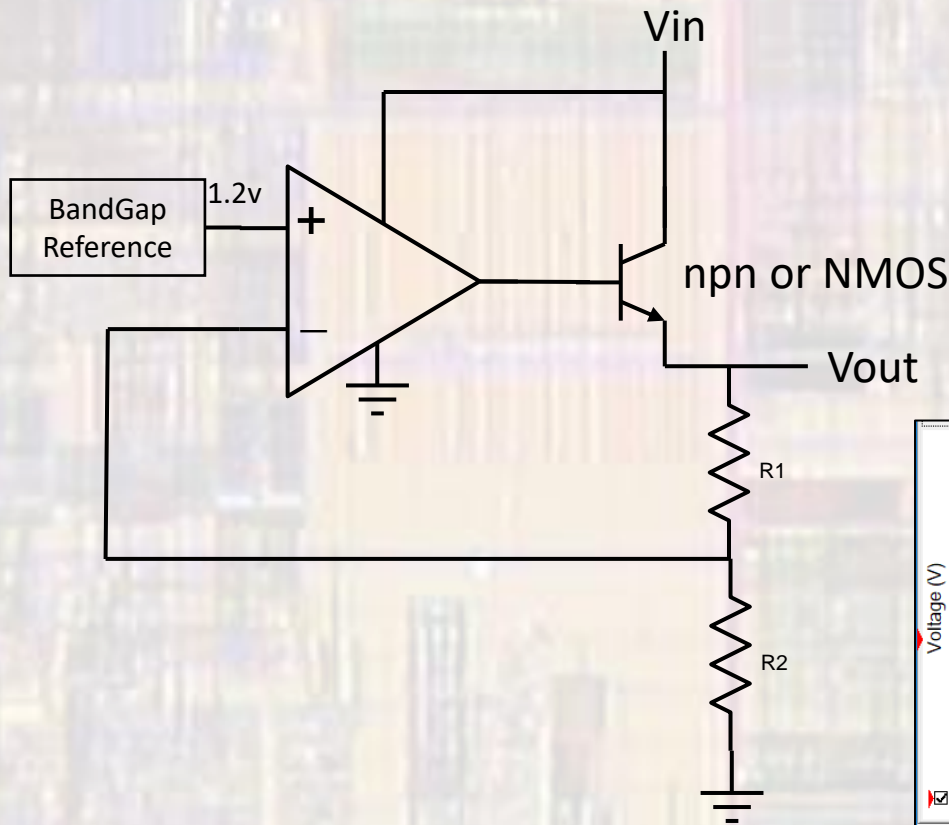- Regulated Supply
 - Super Simple Regulator





$$\frac{R2}{R1 + R2} V_{out} = V_{bg}$$

$$V_{out} = V_{bg} \frac{R1 + R2}{R2}$$

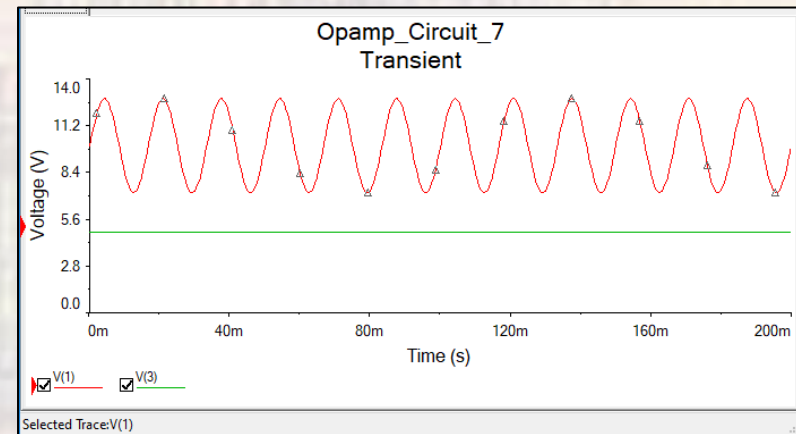

OpAmp Circuit

- Instrumentation Amplifier

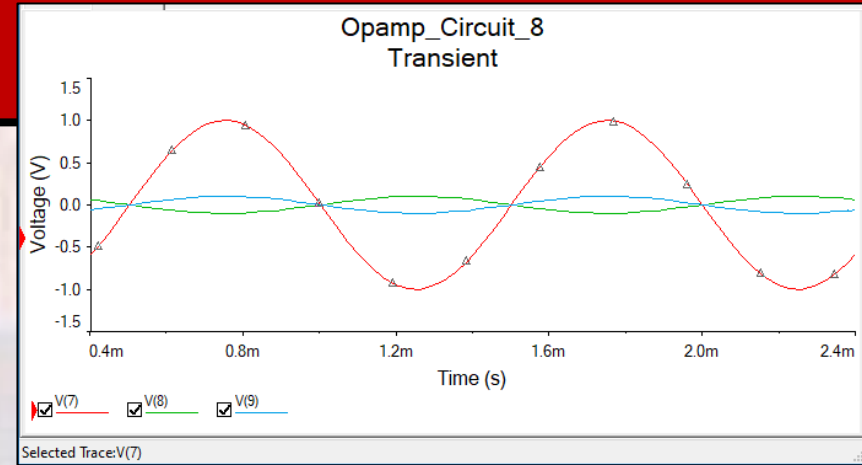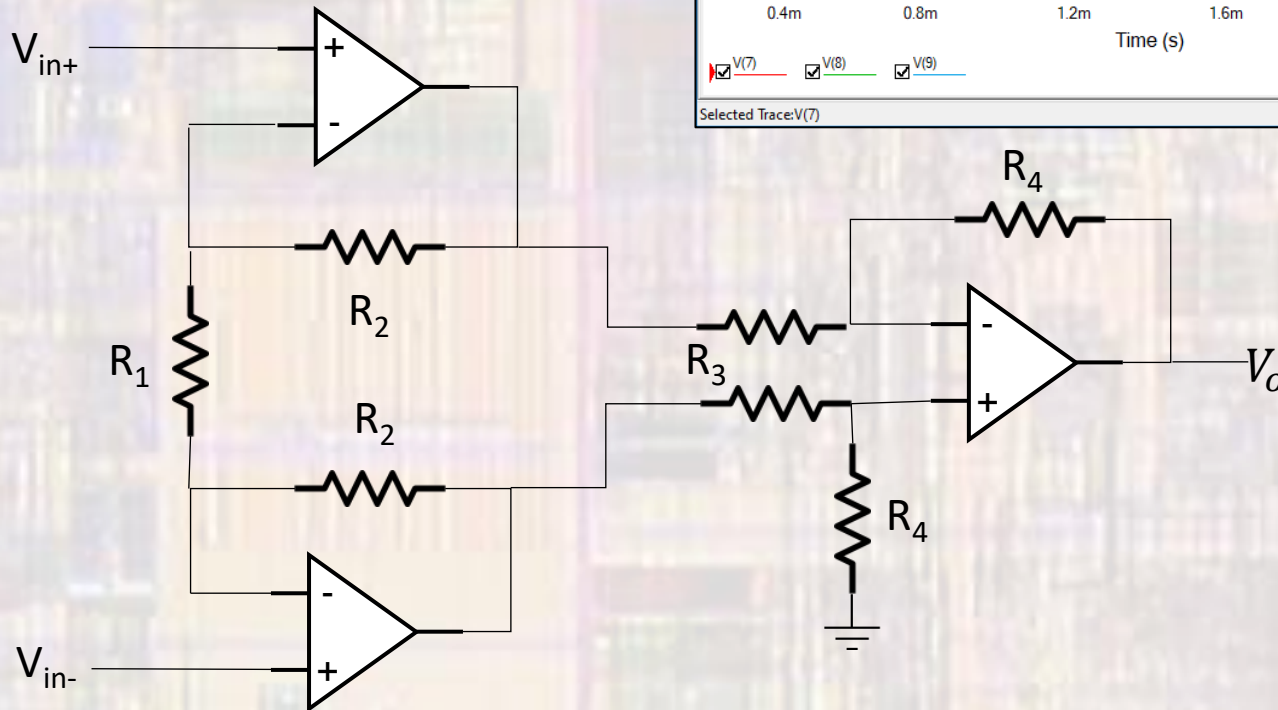

$$V_o = \frac{R_4}{R_3} \left(1 + \frac{2R_2}{R_1} \right) (V_{in+} - V_{in-})$$