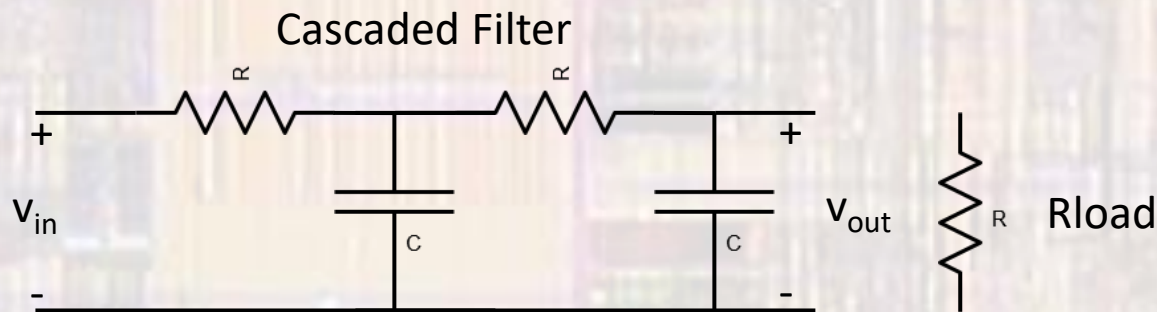


# RC Active Filters

Last updated 1/11/24

# RC Active Filters

- Passive filter concerns
  - Each stage loads the previous stage
  - Best case gain is 1 (0dB)
  - Any non-infinite output load will change the filter output




# RC Active Filters

- Why RC
  - It is much easier and cheaper to build integrated circuit capacitors and resistors than inductors
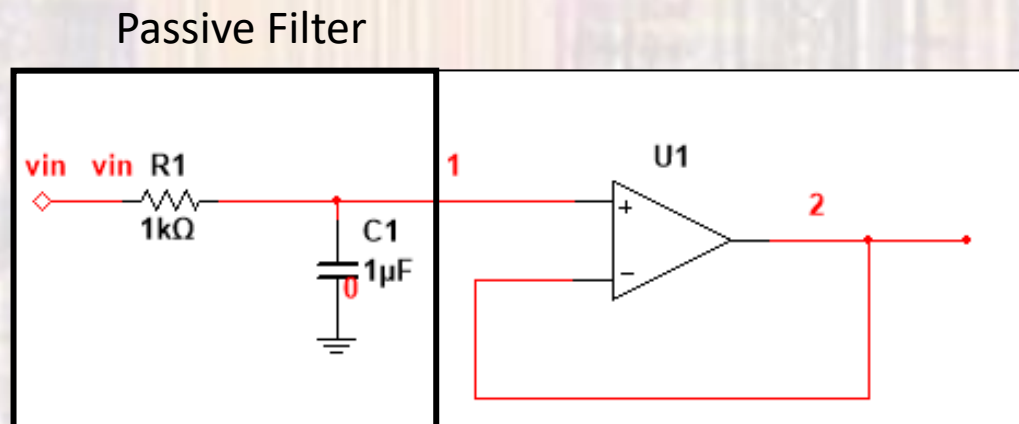
# RC Active Filters

- Just buffer the passive filter – Low Pass
  - Non-inverting
  - Load insensitive
  - Can be cascaded
  - Unity Gain




$$f_c = \frac{1}{2\pi RC}$$


$$A = 1$$

$$A_v = \frac{A}{\sqrt{1 + \left(\frac{f}{f_c}\right)^2}}$$

# RC Active Filters

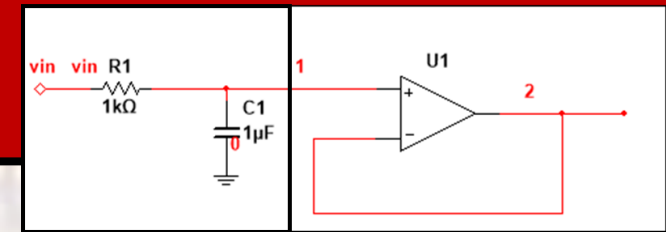

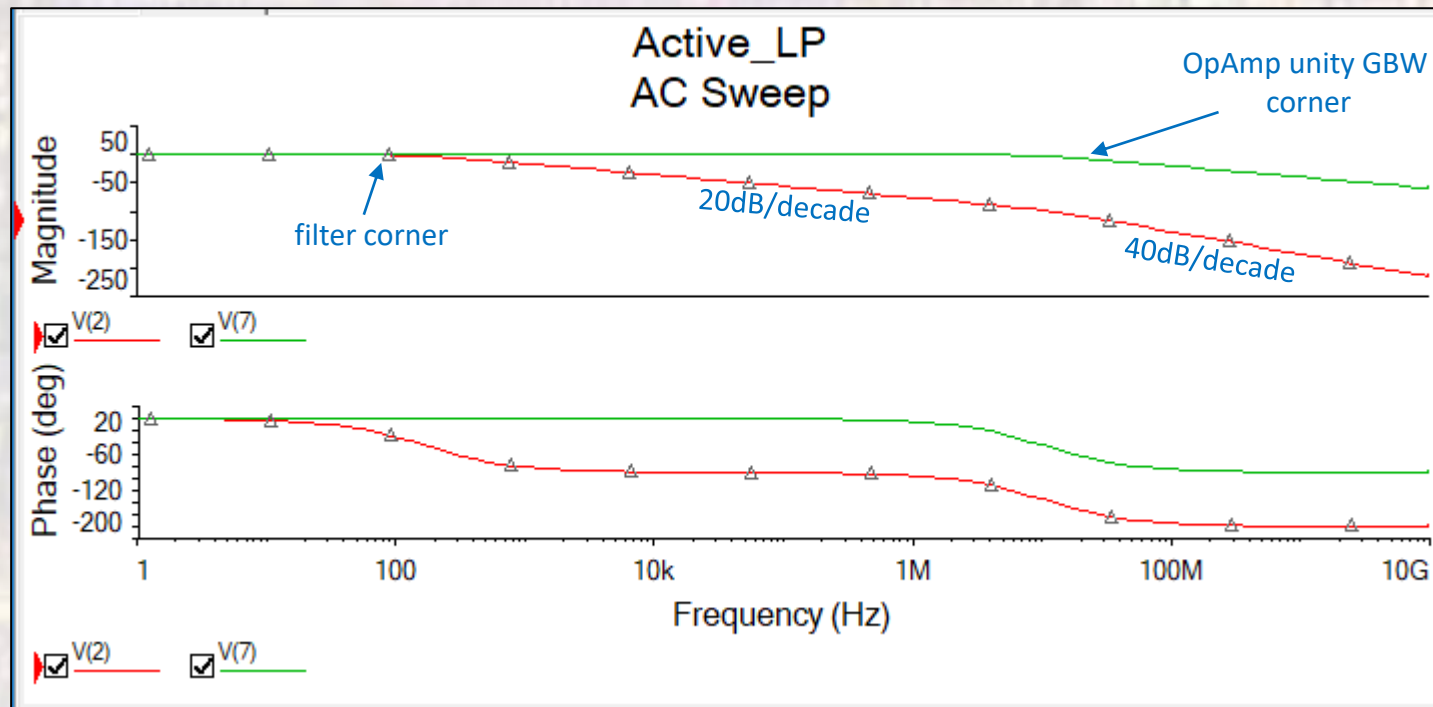
- Just buffer the passive filter – **Caveat # 1**
  - The OpAmp has an internal Lowpass characteristic (GBWP)
    - Can be good or bad depending on the situation




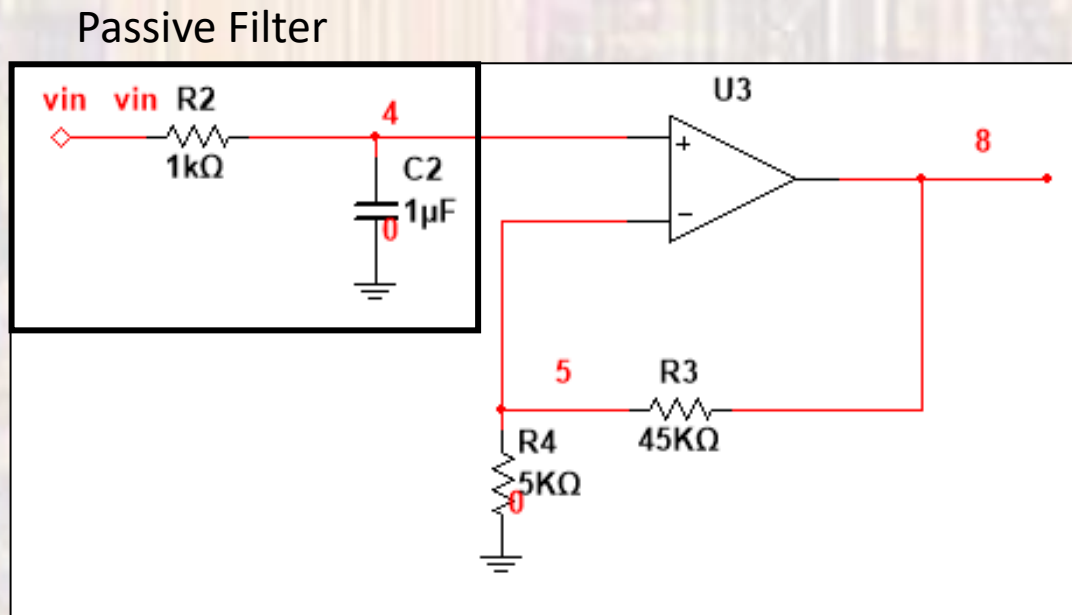
# RC Active Filters

- Buffer the passive filter with gain – Low Pass
  - Non-inverting
  - Load insensitive
  - Can be cascaded
  - Selectable Gain




$$f_c = \frac{1}{2\pi RC}$$

$$A = 1 + \frac{R_F}{R_I}$$

$$A_v = \frac{A}{\sqrt{1 + \left(\frac{f}{f_c}\right)^2}}$$

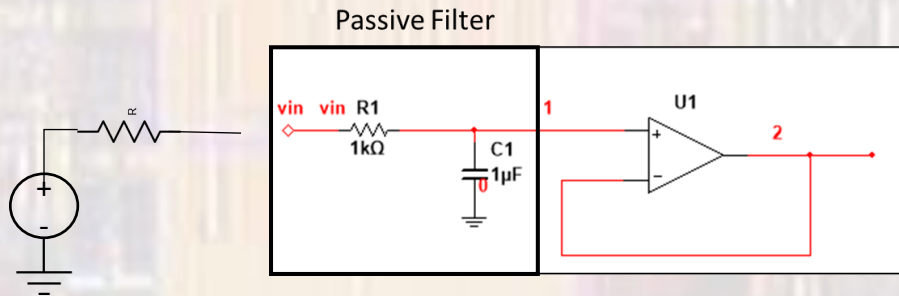
# RC Active Filters

- Buffer the passive filter – **Caveat # 2**
  - The filter has a relatively small input impedance
    - Loads the driver
    - Driver output impedance may affect the filter


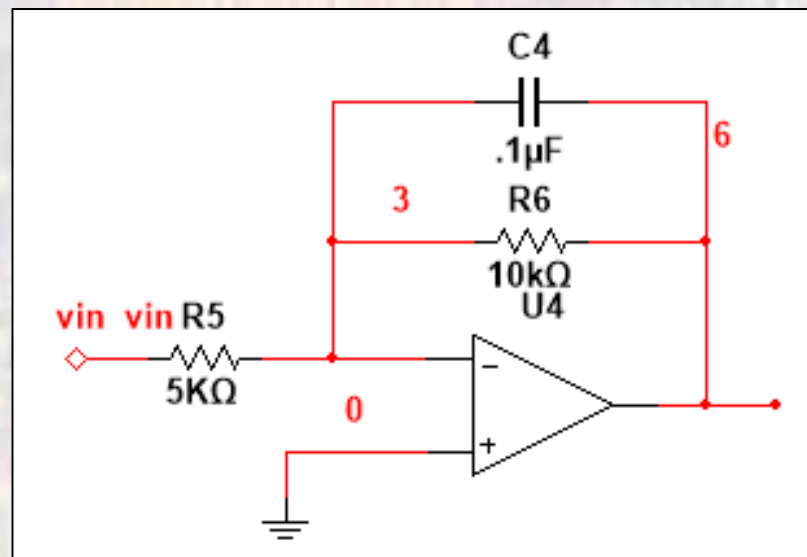
# RC Active Filters

- Buffer the passive filter – Low Pass
  - Remove the reactive element from the input
  - Inverting
  - Selectable Gain



$$f_c = \frac{1}{2\pi R_F C}$$


$$A = -\frac{R_F}{R_I}$$

$$A_v = \frac{A}{\sqrt{1 + \left(\frac{f}{f_c}\right)^2}}$$


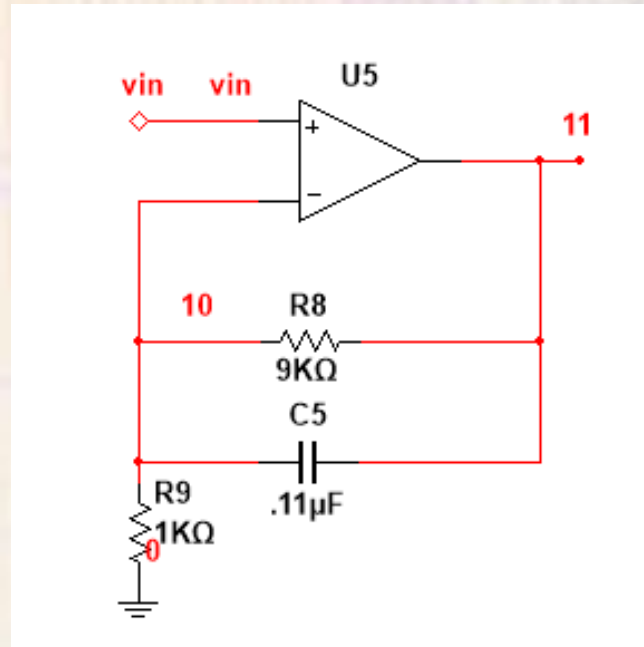
# RC Active Filters

- Buffer the passive filter – Low Pass
  - Remove the reactive element from the input
  - Non-inverting
  - Selectable gain
  - High frequencies  $\rightarrow$  unity gain



$$f_c = \frac{1}{2\pi R_F C}$$


$$A = 1 + \frac{R_F}{R_I}$$

$$A_v^* = \frac{A}{\sqrt{1 + \left(\frac{f}{f_c}\right)^2}}$$

$$* A_{v \min} = 1 = 0dB$$
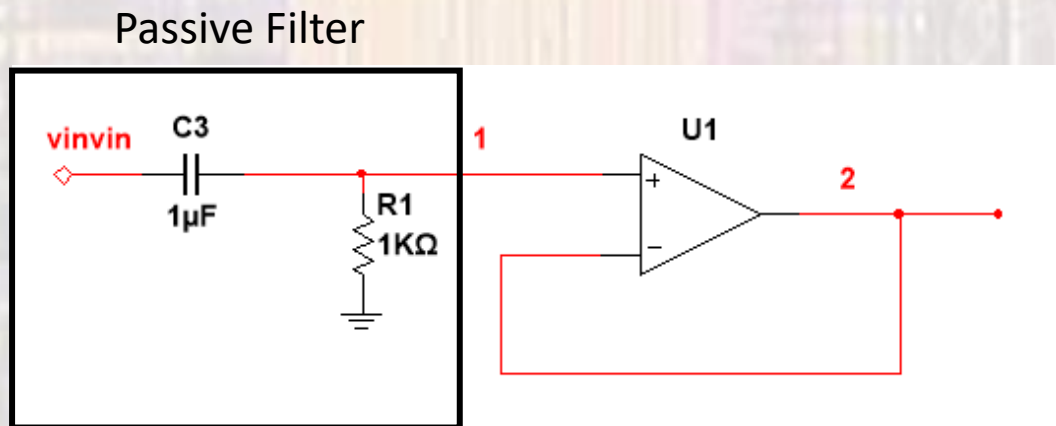
# 1<sup>st</sup> Order RC Active Filters

- First order – High Pass
  - Non-inverting
  - Unity Gain




$$f_c = \frac{1}{2\pi RC}$$

$$A = 1$$

$$A_v = \frac{A \left( \frac{f}{f_c} \right)}{\sqrt{1 + \left( \frac{f}{f_c} \right)^2}}$$
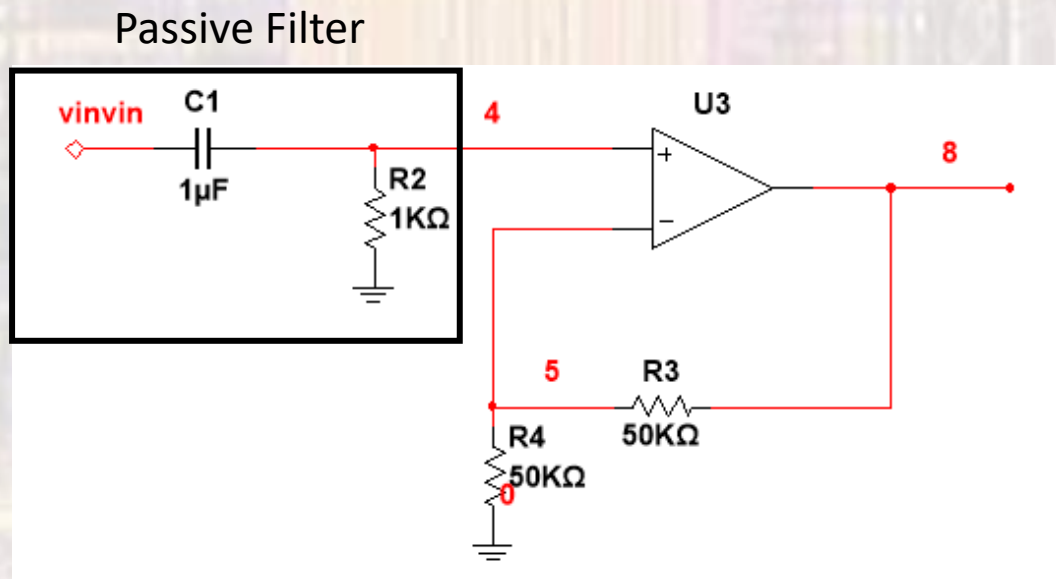
# 1<sup>st</sup> Order RC Active Filters

- First order – High Pass
  - Non-inverting
  - Selectable Gain




$$f_c = \frac{1}{2\pi RC}$$

$$A = 1 + \frac{R_F}{R_I}$$

$$A_v = \frac{A\left(\frac{f}{f_c}\right)}{\sqrt{1 + \left(\frac{f}{f_c}\right)^2}}$$
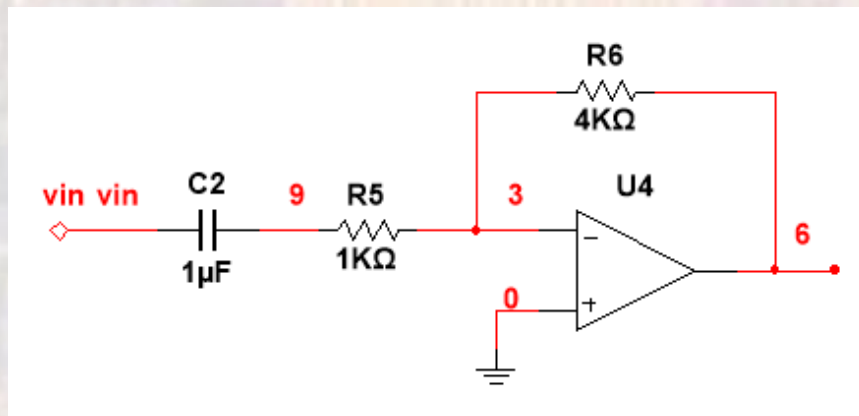
# 1<sup>st</sup> Order RC Active Filters

- First order – High Pass
  - Inverting
  - Selectable Gain




$$f_c = \frac{1}{2\pi RC}$$

$$A = -\frac{R_F}{R_I}$$

$$A_v = \frac{A\left(\frac{f}{f_c}\right)}{\sqrt{1 + \left(\frac{f}{f_c}\right)^2}}$$
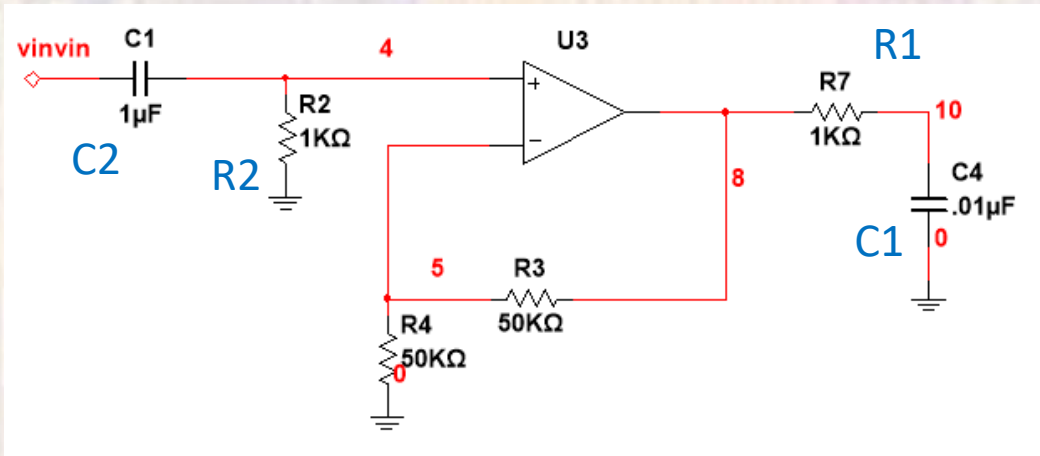
# 1<sup>st</sup> Order RC Active Filters

- First order – Band Pass
  - Non-inverting
  - Selectable Gain
  - Wide passband



$$f_{CL} = \frac{1}{2\pi R_2 C_2}$$

$$f_{CU} = \frac{1}{2\pi R_1 C_1}$$


$$A = 1 + \frac{R_F}{R_I}$$

$$A_v = \frac{A \left( \frac{f}{f_{CH}} \right)}{\sqrt{1 + \left( \frac{f}{f_{CH}} \right)^2}} \frac{1}{\sqrt{1 + \left( \frac{f}{f_{CL}} \right)^2}}$$


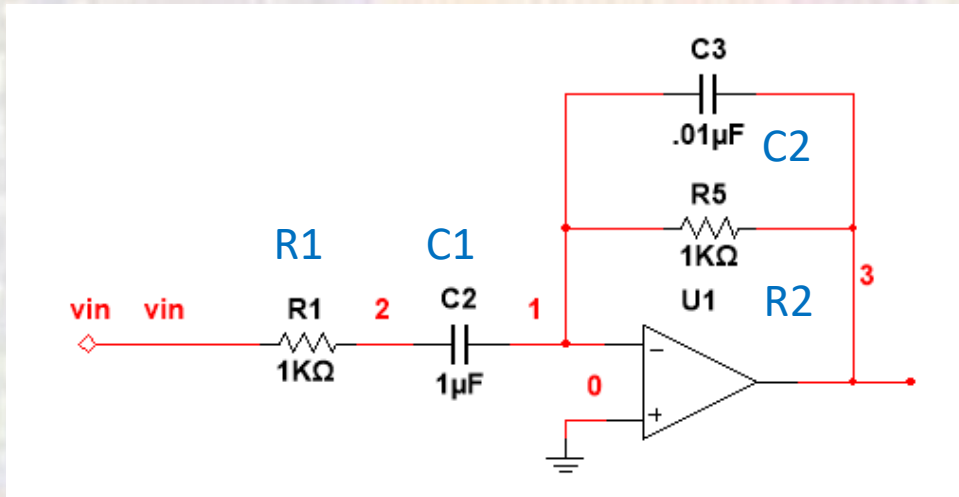
# 1<sup>st</sup> Order RC Active Filters

- First order – Band Pass
  - Inverting
  - Selectable Gain
  - Narrower passbands possible



$$f_{CL} = \frac{1}{2\pi R1 C1}$$

$$f_{CU} = \frac{1}{2\pi R2 C2}$$


$$A = -\frac{R_F}{R_I}$$

$$A_v^* = \frac{A \left( \frac{f}{f_{CH}} \right)}{\sqrt{1 + \left( \frac{f}{f_{CH}} \right)^2}} \frac{1}{\sqrt{1 + \left( \frac{f}{f_{CL}} \right)^2}}$$

\* At high frequencies, the OpAmp internal capacitance limits the rolloff
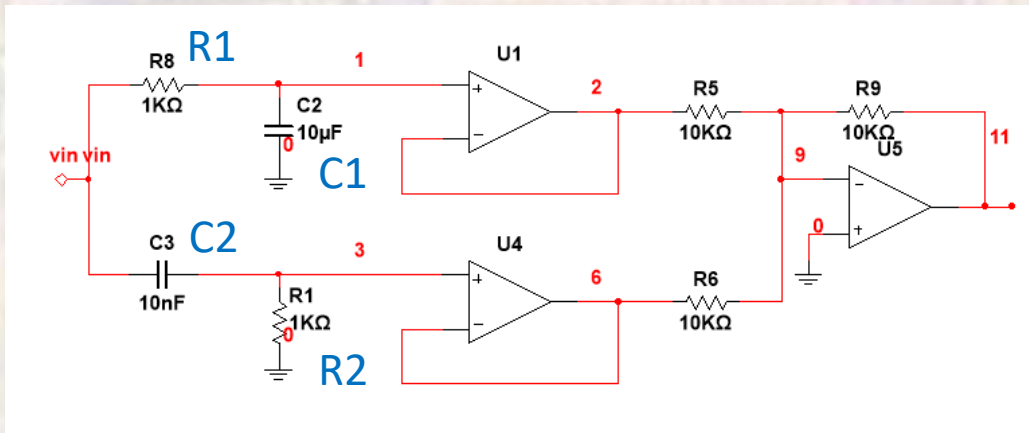
# 1<sup>st</sup> Order RC Active Filters

- First order – Band Stop
  - Non-inverting
  - Selectable Gain



$$f_{CL} = \frac{1}{2\pi R1C1}$$

$$f_{CU} = \frac{1}{2\pi R2C2}$$


$$A = -\frac{R_F}{R_I}$$

$$A_v^* = \frac{A \left( \frac{f}{f_{CH}} \right)}{\sqrt{1 + \left( \frac{f}{f_{CH}} \right)^2}} \frac{1}{\sqrt{1 + \left( \frac{f}{f_{CL}} \right)^2}}$$

\* At high frequencies, the OpAmp internal capacitance limits the rolloff

# 2<sup>nd</sup> Order RC Active Filters


- Generalized Second Order Configuration

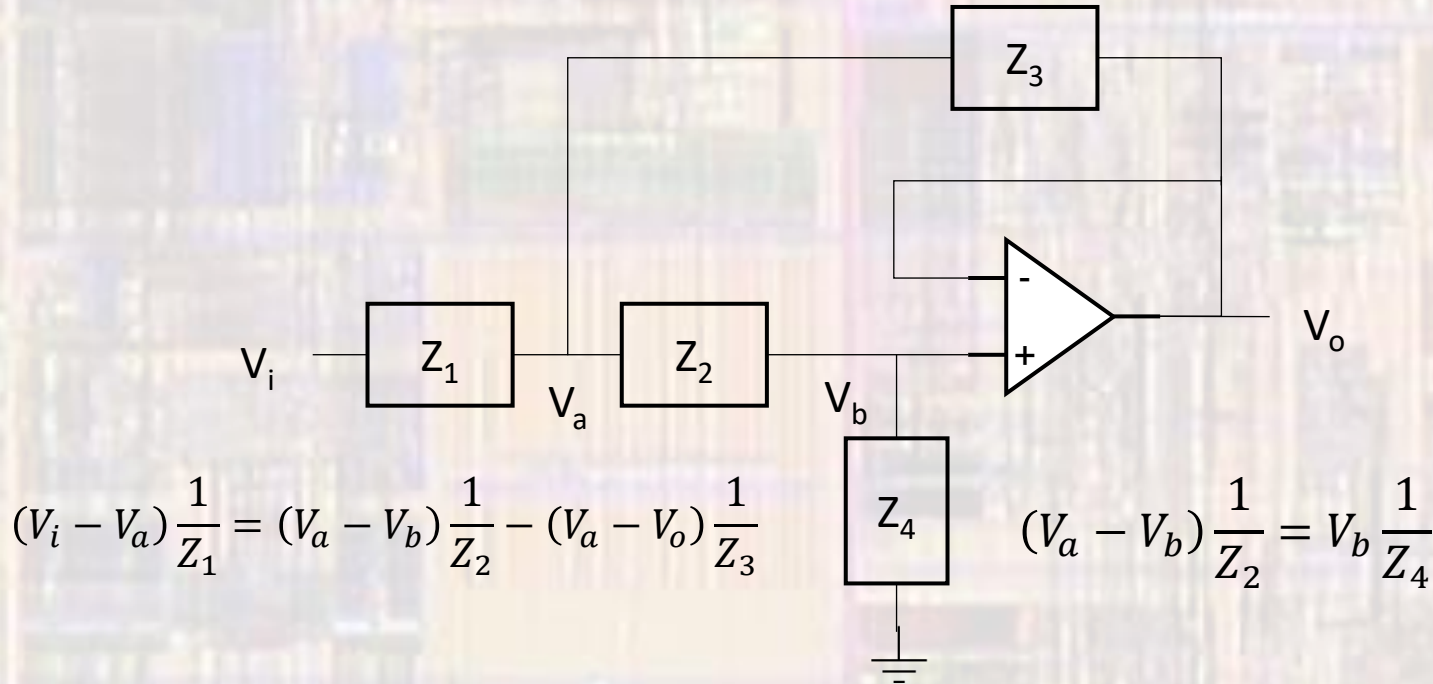

$$A_v = \frac{\frac{1}{Z_1} \frac{1}{Z_2}}{\frac{1}{Z_1} \frac{1}{Z_2} + \frac{1}{Z_4} \left( \frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3} \right)}$$

# 2<sup>nd</sup> Order RC Active Filters

- Generalized Second Order Configuration

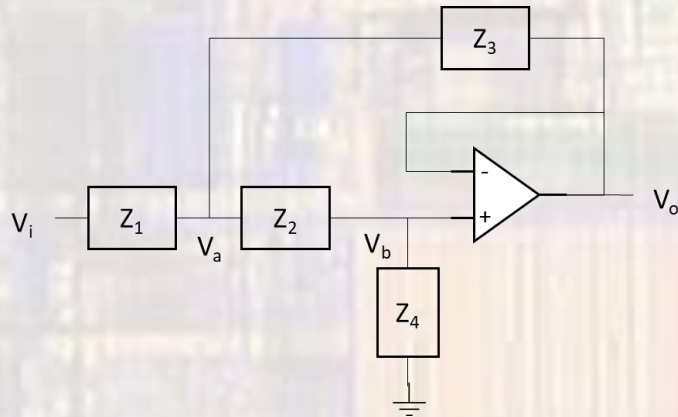

$$A_v = \frac{\frac{1}{Z_1} \frac{1}{Z_2}}{\frac{1}{Z_1} \frac{1}{Z_2} + \frac{1}{Z_4} \left( \frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3} \right)}$$

- Can be generalized to the form

$$H_s = \frac{a_2 s^2 + a_1 s + a_0}{s^2 + s \frac{\omega_0}{Q} + \omega_0^2}$$

$\omega$  – characteristic frequency


$Q$  – quality factor

$a_0 \neq 0$     low pass  
 $a_1 \neq 0$     band pass  
 $a_2 \neq 0$     high pass




# 2<sup>nd</sup> Order RC Active Filters

- Generalized Second Order Configuration

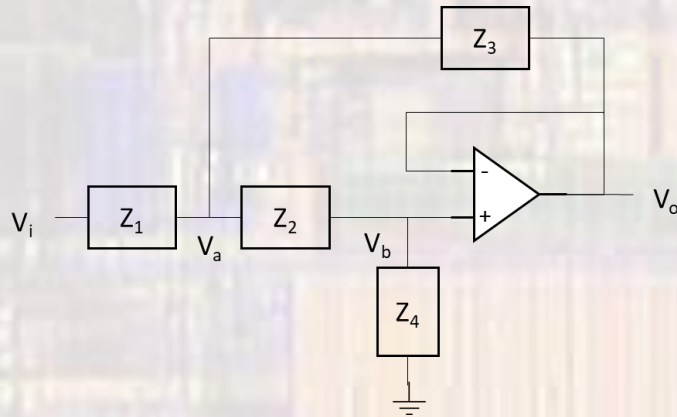

$$H_s = \frac{a_2 s^2 + a_1 s + a_0}{s^2 + s \frac{\omega_0}{Q} + \omega_0^2}$$

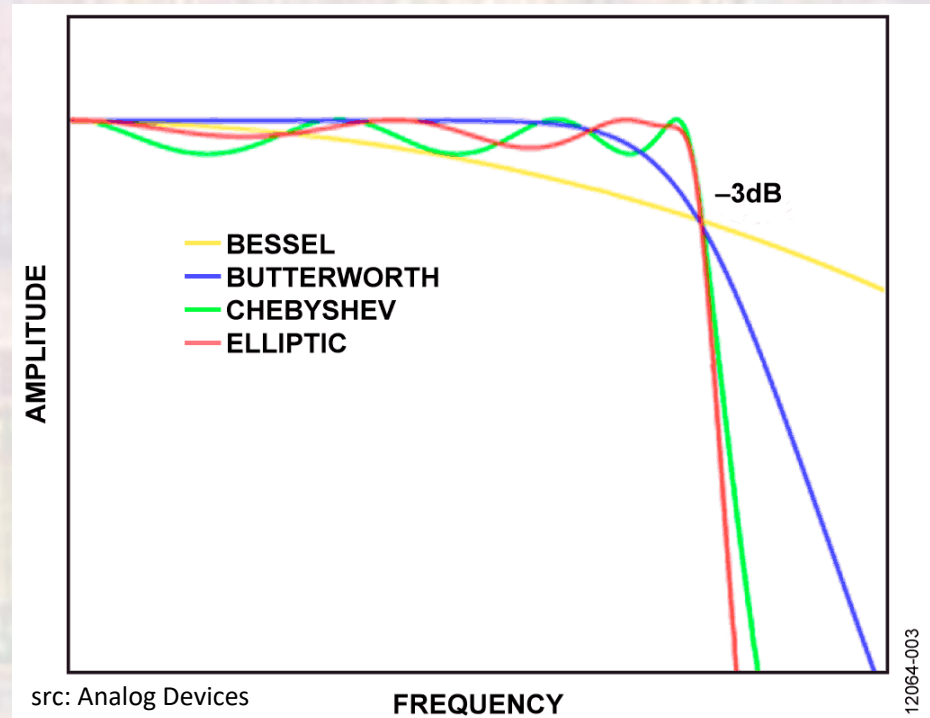- Variations in  $a$ ,  $\omega$ , and  $Q$  generate different passband characteristics
- $a$ ,  $\omega$ , and  $Q$  are set by the values of  $Z_1$ ,  $Z_2$ ,  $Z_3$ ,  $Z_4$





# 2<sup>nd</sup> Order RC Active Filters

- Butterworth – Maximally Flat
  - Low Pass



$$H_s = \frac{a_2 s^2 + a_1 s + a_0}{s^2 + s \frac{\omega_0}{Q} + \omega_0^2}$$

For the Butterworth response

$$R_1 = R_2$$

$$C_3 = 2C_4$$
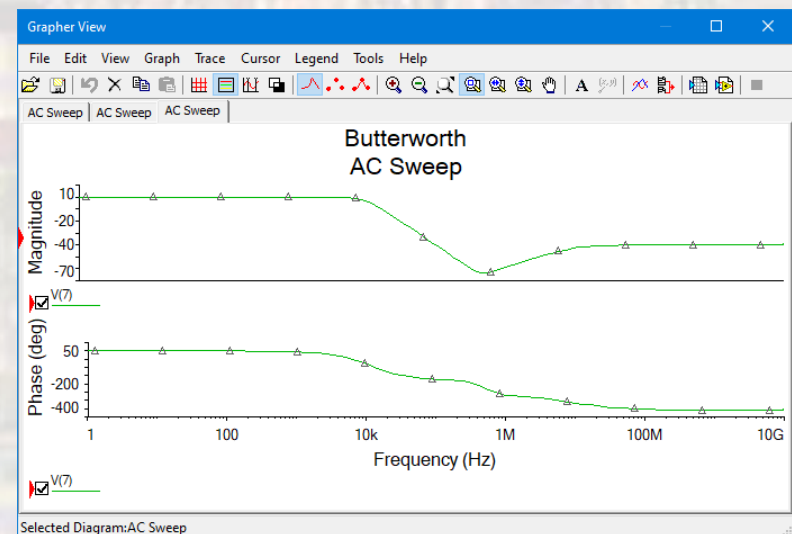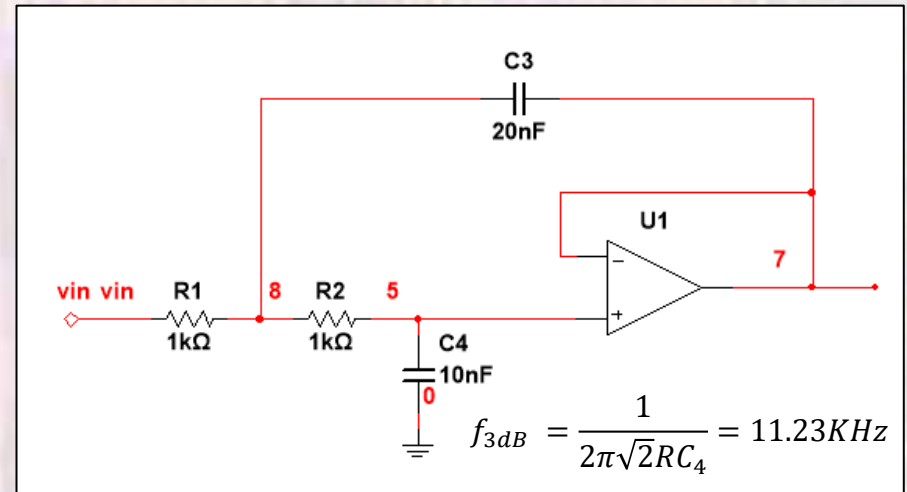
$$\omega_{3dB} = \frac{1}{\sqrt{2}RC_4}$$



# 2<sup>nd</sup> Order RC Active Filters

- Butterworth – Maximally Flat
  - High Pass



$$H_s = \frac{a_2 s^2 + a_1 s + a_0}{s^2 + s \frac{\omega_0}{Q} + \omega_0^2}$$

For the Butterworth response

$$R_4 = 2R_3$$

$$C_1 = C_2$$


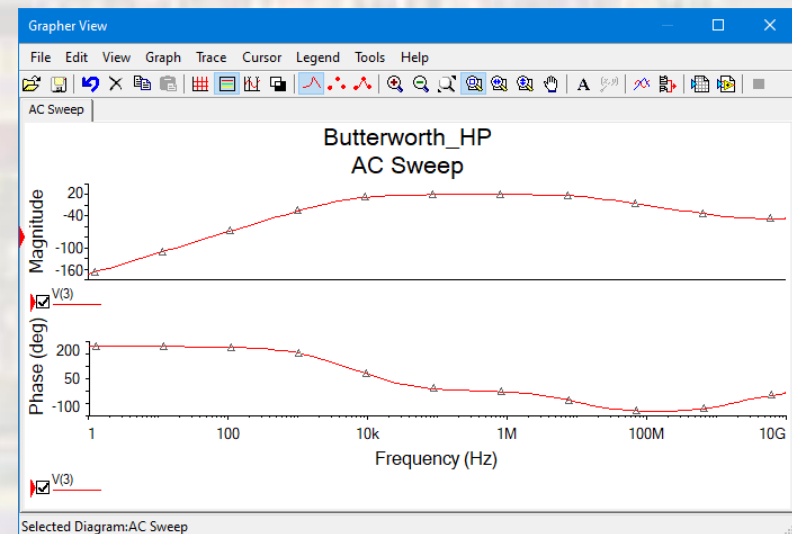
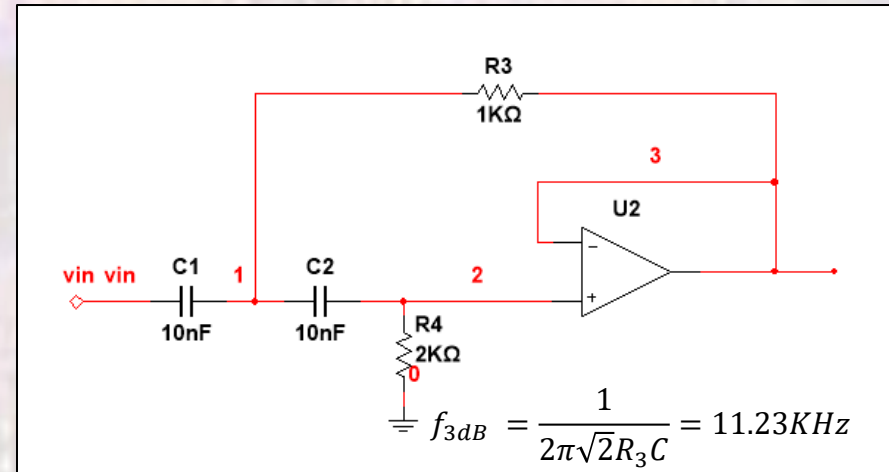
$$\omega_{3dB} = \frac{1}{\sqrt{2}R_3C}$$


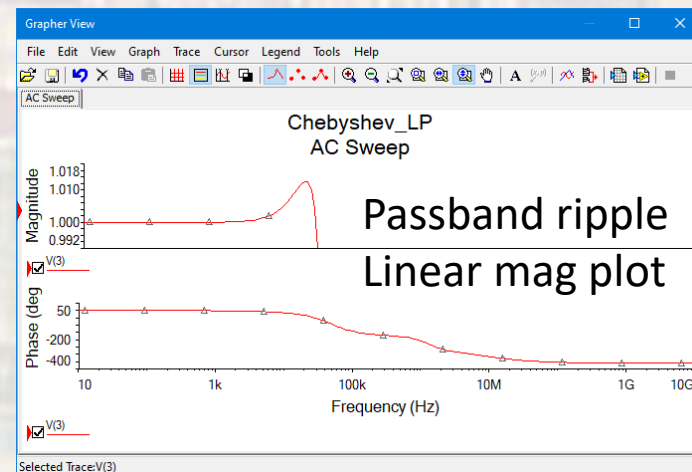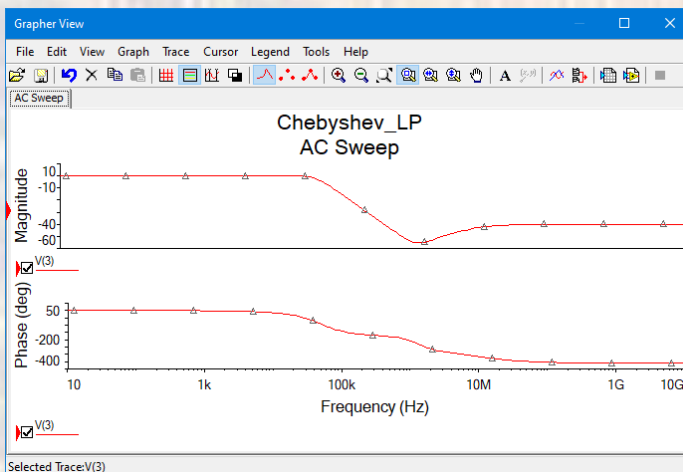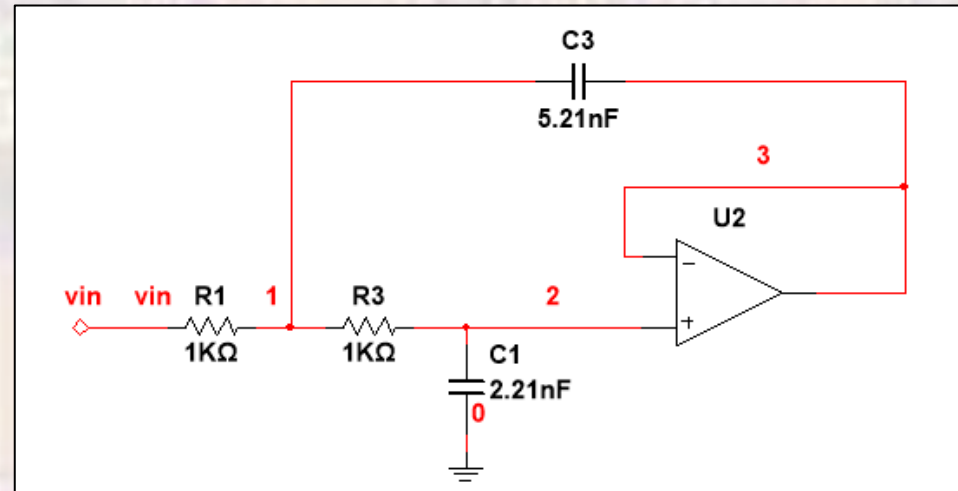
# 2<sup>nd</sup> Order RC Active Filters


- Chebyshev – Enhanced initial rolloff
  - Low Pass

$$H_s = \frac{a_2 s^2 + a_1 s + a_0}{s^2 + s \frac{\omega_0}{Q} + \omega_0^2}$$


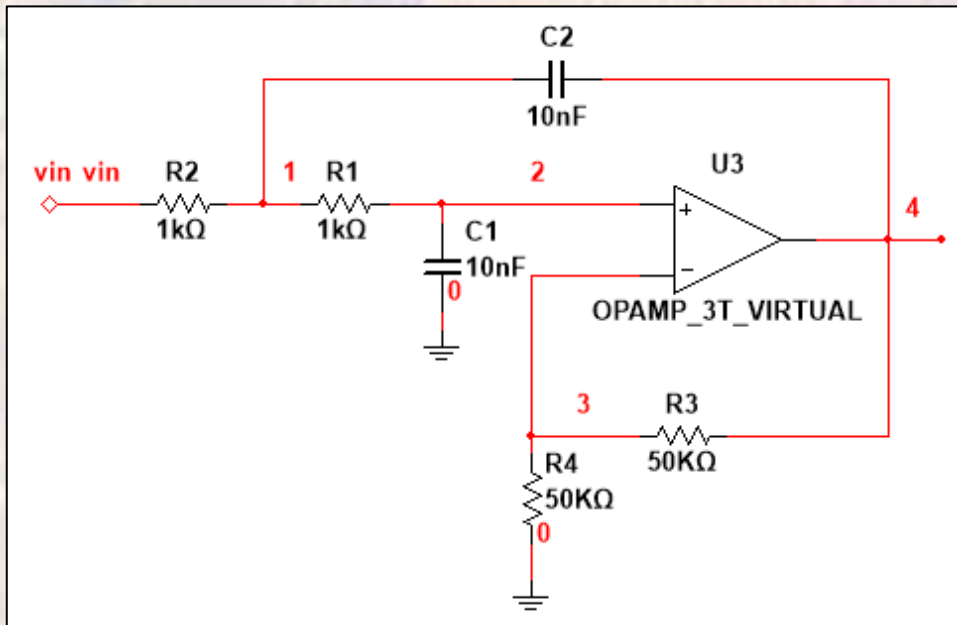
# 2<sup>nd</sup> Order RC Active Filters

- Second order filters
  - Non-inverting
  - Selectable gain
  - High frequencies → unity gain



$$f_c = \frac{1}{2\pi\sqrt{R_1 C_1 R_2 C_2}}$$

$$A = 1 + \frac{R_F}{R_I}$$

$$A_v = A \times \frac{\omega_0^2}{\sqrt{(\omega_0^2 - \omega^2)^2 + \left(\frac{\omega_0}{Q} \times \omega\right)^2}}$$

# 2<sup>nd</sup> Order RC Active Filters

- Second order filters
  - 2<sup>nd</sup> order filters with gain exhibit a more complex response than 2<sup>nd</sup> order passive filters
    - Q – quality factor = gain at the 3db point
    - ζ – zeta – damping factor = 1/(2Q)
    - ω<sub>0</sub> – characteristic frequency – where things change in the frequency response

2<sup>nd</sup> order LPF

$$A_v = A \times \left| \frac{\omega_0^2}{-\omega^2 + j \left(\frac{\omega_0}{Q}\right) \omega + \omega_0^2} \right| = A \times \frac{\omega_0^2}{\sqrt{(\omega_0^2 - \omega^2)^2 + \left(\frac{\omega_0}{Q} \times \omega\right)^2}}$$

$$\omega_c = \omega_0 \sqrt{1 - \frac{1}{2Q^2} + \sqrt{1 + \left(1 - \frac{1}{2Q^2}\right)^2}}$$

$$Q = \frac{1}{A - 3}$$

$$A = 3 - \frac{1}{Q}$$



# 2<sup>nd</sup> Order RC Active Filters

- Second order filters
  - 2<sup>nd</sup> order filters with gain exhibit a more complex response than 2<sup>nd</sup> order passive filters

2<sup>nd</sup> order LPF

$$A_v = A \times \frac{\omega_0^2}{\sqrt{(\omega_0^2 - \omega^2)^2 + \left(\frac{\omega_0}{Q} \times \omega\right)^2}}$$

$$\omega = 0, \quad A_v = A$$

$$\omega = \omega_0, \quad A_v = A \times Q$$

$$\omega \gg \omega_0, \quad A_v = A \times \frac{\omega_0^2}{\omega^2} = 0$$

$$\omega_c = \omega_0 \sqrt{1 - \frac{1}{2Q^2} + \sqrt{1 + \left(1 - \frac{1}{2Q^2}\right)^2}}$$

$$Q = \frac{1}{\sqrt{2}}, \quad \omega_c = \omega_0, \quad A = 1.58$$

# 2<sup>nd</sup> Order RC Active Filters

- Second order filters

- 2<sup>nd</sup> order filters with gain exhibit a more complex response than 2<sup>nd</sup> order passive filters

- Over damped: Filter response is smooth and slow  
Transient response is smooth and slow

$$A < 1.586 \quad Q < \frac{1}{\sqrt{2}} \quad \zeta > 0.707$$

- Critically damped: Filter response matches the passive filter





$$A = 1.586 \quad Q = \frac{1}{\sqrt{2}} \quad \zeta = 0.707$$





- Under damped: Filter response is peaked  
Transient response “rings”

$$A > 1.586 \quad Q > \frac{1}{\sqrt{2}} \quad \zeta < 0.707$$

- Unstable: Filter circuit oscillates independently
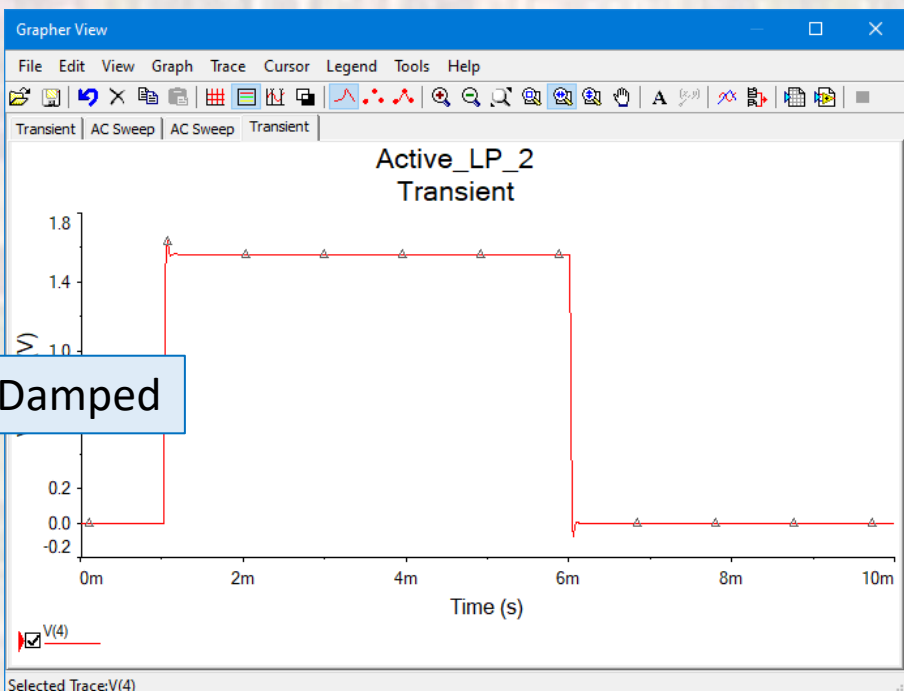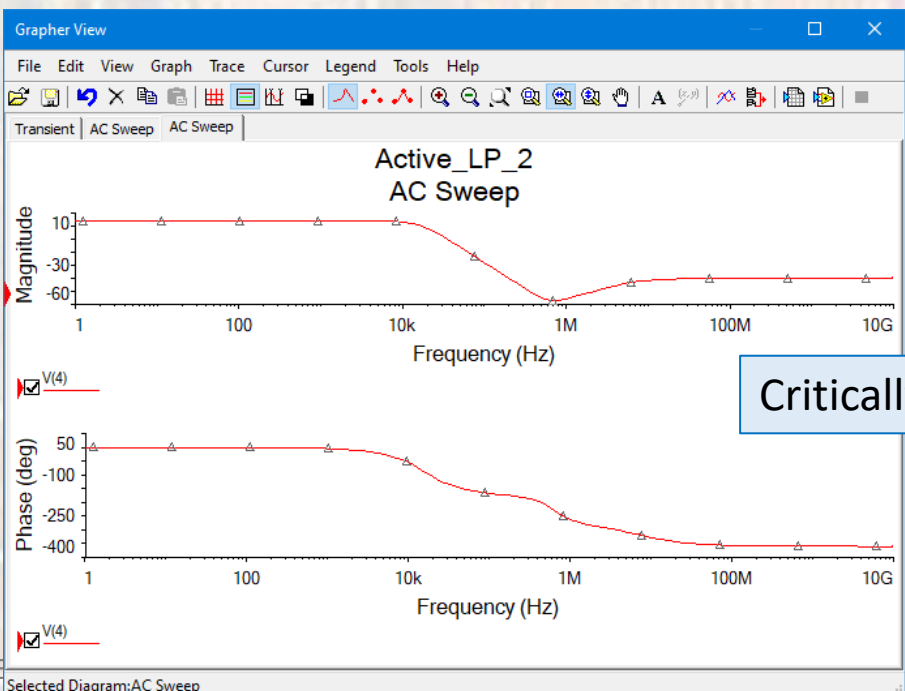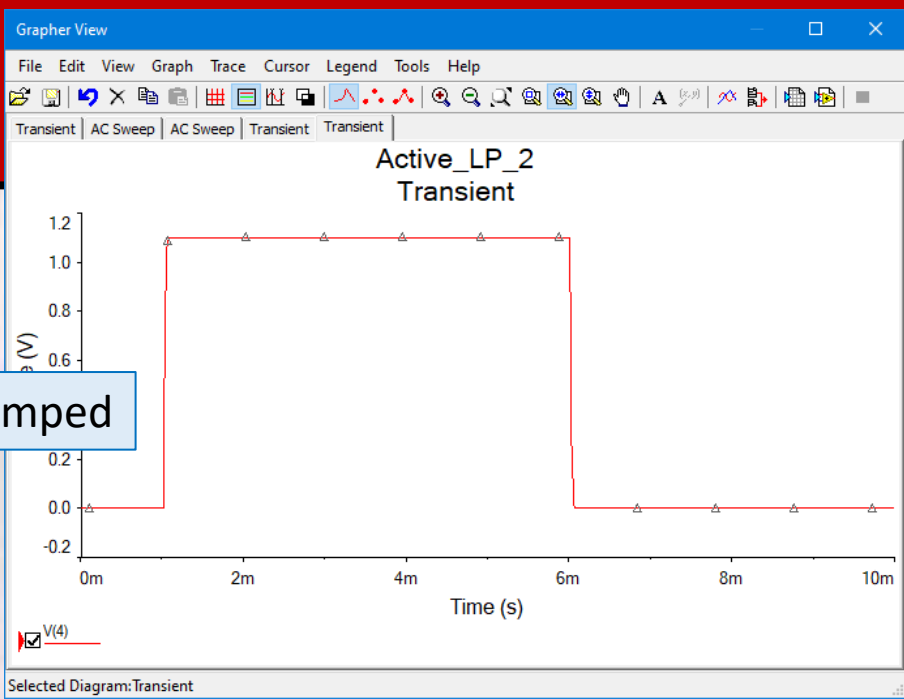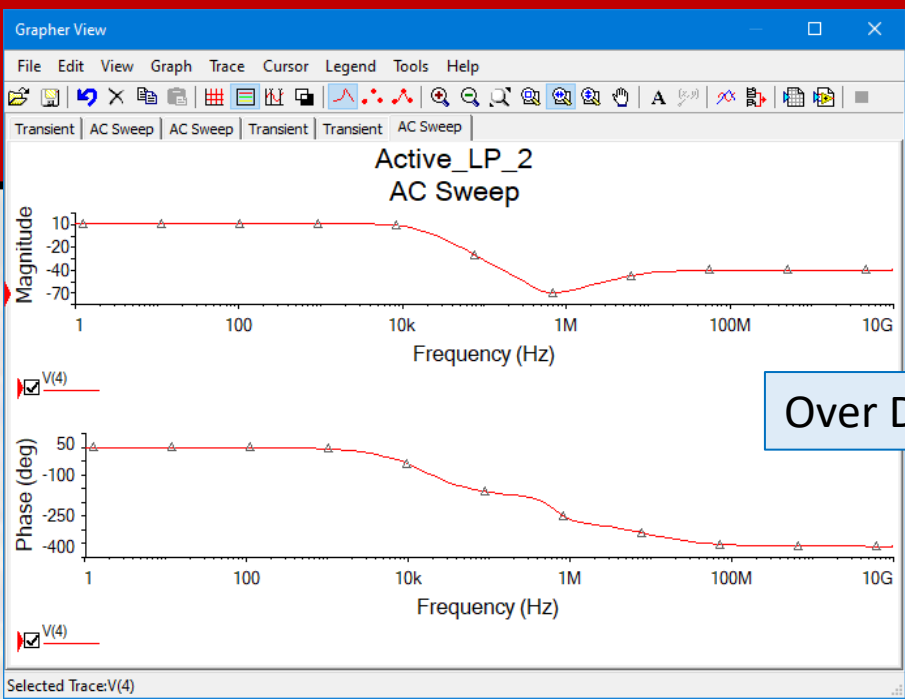
$$A \rightarrow 3 \quad Q = \infty \quad \zeta \rightarrow 0$$



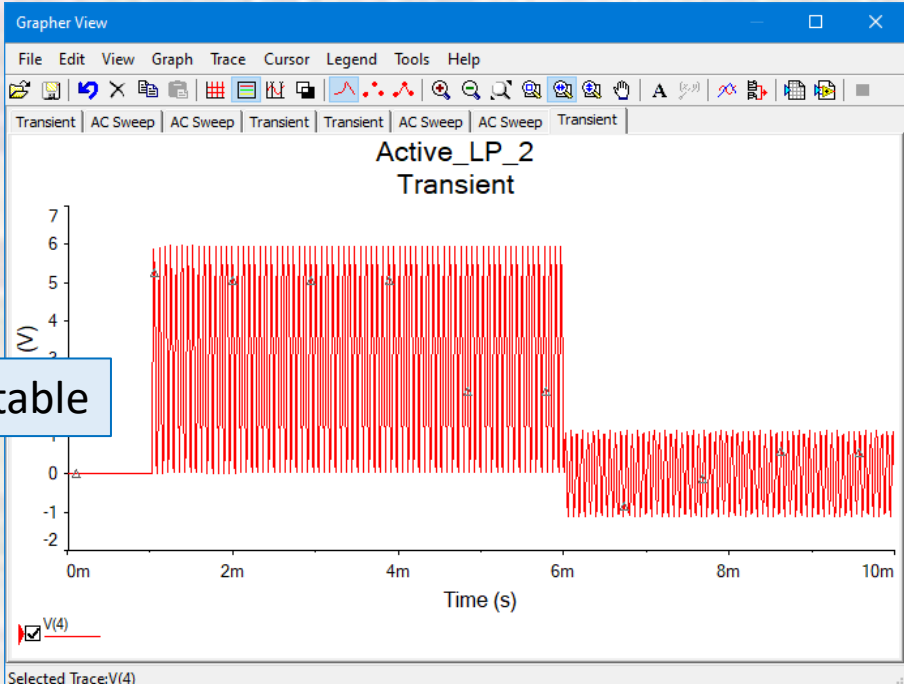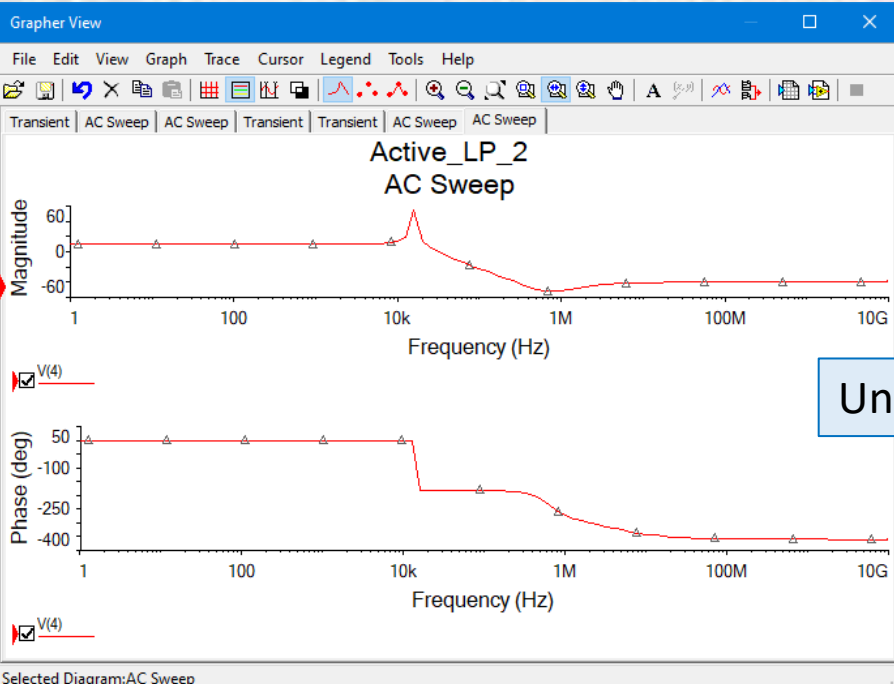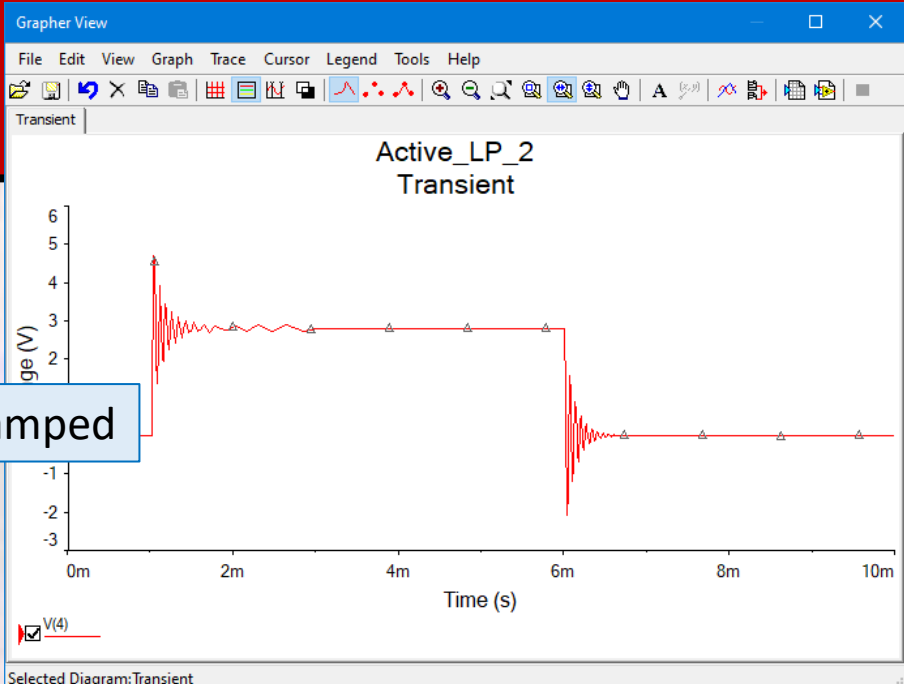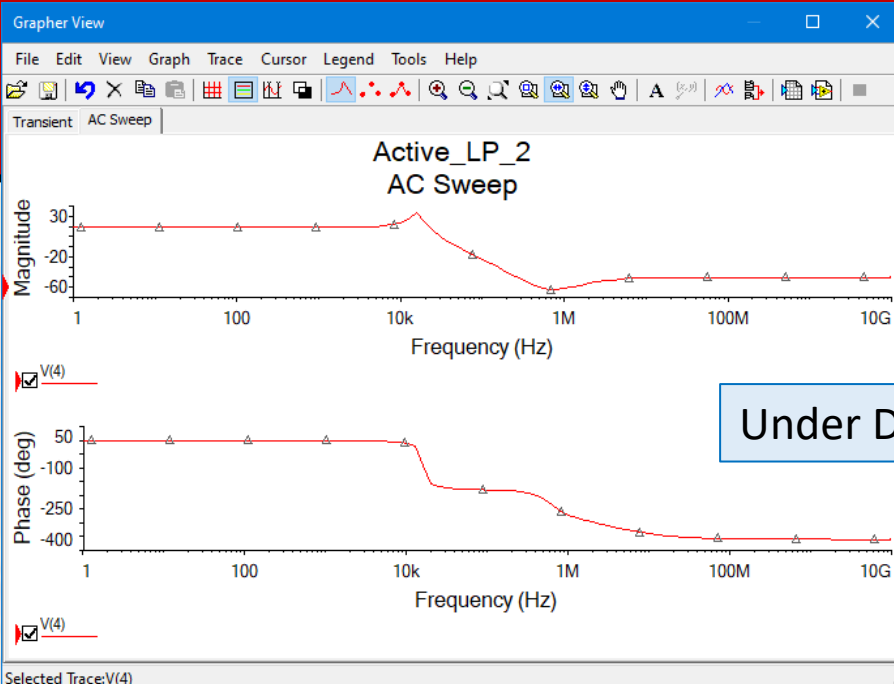

# N<sup>th</sup> Order RC Active Filters

- Order > 2 active Filters
  - Cascade 1<sup>st</sup> and 2<sup>nd</sup> order stages
  - Remember, gain can be tricky in 2<sup>nd</sup> order stages
    - Move gain to 1<sup>st</sup> order stages where possible
- Computer programs and calculators available



# N<sup>th</sup> Order RC Active Filters

- Chebyshev – 5<sup>th</sup> order HP
- High Pass

