

Switched Regulation


Last updated 1/18/24

Switched Regulation

- Switched Regulation
 - Create a DC voltage from an DC signal
 - Input could be from a sloppy linear regulator
 - Uses linear and non-linear components along with switching elements
 - 3 primary types
 - Buck – high voltage to lower voltage with higher current
 - Boost – low voltage to higher voltage with less current
 - Buck-Boost – convert both directions

Switched Regulation

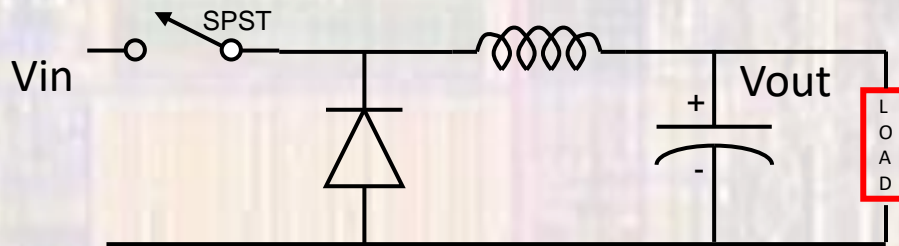- Buck Converter
 - High voltage to lower voltage with higher current
 - Can be very power efficient 95%+



$$V_{out} = V_{in} * \text{Duty Cycle}$$

Choose L or ΔI_L


$$\Delta I_L = \frac{V_{in} \times (1 - D) \times T_{on}}{L}$$

$$L = \frac{(V_{in} - V_{out}) \times D \times (1 - D) \times T_{on}}{\Delta I_L}$$

$$C = \frac{\Delta I_L}{F_s \times V_{out} \times V_{out \text{ ripple}}}$$


Switched Regulation

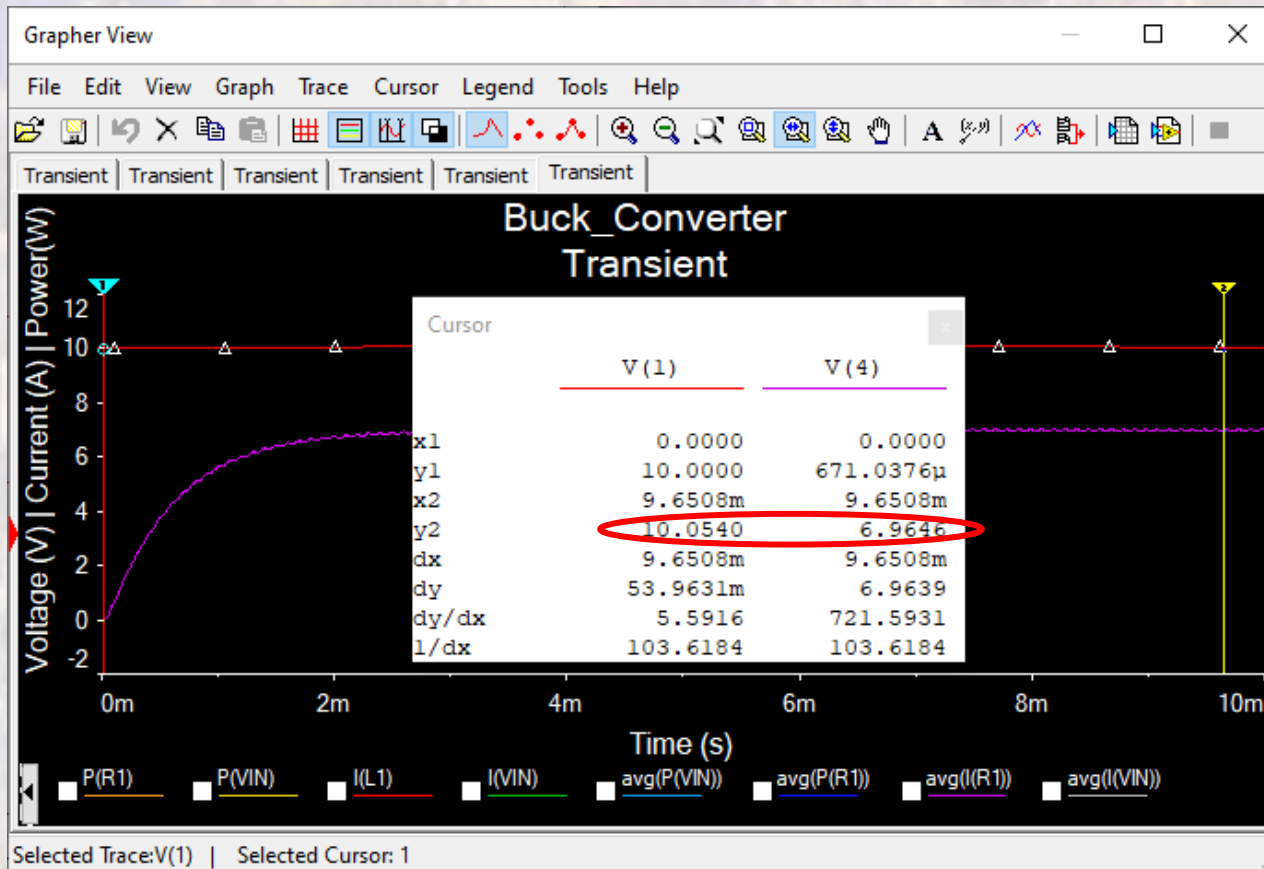- Buck Converter
 - $F_s = 10\text{KHz}$, $D = 0.7$, $L = 44\text{mH}$, $C = 681\text{nF}$, $R_L = 70\Omega$
 - $V_{in} = 10\text{V}$, $V_{out} = 7\text{V}$




Switched Regulation

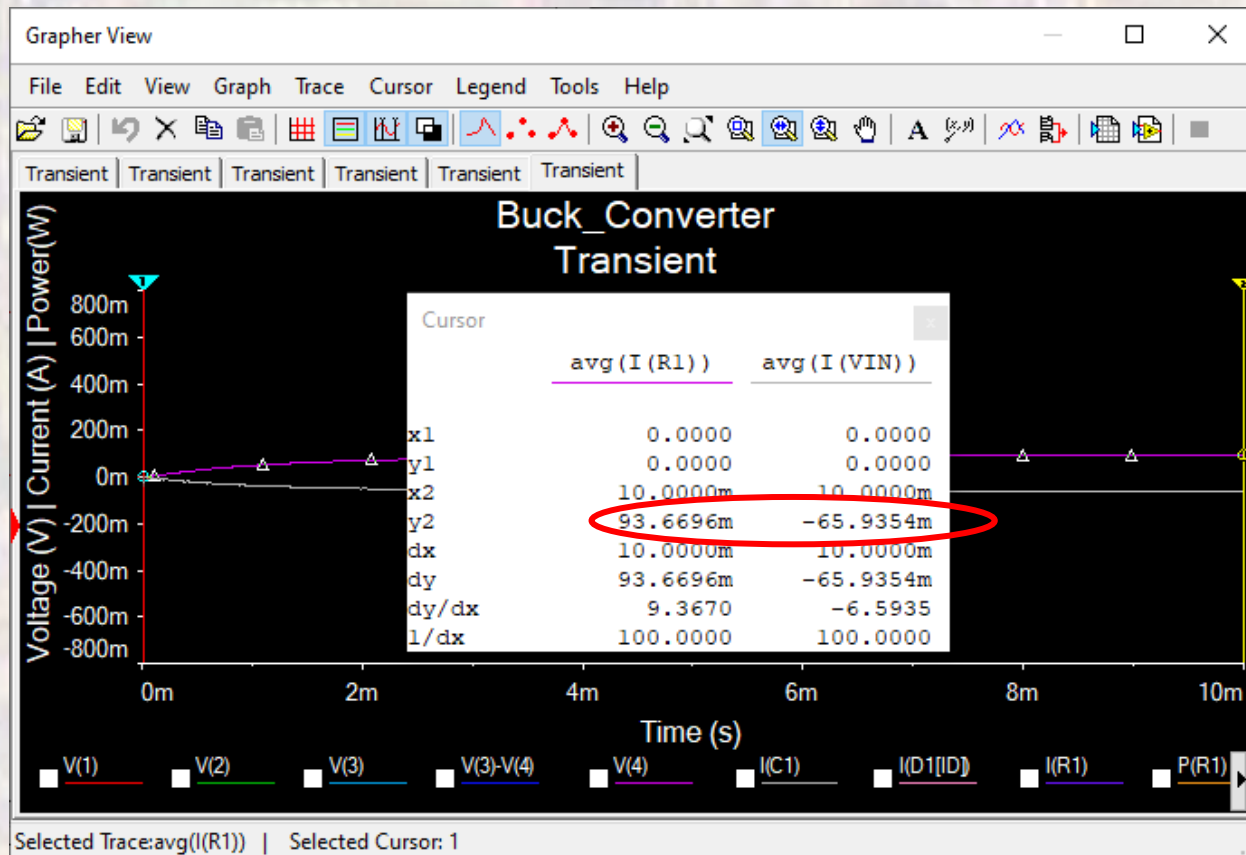- Buck Converter
 - $F_s = 10\text{KHz}$, $D = 0.7$, $L = 44\text{mH}$, $C = 681\text{nF}$, $R_L = 70\Omega$
 - $I_{in} = 66\text{mA}$, $I_{out} = 93.6\text{mA}$




Switched Regulation

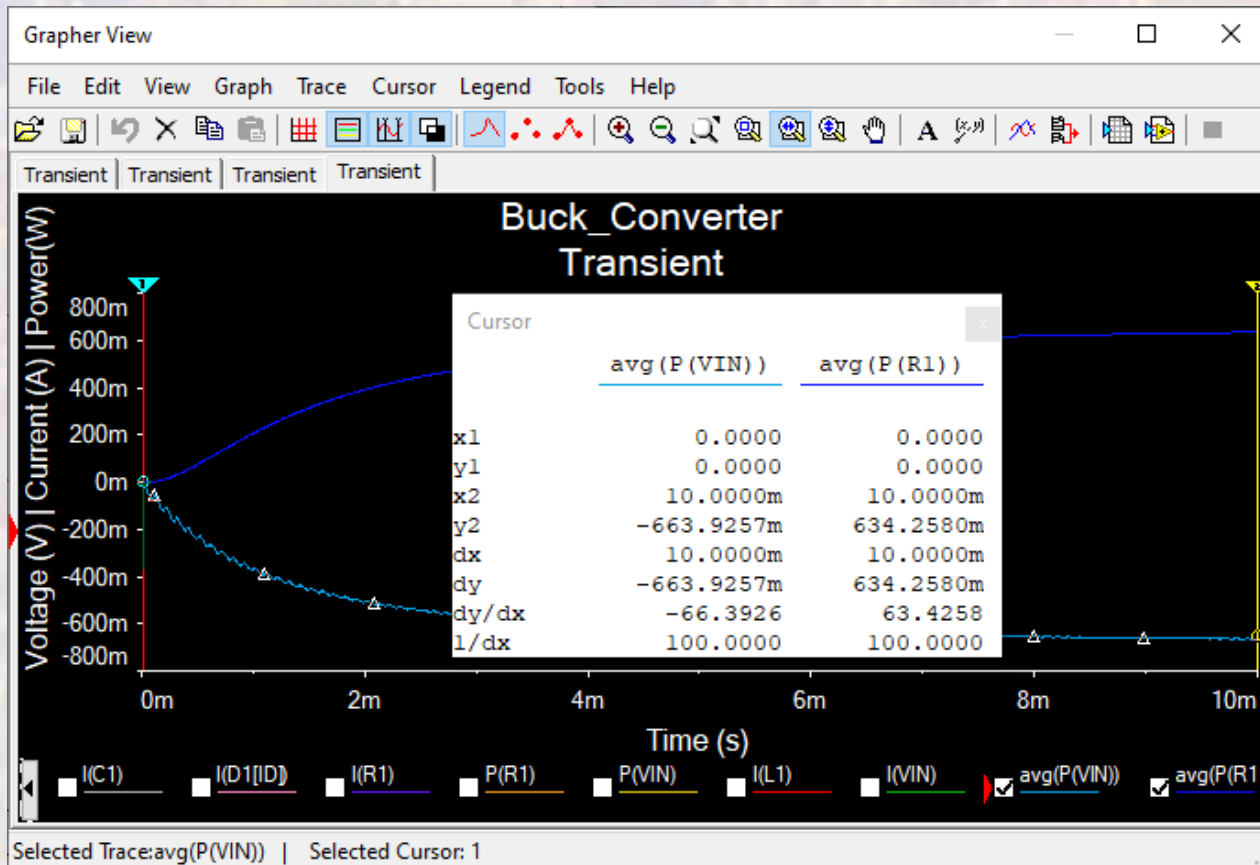- Buck Converter
 - $F_s = 10\text{KHz}$, $D = 0.7$, $L = 44\text{mH}$, $C = 681\text{nF}$, $R_L = 70\Omega$
 - $P_{in} = 663\text{mW}$, $P_{out} = 634\text{mW} \rightarrow 95.5\%$ efficiency



Switched Regulation

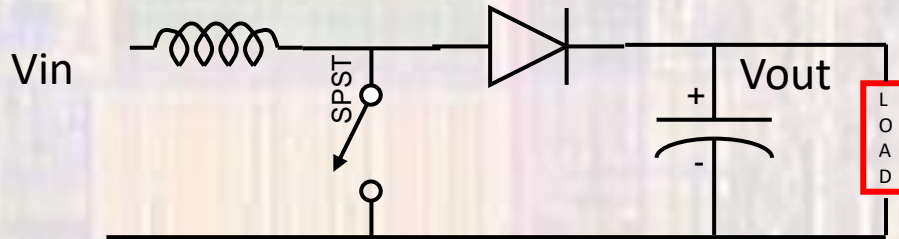- Boost Converter
 - Low voltage to higher voltage with lower current
 - Can be very power efficient 95%+



$$V_{out} = V_{in} / (1 - \text{Duty Cycle})$$

Choose L or ΔI_L


$$\Delta I_L = \frac{V_{out} \times D \times T_{on}}{L}$$

$$L = \frac{V_{in} \times (1 - D) \times T_{on}}{\Delta I_L}$$

$$C = \frac{\Delta I_L}{F_s \times V_{out} \times V_{out \text{ ripple}}}$$


Switched Regulation

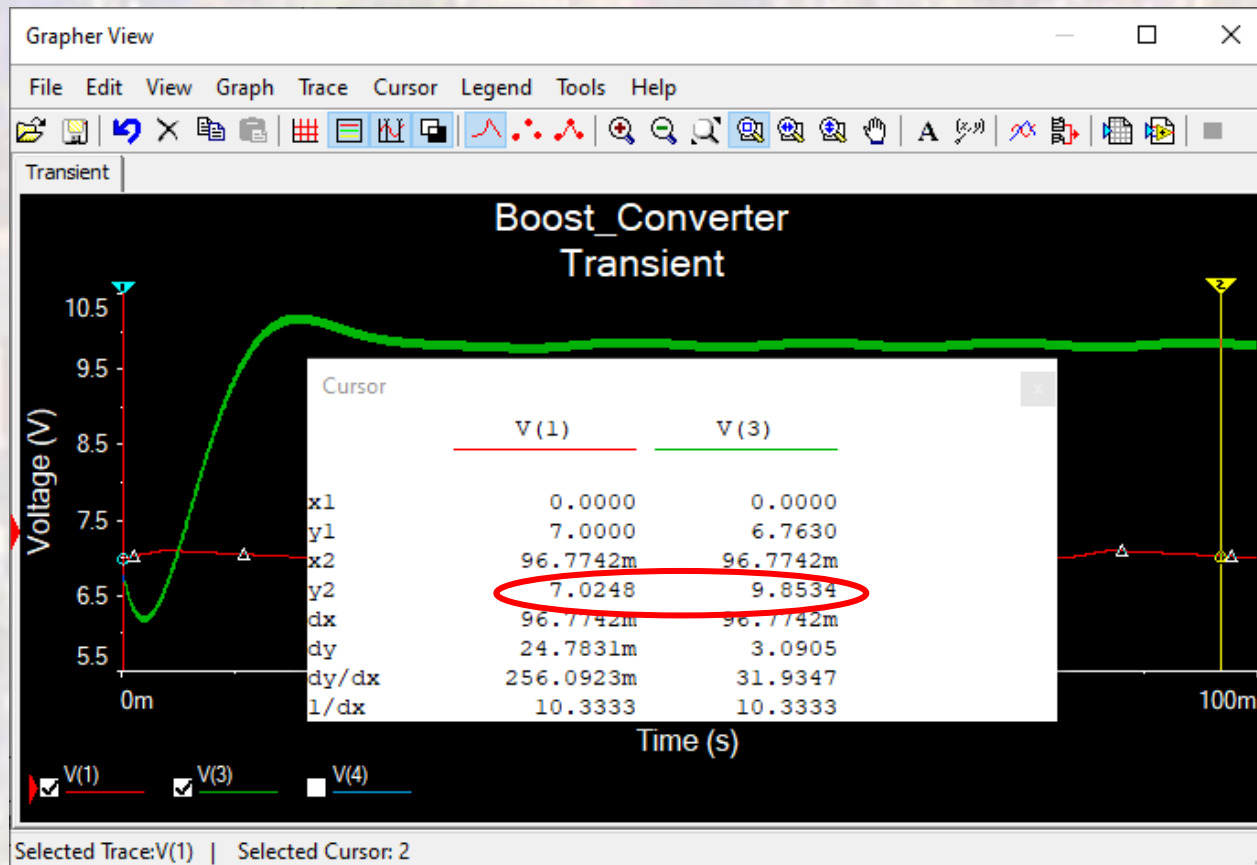- Buck Converter
 - $F_s = 10\text{KHz}$, $D = 0.3$, $L = 147\text{mH}$, $C = 43\mu\text{F}$, $R_L = 70\Omega$
 - $V_{in} = 7\text{V}$, $V_{out} = 10\text{V}$



Switched Regulation

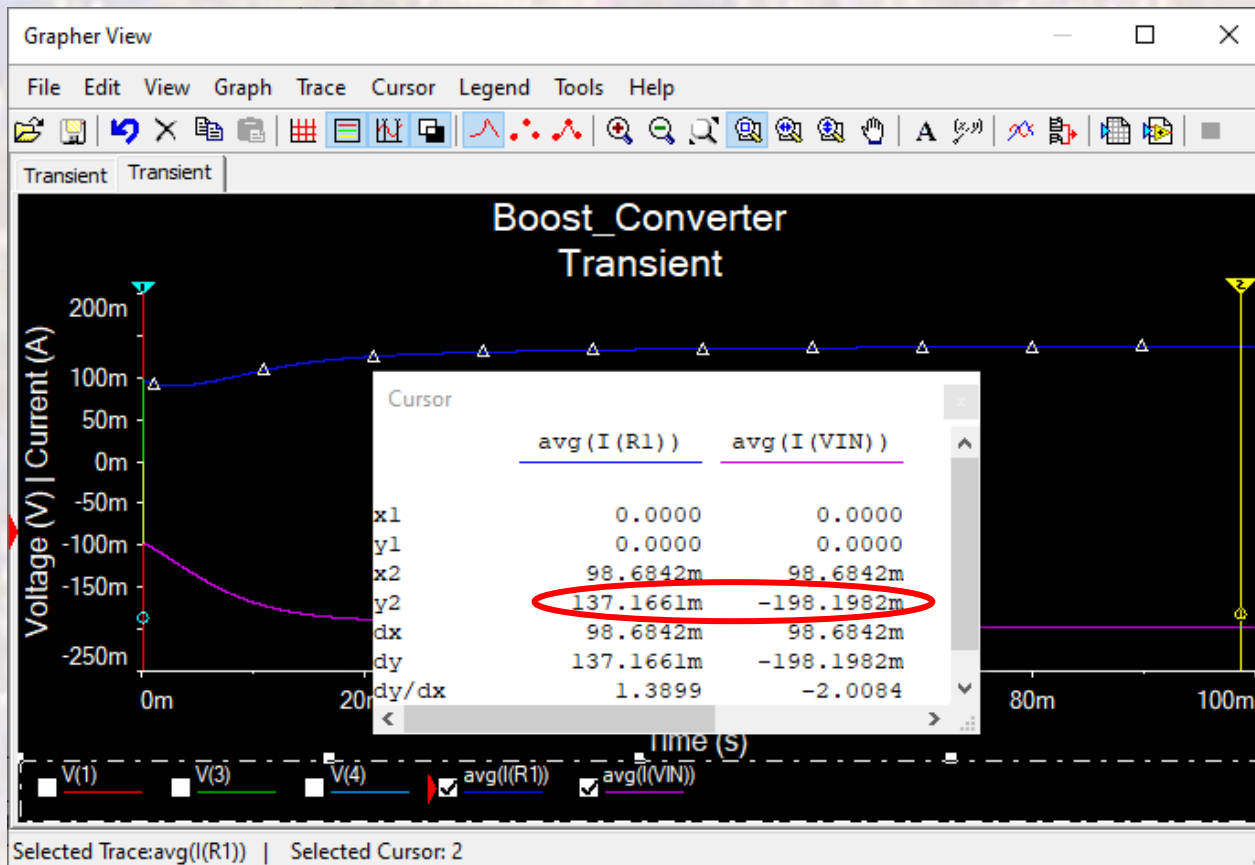- Buck Converter
 - $F_s = 10\text{KHz}$, $D = 0.3$, $L = 147\text{mH}$, $C = 43\mu\text{F}$, $R_L = 70\Omega$
 - $I_{in} = 198\text{mA}$, $I_{out} = 137\text{mA}$



Switched Regulation

- Buck Converter
 - $F_s = 10\text{KHz}$, $D = 0.3$, $L = 147\text{mH}$, $C = 43\mu\text{F}$, $R_L = 70\Omega$
 - $P_{in} = 1.4\text{W}$, $P_{out} = 1.32\text{W} \rightarrow 94.3\%$ efficiency

