

ELE 555  
Spring 2016

Homework 5A

Due 3/8  
Beginning of class

1) Our MIPS pipeline currently has not implemented the barrel shifter from our ALU discussion. Add the barrel shifter to our design and propose a location, inputs, outputs and control signals (do not worry about hazard conditions) and explain your decisions - 30pts

