

ELE 455/555

Computer System Engineering

Section 1 – Review and
Foundations

Class 3 – Technology

Technology

MOSFETs

- MOSFET Terminology
 - Metal Oxide Semiconductor Field Effect Transistor
 - 4 terminal device
 - Source, Gate, Drain, Body
 - Threshold Voltage (V_{th} or V_t)
 - The voltage from gate to source (V_{gs}) required to “turn on” the device
 - R_{on} / R_{off}
 - Device impedance in the “on” or “off” state
 - Leakage Current
 - Parasitic current from junctions to substrate or gate to junctions


Technology

MOSFETs

- MOSFET Terminology

- N-type (N-channel)

 - Forms a conducting n-channel from source to drain
- Requires a positive $V_{gs} > V_{th}$ to form the channel and “turn on” the device





Technology

MOSFETs

- MOSFET Terminology

- P-type (P-channel)

  
- Forms a conducting p-channel from source to drain
- Requires a negative $V_{gs} > V_{th}$ to form the channel and “turn on” the device



Technology

MOSFETs

 
- MOSFET Terminology
 - CMOS
 - Complementary MOS
 - Contains both P-MOS and N-MOS devices
 - Almost all digital circuits today are built using CMOS technology



Technology

CMOS Technology Trends


- CMOS Process Technology
 - Traditionally referenced to the gate length or metal 1/2 pitch
 - 0.25 micron process, 130nm process
 - Over the last 5 years the relationship between reference name and physical parameters has become tenuous
 - Current generation processes are 22nm shifting to 14nm
 - $22\text{nm} = 22 \times 10^{-9} \text{ meters} = 22 \times 10^{-6} \text{ millimeters} = 22 \text{ millionths of a mm}$
 - 1 silicon atom $\sim 5 \text{ angstrom spacing} = 5 \times 10^{-10} \text{m}$
 - $22\text{nm} = 44 \text{ atoms}$
 - Gate oxide thickness is 2nm
 - 4 rows of atoms

 

Technology

CMOS Technology Trends


- Processor Performance

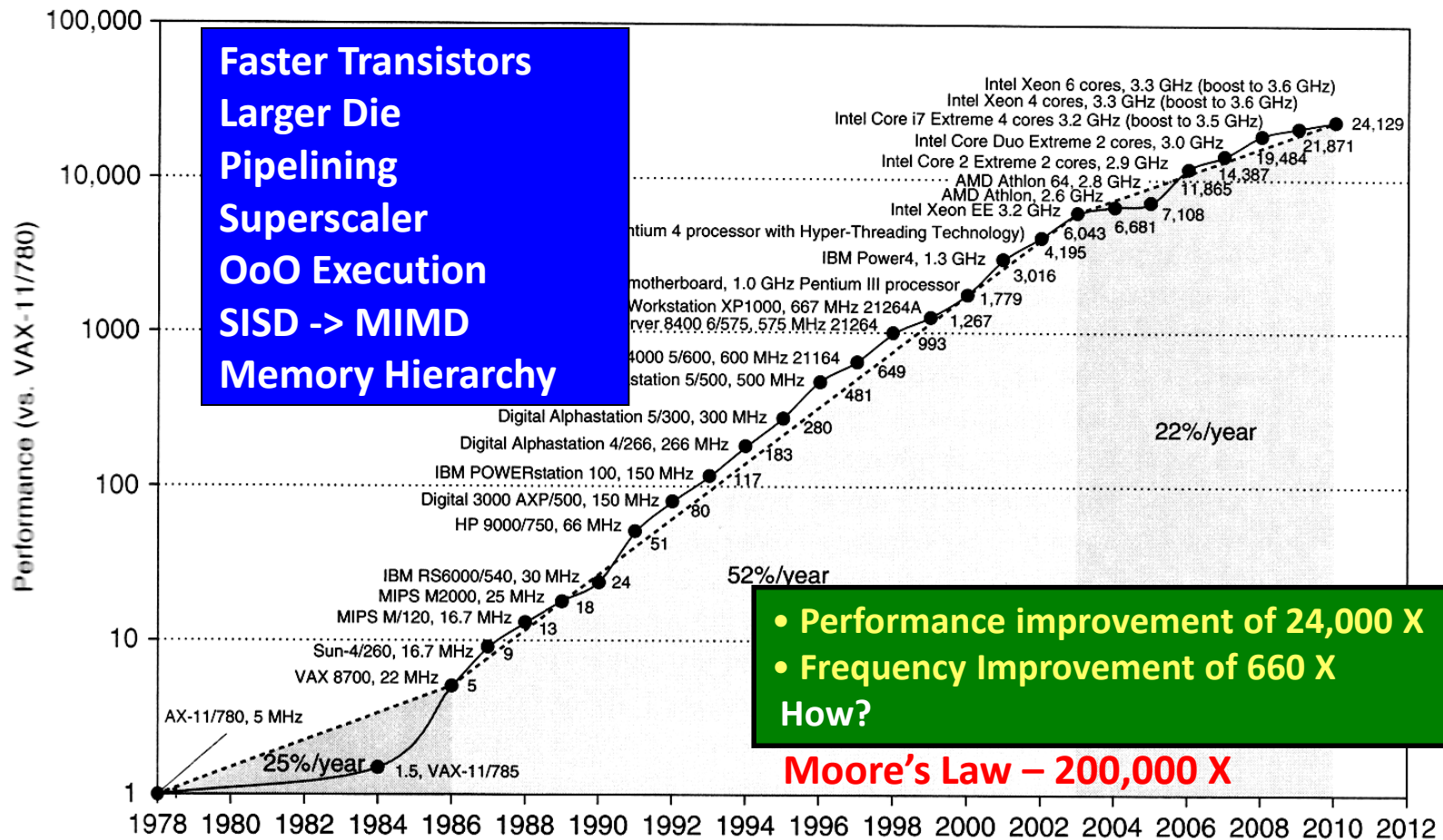

Technology

CMOS Technology Trends


- Transistors per chip

 

Technology

CMOS Technology Trends


- SPECint Performance – single CPU

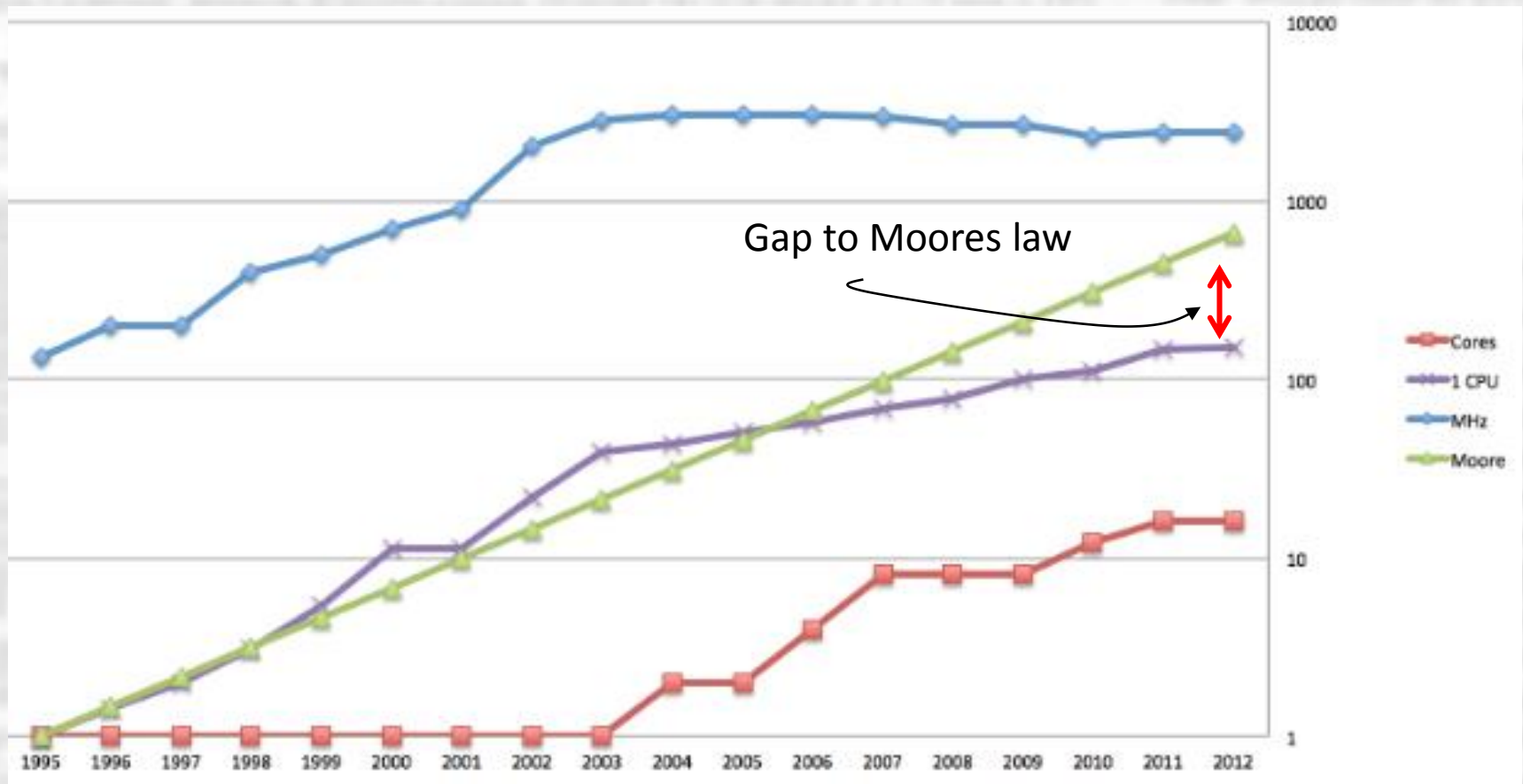

Technology

CMOS Technology Trends

 
- SPECint Performance – Including multi-core



Technology

CMOS Technology Trends

- Half-Pitch Trends

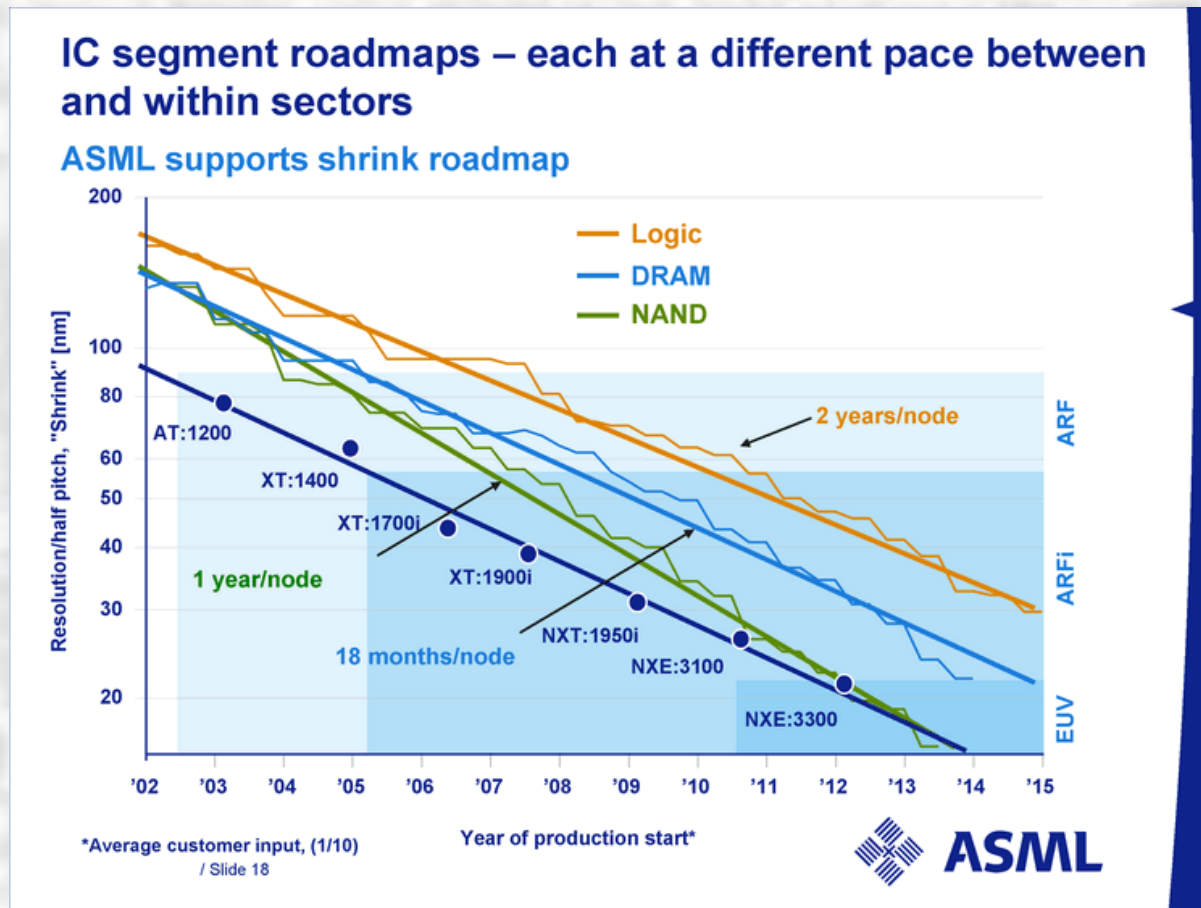

Technology

CMOS Logic




- Simplified CMOS Digital Design
 - Use simplified models for the MOSFETs
 - switch – either “on” or “off”
 - N-MOS devices
 - “on” when a logic **high** is applied to the gate
 - “off” when a logic **low** is applied to the gate
 - P-MOS devices
 - “on” when a logic **low** is applied to the gate
 - “off” when a logic **high** is applied to the gate



Technology

CMOS Logic

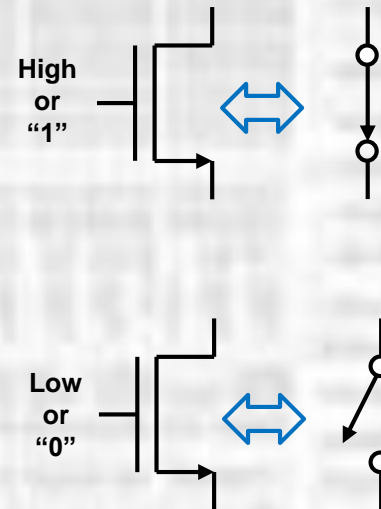  
- Simplified CMOS Digital Design
 - N-MOS devices
 - “on” when a logic **high** is applied to the gate
 - “off” when a logic **low** is applied to the gate





Technology

CMOS Logic

 - Simplified CMOS Digital Design
 - P-MOS devices
 - “on” when a logic **low** is applied to the gate
 - “off” when a logic **high** is applied to the gate



Body Connection
is assumed Vdd

  




Technology

CMOS Logic

- Simplified CMOS Digital Design

- CMOS Inverter

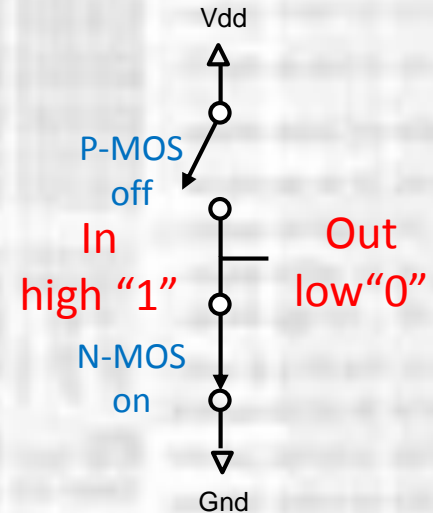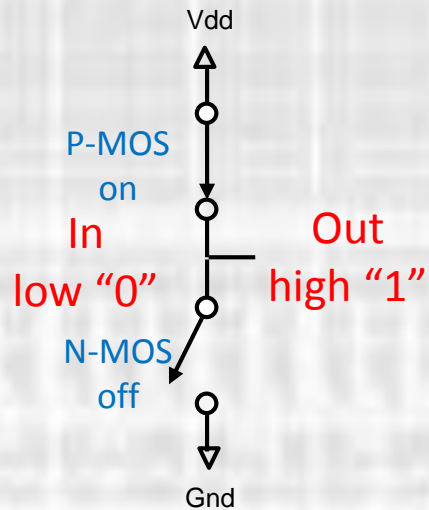 - logic low "0" is Gnd
- logic high "1" is Vdd








Technology

CMOS Logic

- Simplified CMOS Digital Design

A	B	Out
0	0	1
0	1	1
1	0	1
1	1	0

- CMOS Nand Gate

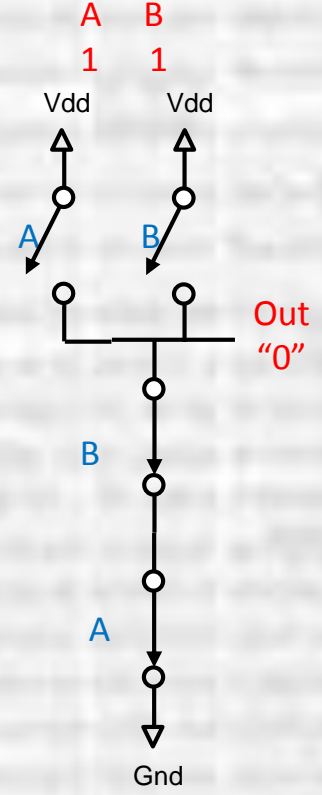    




Technology

CMOS Logic

- Gate Level Performance

- DC Characteristics

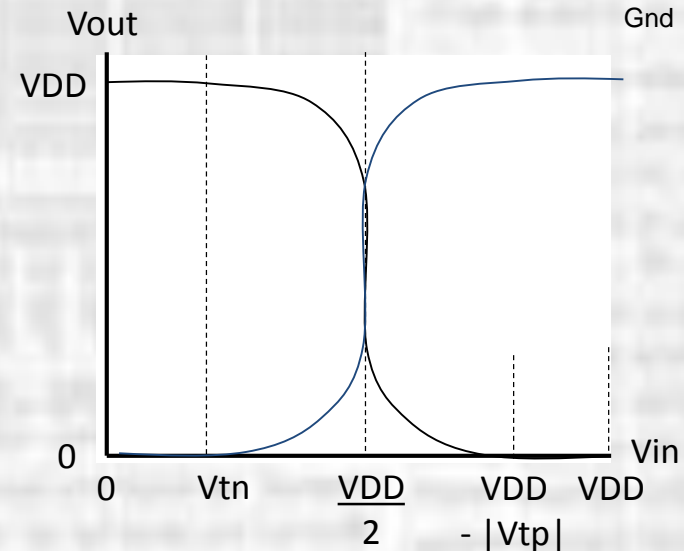 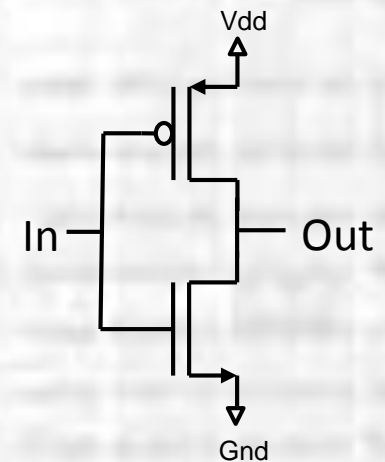- $I_{DS} = \beta[(V_{GS} - V_t)V_{DS} - V_{DS}^2/2]$ - linear region
- $I_{DS} = \beta/2 (V_{GS} - V_t)^2$ - saturated region
- $\beta = \frac{\mu\epsilon W}{t_{ox} L}$ $\beta_n \cong 2.8\beta_p$



Technology

CMOS Logic

- Gate Level Performance

- Transient Characteristics



- Equalize t_r and t_f by making $W_p \cong 2.8 W_n$

- $t_r \cong t_f \cong K_n \frac{C_L}{\beta_n V_{DD}} \cong K_p \frac{C_L}{\beta_p V_{DD}}, \quad K_n \sim K_p \sim 3.5$

- $t_d \cong t_r/2 \cong t_f/2$

- Optimize delay

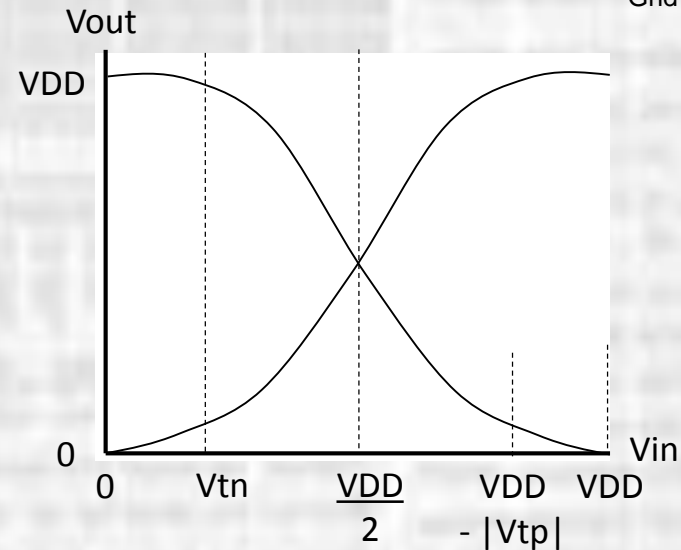 
- reduce C_L
- increase V_{DD}
- increase $\beta \rightarrow$ reduce t_{ox}
 - why might this be the best approach?



Technology

CMOS Logic

 
- Gate Level Power
 - 3 primary components of gate level power
 - Static Power (leakage)
 - Dynamic Power (CV^2F)
 - Short Circuit Power (shoot-through)



Technology

CMOS Logic

- Gate Level Power
 - Static Power
 - Leakage currents through the reverse biased diode junctions – always present
 - Sub-threshold current – current from S-D when the input voltage is below V_t – due to voltage drops
 - Gate leakage current – current from the gate to S/D/Body – due to oxide defects or quantum tunneling
 - Design Considerations
 - Multiple V_t devices
 - Thick oxide devices
 - Reduce supply voltages – why?

 

Technology

CMOS Logic

- Gate level Power

- Dynamic Power

- Power associated with slewing the load capacitance

- $E = \int P dt = \int IV dt = \int C \frac{dv}{dt} V dt = \int CV dv = \frac{CV^2}{2}$


- energy per transition = $C_L V_{dd}^2 / 2$

- Power is energy / time

- $P_{dynamic} = CV^2 f$

- Design considerations

 - Run circuits at the lowest possible speed
 - Reduce supply voltages
 - Minimize capacitance



Technology

CMOS Logic

- Gate Level Power

- Short Circuit Power

- Both devices are on



- Symmetrical gate →

$$P_{sc} \cong \frac{\beta}{12} (V_{DD} - 2V_t)^3 f t_{rf}$$

- Design Considerations

- large relative loads → lower Psc
 - small relative loads → higher Psc
 - Match t_r and t_f through the chain

- Reduce supply voltages

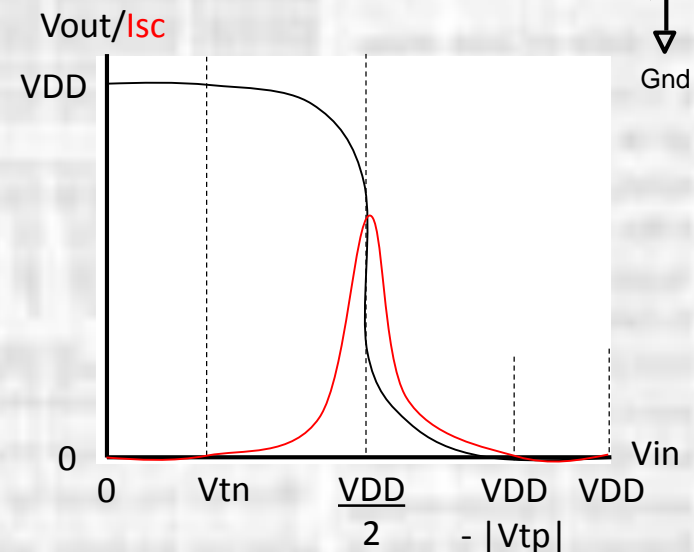 

Technology

CMOS Integrated Circuits

- Chip Level Considerations
 - Millions to hundreds of millions of gates
 - Physical Space
 - Sheer numbers of gates
 - Keeping shared resources close to multiple users (memory)
 - I/O pin access and placement
 - Interconnect – getting all the wires connected
 - Typical processes have 6 – 10 layers of interconnect
 - Cell, local, global, power
 - Performance
 - Power / Heat Dissipation

Technology

CMOS Integrated Circuits

- Chip Level Considerations
 - Performance Drivers
 - Process Technology
 - Transistor performance
 - Short channel vs. long channel devices
 - High V_t and Low V_t devices
 - Clock Frequency
 - Maximum is set by the longest unit delay
 - Very complex timing tools used to ensure max frequency
 - Interconnect
 - RC delays
 - Capacitive coupling

Technology

CMOS Integrated Circuits

- Chip Level Considerations
 - Power Drivers
 - Process Technology - Dynamic, Static, Short circuit (D/S/SC)
 - Number of gates – D/S/SC
 - Clock Frequency – D/SC
 - Dynamic power becomes CV^2f , where f is clock frequency
 - Short circuit power is also multiplied by f
 - Supply Voltage – D/S/SC
 - Routing Efficiency – D/SC
 - Minimizing capacitance is critical

Technology

CMOS Integrated Circuits

- Chip Level Considerations
 - Power / Performance Balance
 - Device Level Solutions
 - Multiple V_{th} devices
 - Low V_{th} devices for high performance paths
 - High V_{th} devices for low performance paths
 - Chip Level Solutions
 - Reduced interconnect R and C
 - Power islands – gating the power to circuits not in use
 - Clock Gating – turn off the clocks to circuits not in use

Technology


CMOS Integrated Circuits

- Chip Level Considerations
 - Power / Performance Balance
 - System Level Solutions
 - Dynamic Voltage Scaling – changing VDD as needed
 - Dynamic Frequency Scaling – changing the clock frequency as needed
 - Together these are referred to as DVFS
 - Architectural Solutions
 - Pipelining
 - Multi-core processors
 - Homogeneous – dual/quad core
 - Heterogeneous – big/little
 - Memory Hierarchy

Technology

CMOS Integrated Circuits


- Power – Performance Tradeoffs

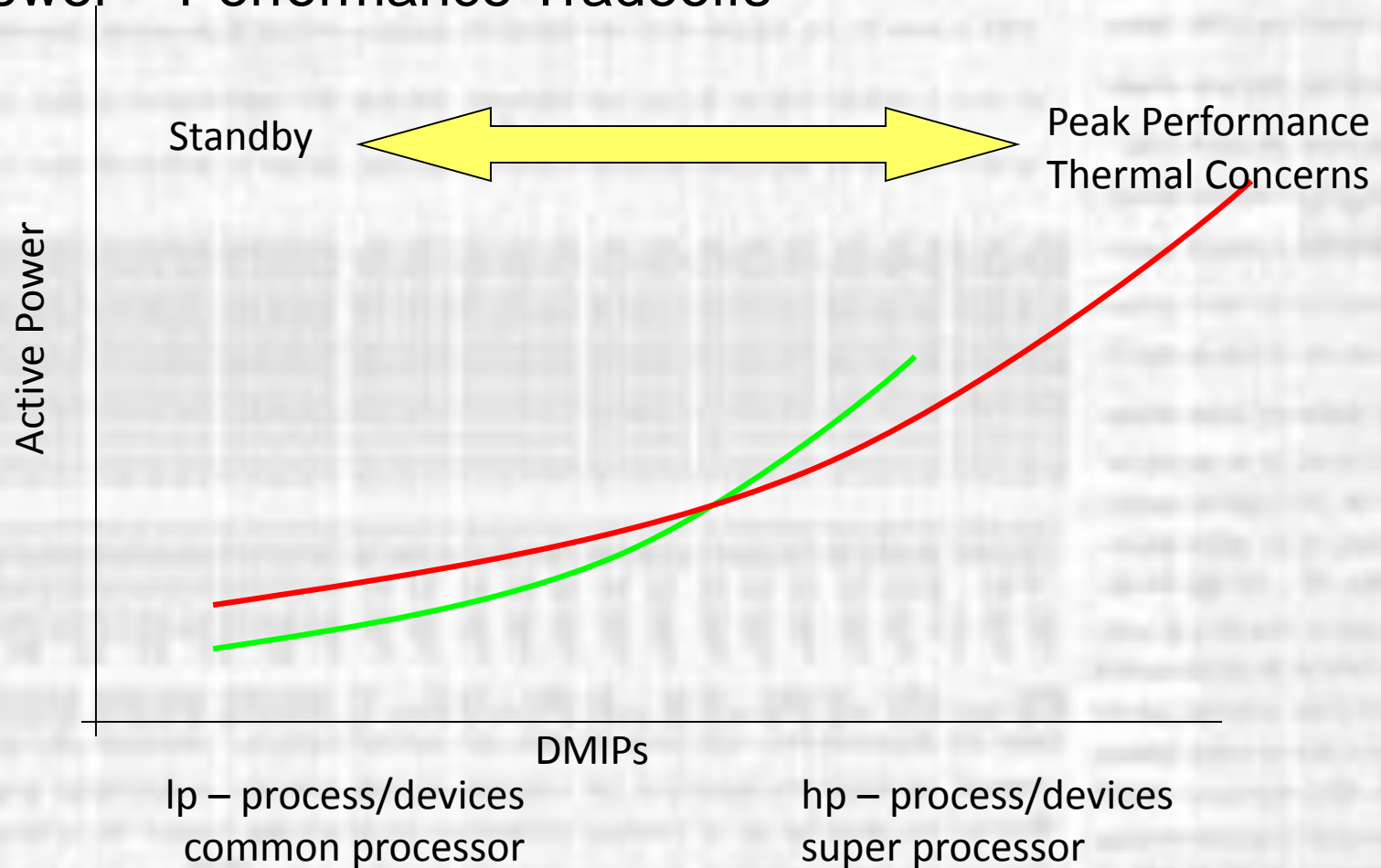

Technology

CMOS Integrated Circuits


- Power – Performance Tradeoffs

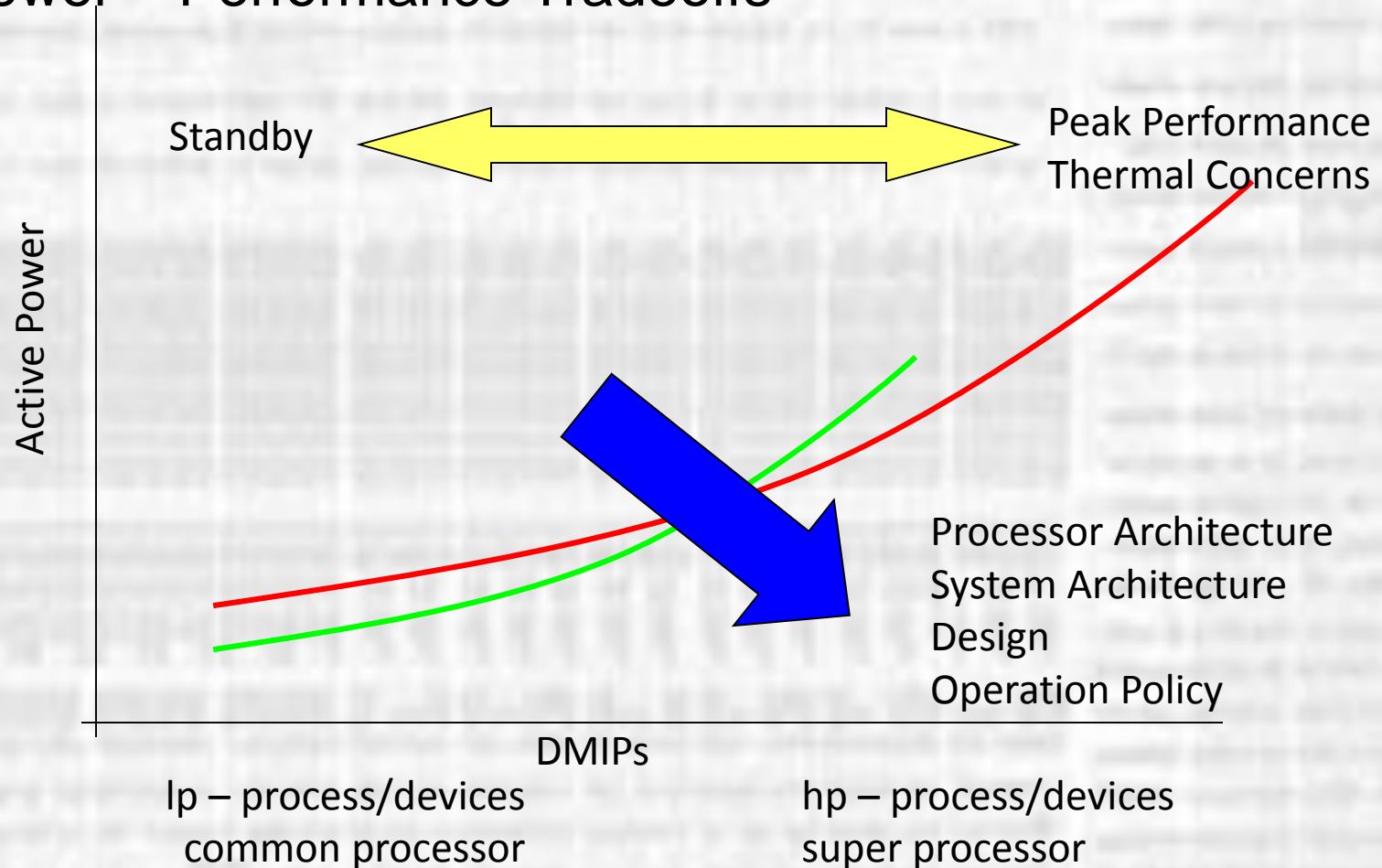

Technology

Memory


- Memory Taxonomy

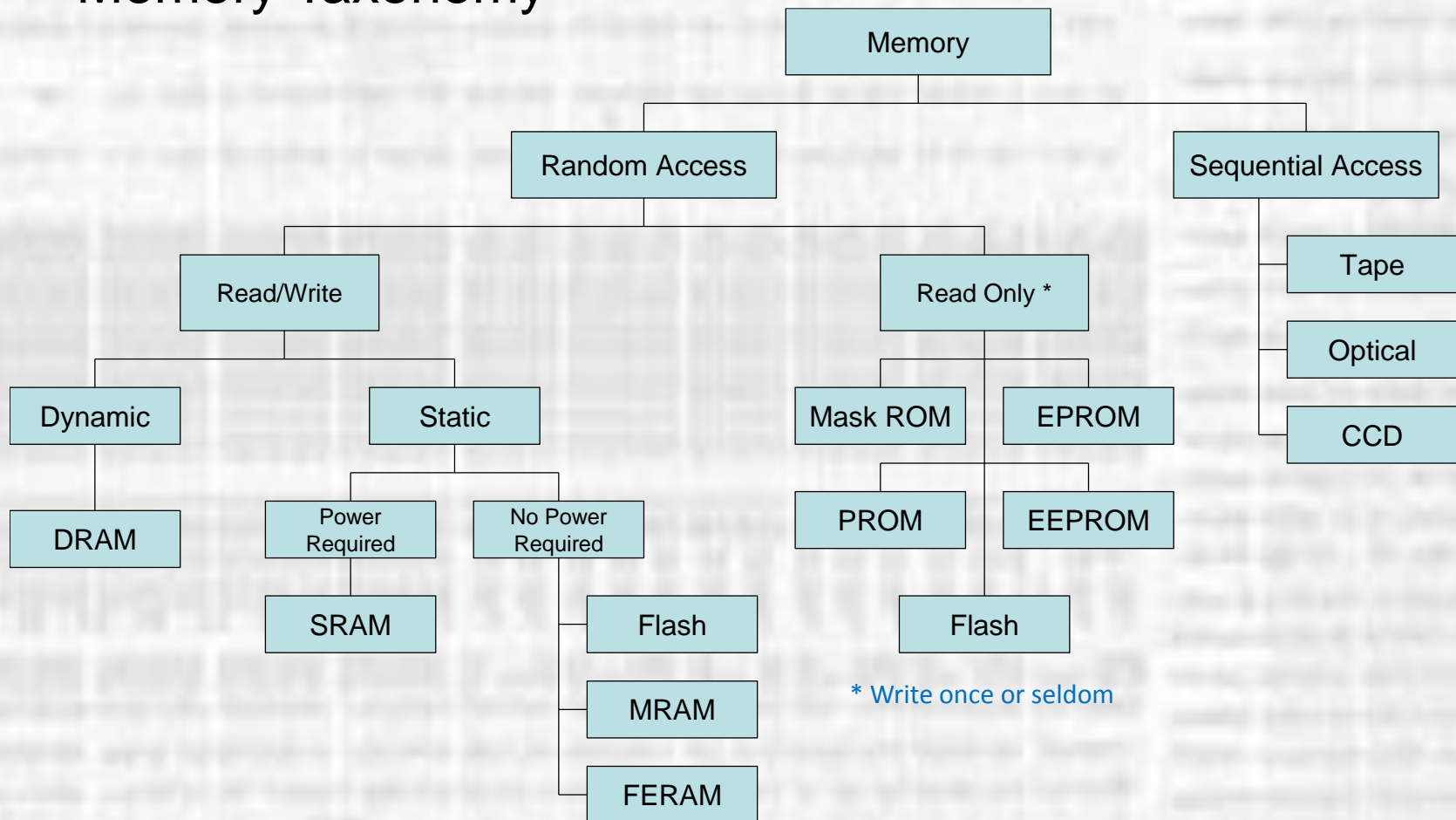

Technology

Memory

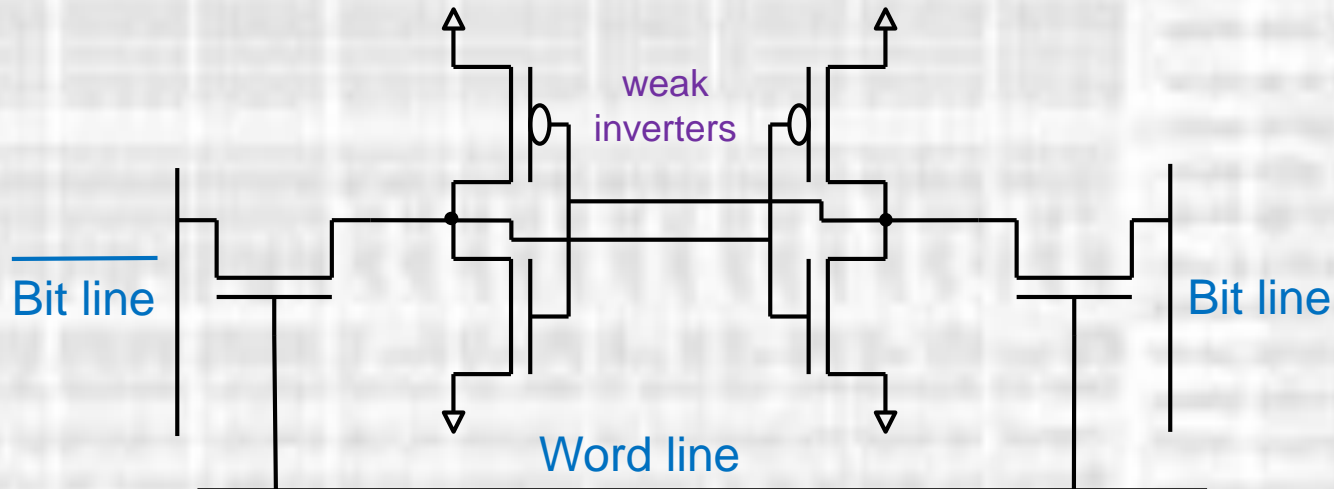- SRAM – Static Random Access Memory
 - Memory cell (1 bit) is based on a feedback circuit
 - Bit value is retained as long as power is maintained
 - Fastest read/write (R/W)
 - Highest power
 - Lowest density
 - Used in caches and small data memories





Technology

Memory

- SRAM – Static Random Access Memory

- Write

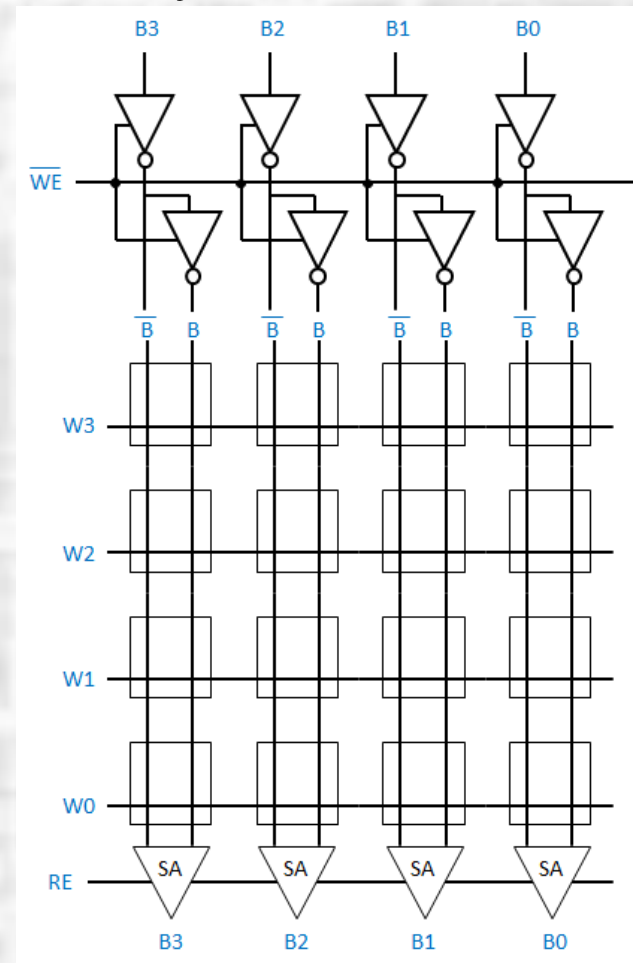 - All Word lines low
 - Read Enable (RE) disabled (low)
 - Place B0, B1, B2, B3 on inputs
 - Pull write enable bar (\overline{WE}) low
 - Strobe the desired word line high
-
- Bit lines override the bit cell inverters and store the new value in the cell





Technology

Memory

- SRAM – Static Random Access Memory

- Read

 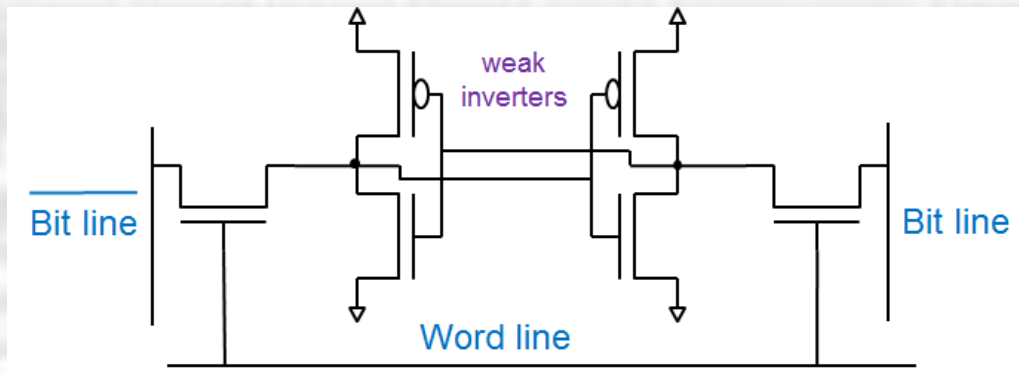
- All Word lines low
 - Write enable bar (\overline{WE}) high
 - inverters tristated
 - Read Enable (RE) high
 - Strobe the desired word line high
-
- Bit cell inverters drive the bit lines and sense amplifiers read the value



Technology

Memory



- SDRAM – Synchronous Dynamic Random Access Memory
 - Memory cell (1 bit) is based on capacitor charge storage
 - Bit value decays over time
 - must be recharged – called a refresh cycle
 - Standard SDRAM transfers 1 word each clock cycle
 - DDR – double data rate – transfers 2 words each clock cycle
 - DDR2, DDR3, DDR4 – transfer 4,8,16 words each array access
 - Medium speed
 - Highest density
 - Used as main memory

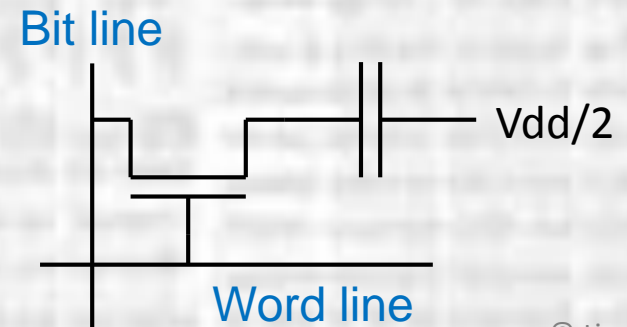

Technology

Memory

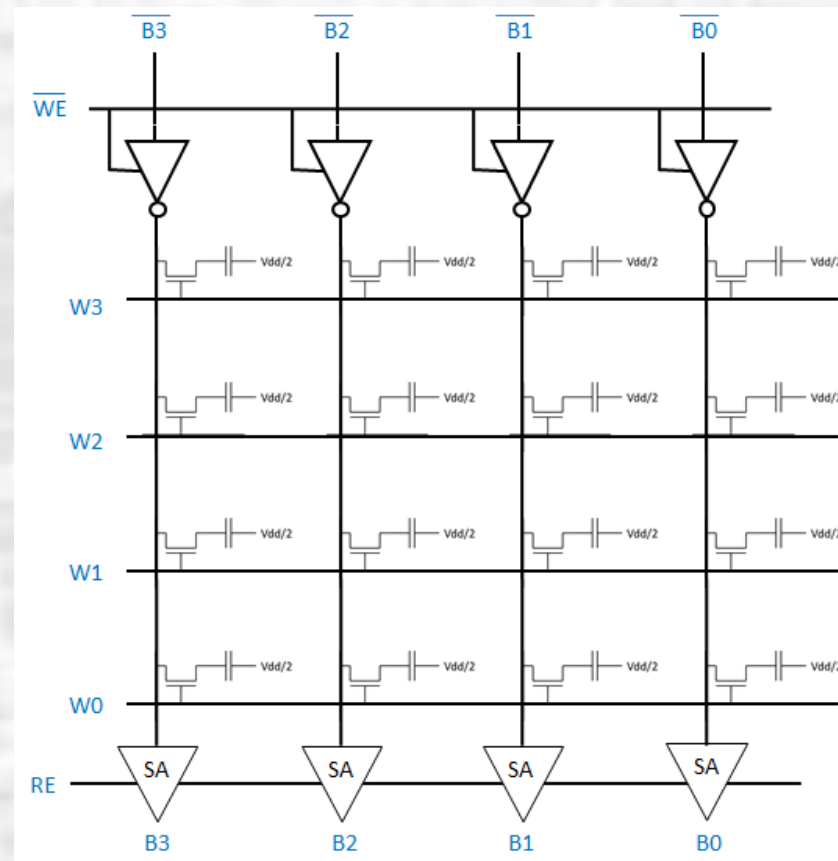 
- SDRAM – Synchronous Dynamic Random Access Memory
 - Read
 - All Word lines low
 - Write enable bar (WE) high
 - inverters tristated
 - Read Enable (RE) high
 - Strobe the desired word line high
 - Sense amplifiers read the value of the capacitors



Technology

Memory



- ROM – Read Only Memory
 - Memory cell (1 bit) is based on whether a MOSFET is or is not connected between the bit line and word line
 - The MOSFET structure is always part of the bit cell
 - It can be connected to the bit line through a contact or via (via ROM)
 - It can be disabled by removing the S/D diffusion (diffusion ROM)
 - Cannot be modified once the part is built
 - Typically used as Boot memory or to hold chip configuration data

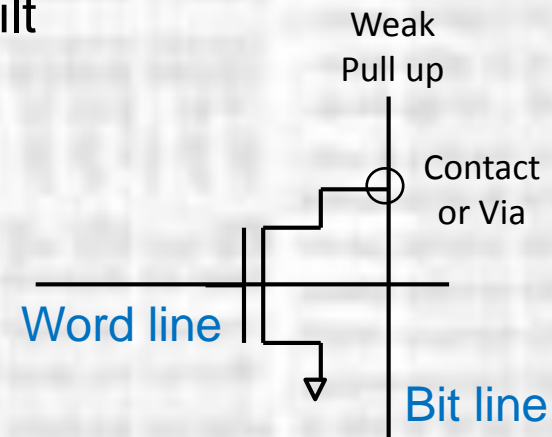

Technology

Memory

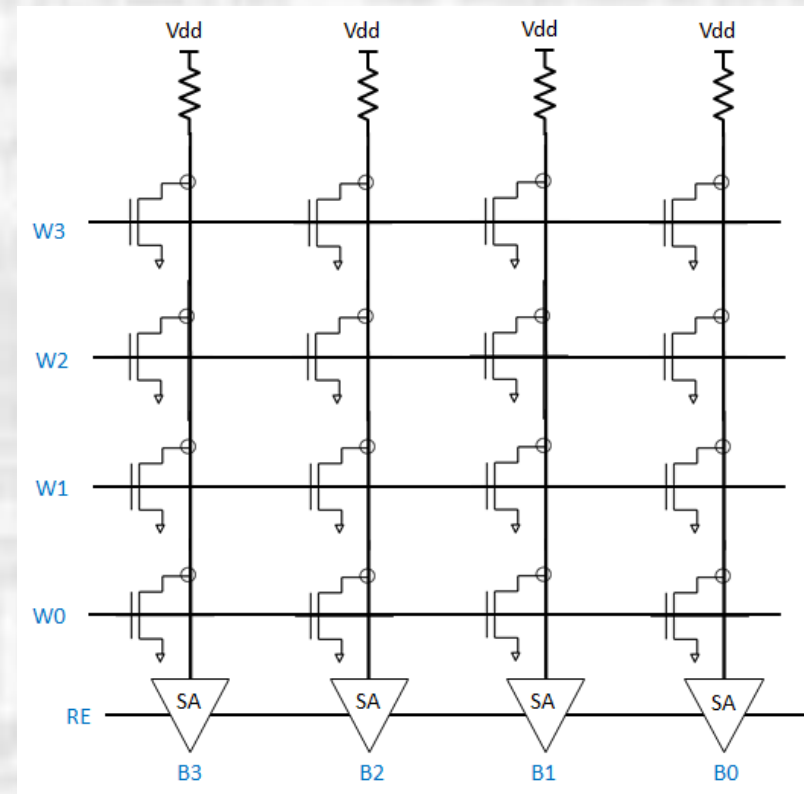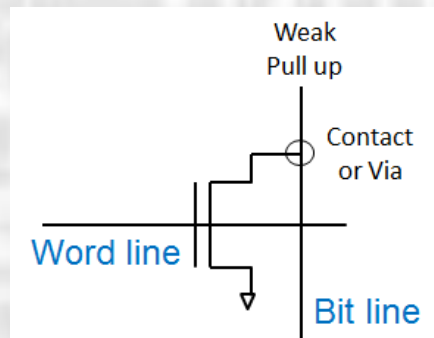- ROM – Read Only Memory
 - Read
 - All Word lines low
 - Read Enable (RE) high
 - Strobe the desired word line high
 - Sense amplifiers read the value of the bit lines
 - If connected – will read a “0”
 - If not connected – will read a “1”





Technology

Memory

- Flash Memory

- Memory cell (1 bit) is based on charge stored on a floating capacitor
 - The capacitor modifies the threshold voltage of a MOSFET
 - with negative charge stored – need higher gate voltage to turn on the MOSFET
 - Creates 2 possible threshold voltages
 - $V_{th \text{ High}}$ is required to turn on the MOSFET if charge is stored
 - $V_{th \text{ Low}}$ is required to turn on the MOSFET if no charge is stored

  

Technology

Memory


- Flash Memory

- Cell write

- High voltage process that allows electrons to be injected into (erase) or tunnel out of (write) the floating gate
- Once the high voltage is removed the electrons are trapped

- Cell read

 - Place a voltage on the gate midway between $V_{th\ High}$ and $V_{th\ Low}$
- Use the circuit to determine if the MOSFET is on or off




If charge stored on capacitor (erased)
 $V_{th\ mid} < (V_{th} = V_{th\ High}) \rightarrow V_{out} = \text{high} \rightarrow \text{"0"}$

If no charge stored on capacitor (programmed)
 $V_{th\ mid} > (V_{th} = V_{th\ Low}) \rightarrow V_{out} = \text{low} \rightarrow \text{"1"}$

Technology

Memory

 
- Flash Memory
 - NOR Flash
 - Block Erase
 - Less dense than Nand Flash (extra wires and connections)
 - Slower sequential access than Nand Flash
 - **Fast (true) random access**
 - Used as program memory



Technology

Memory

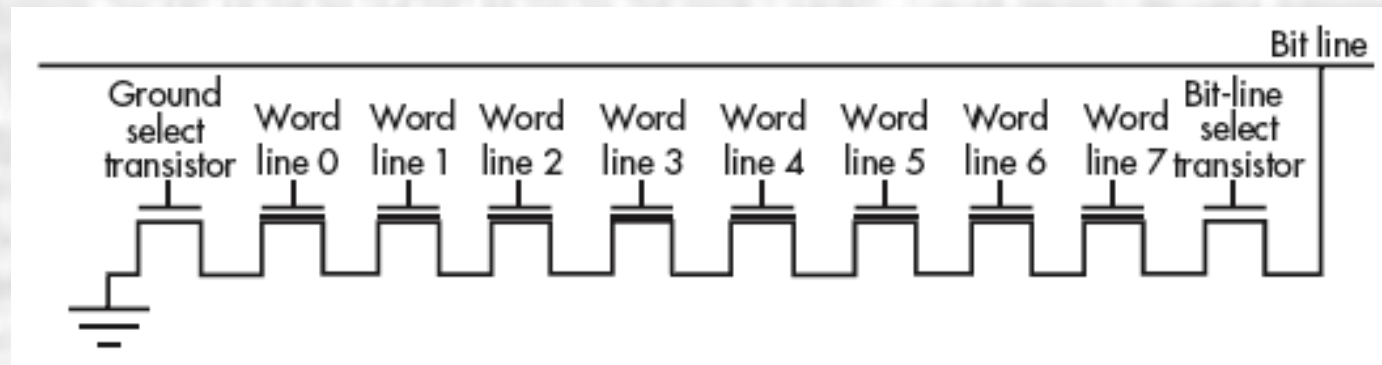
- Flash Memory
 - NAND Flash
 - Block Erase
 - **More dense than Nor Flash**
 - Faster sequential access than Nor Flash
 - Random access requires additional parts and time
 - Used as file storage memory (Flash Drives)



Technology

Memory

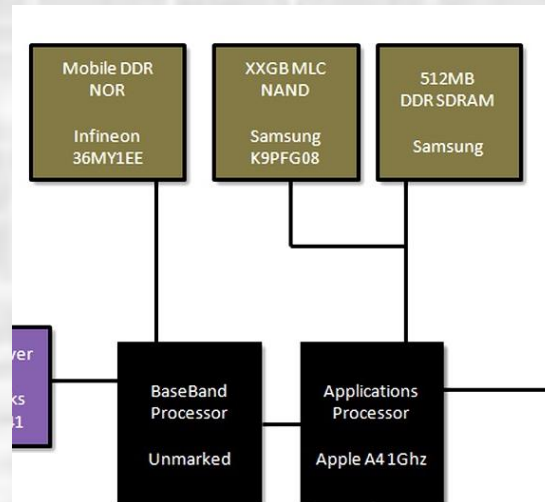- Flash Memory
 - Shadowing
 - Store large amounts of program and data in Nand Flash
 - At boot, copy a portion of the Nand memory into SRAM or SDRAM
 - Use the SRAM as the processor program and data memory
 - As additional program or data are needed – swap out a portion of the SRAM/SDRAM



Technology

Memory

- Flash memory
 - XIP – Execute in Place
 - Execute directly out of NOR flash
 - Nor Flash densities are growing rapidly
 - Nor Flash speeds are fast enough to support the memory hierarchy
 - Requires a caching system

Technology

Memory

- Access
 - Many variations, but all basically the same
- Two Buses
 - Address Bus
 - Address width (# of bits) is $\log_2 m$ where m is the number of memory locations
 - Uni-directional – only written by processor, read by memory
 - Data Bus
 - Data width (# of bits) is set by the memory/system interface
 - Bi-directional – both memory and processor can R/W this bus
- 3 Control Signals
 - Chip Enable
 - Used to choose one of several possible memory devices
 - Read
 - Asserted by the processor to signal a read operation
 - Write
 - Asserted by the processor to signal a write operation

Technology



Memory

- Access
 - Simplified Process
- Read
 - Processor selects the appropriate CE
 - Processor places the desired read address on the address bus
 - Processor asserts the read signal
 - Memory fetches the data and places it on the data bus
 - Processor reads the data bus
- Write
 - Processor selects the appropriate CE
 - Processor places the desired write address on the address bus
 - Processor places the data on the data bus
 - Processor asserts the write signal
 - Memory reads the data on the data bus and stores it

Technology

Packaging



- Ball Grid Array

  

Technology



Packaging

  - Ball Grid Array
 - Bonded vs. Flip Chip




Technology Packaging

- Stacked Package

 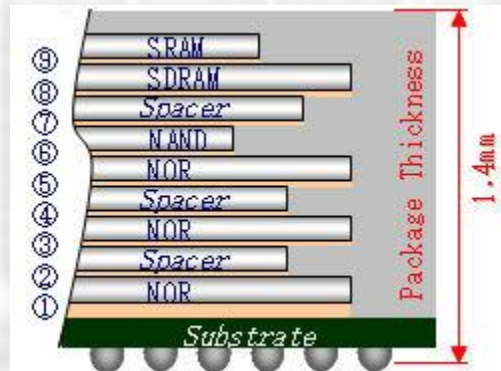

Technology Packaging

- PoP Package

 

Technology

Packaging

- Silicon Through Via Package

