

NAME: _____

ITEM	DEMO ON TIME	GRADING POINTS
UPDOWN2 counter: state machine diagram		___ / 1
UPDOWN2 counter: truth tables		___ / 1
UPDOWN2 counter: equation derivation for D1		___ / 1
UPDOWN2 counter: equation derivation for D0		___ / 1
UPDOWN2 counter: Quartus schematic with neatness and visual line		___ / 1
UPDOWN2 counter: Quartus simulation showing rst, up, and down behaviors		___ / 1
GRAY3 counter: state machine diagram		___ / 1
GRAY3 counter: equation derivations		___ / 1
GRAY3 counter: Quartus schematic with neatness and visual line		___ / 1
GRAY3 counter: Quartus simulation showing rst and up behavior.		___ / 1
TOTAL		___ / 10 = _____ %

- **Print** this coversheet and attach it to the top of your **laboratory submission packet**.
- **Packets** must always include:
 - **Design files:** blueprints, VHDL, synthesis generates RTL diagrams
 - **Test files:** simulation waveforms, oscscope photos, and photos of any built circuits.
- **Submit by:** 5:00 p.m. one academic day after your laboratory period.
One academic day after Friday is Monday.
- **How to submit (choose one):**
 - **Pin** to Dr. Meier's office bulletin board (L-349).
 - **Slide** under Dr. Meier's office door (L-349).
 - **Hand** to Dr. Meier if he is in his office (L-349).
 - **Put** in Dr. Meier's mailbox (L-350).