

# Linear Circuits

SE3910 – Lab 2

Name: \_\_\_\_\_

Date: \_\_\_\_\_

Spring 2015

Milwaukee School of Engineering (MSOE)

Electrical Engineering and Computer Science (EECS)

Instructor: Dr. Josiah Yoder


## Introduction

---

### Circuit 1
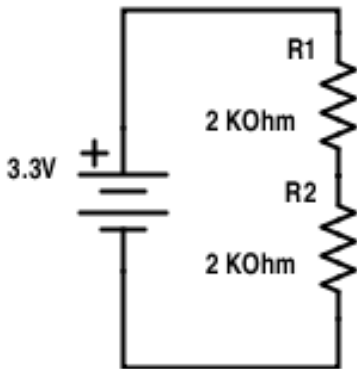
#### Prelab – Analyze Circuit

Label the circuit below with the voltage across and current through each component. You may do the analysis on the side




#### In Lab – Measure Voltage

Measured: R1: \_\_\_\_\_ R2: \_\_\_\_\_

### Circuit 2
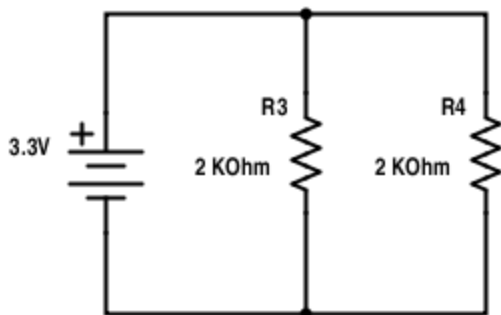
#### Prelab – Analyze Circuit

Label the circuit below with the voltage across and current through each component. You may do the analysis on the side




#### In Lab – Measure Voltage

Measured: R3: \_\_\_\_\_ R4: \_\_\_\_\_

### Circuit 3
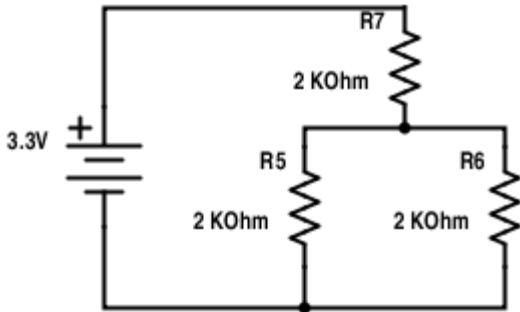
#### Prelab – Analyze Circuit

Label the circuit below with the voltage across and current through each component. You may do the analysis on the side




#### In Lab – Measure Voltage

Measured: R5: \_\_\_\_\_ R6: \_\_\_\_\_ R7: \_\_\_\_\_

### Circuit 4
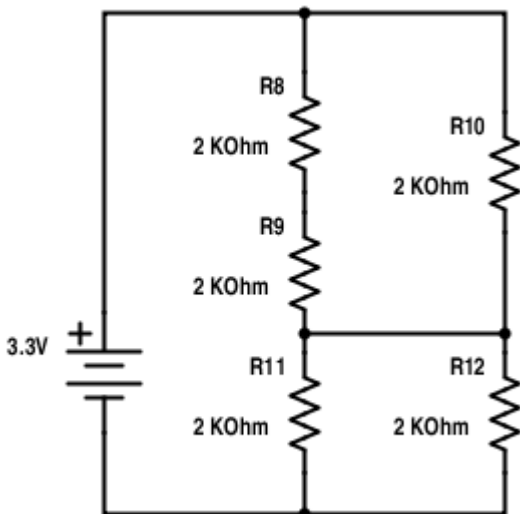
#### Prelab – Analyze Circuit

Label the circuit below with the voltage across and current through each component. You may do the analysis on the side




#### In Lab – Measure Voltage

Measured: R10: \_\_\_\_\_ R12: \_\_\_\_\_

### Circuit 5
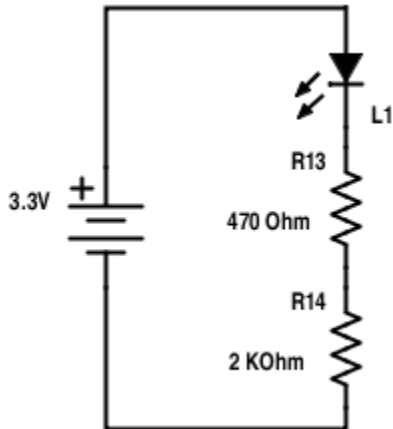
#### Prelab – Analyze Circuit

Label the circuit below with the voltage across and current through each component. You may do the analysis on the side



#### In Lab – Measure Voltage


Measured: R14: \_\_\_\_\_ (EC: V needed for 20mA: \_\_\_\_\_)

*Please check* with a full analysis that any voltages you apply will not damage the LED. You may also want to turn up the supply slowly.)

### Circuit 6
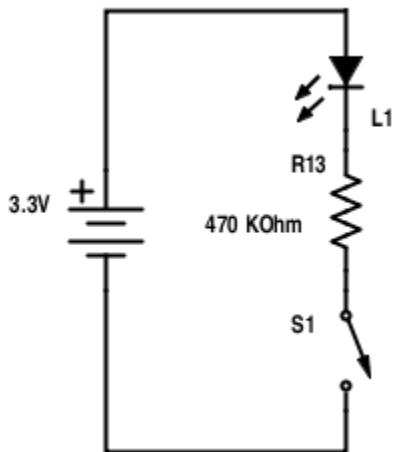
#### Prelab – Analyze Circuit

Label the circuit below with the voltage across and current through each component. You may do the analysis on the side




#### In Lab – Measure Voltage

Measured: S1 closed: \_\_\_\_\_ S1 open: \_\_\_\_\_

### Circuit 7
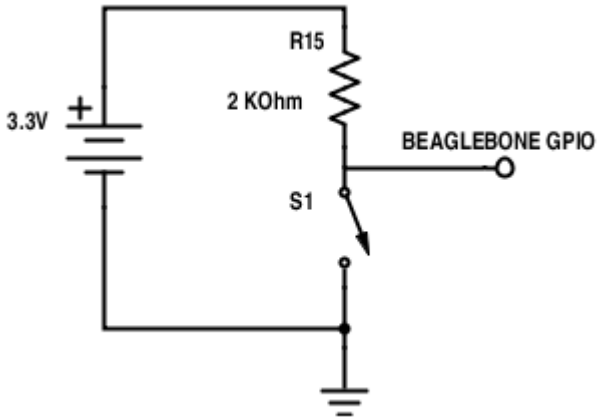
#### Prelab – Analyze Circuit

Label the circuit below with the voltage across and current through each component. You may do the analysis on the side



#### In Lab – Measure Voltage


Measured: GPIO open: \_\_\_\_\_ GPIO closed: \_\_\_\_\_

### Circuit 8
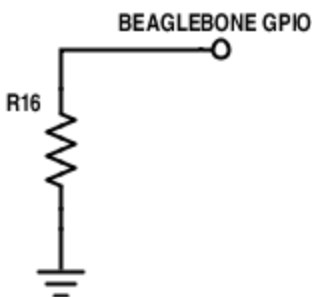
#### Prelab – Analyze Circuit

The minimum resistance for R16: \_\_\_\_\_

*Show work and explain why* this is a minimum resistance rather than a maximum resistance.



#### In Lab – Don't Confirm your predictions! 😊

(Nothing required)

### *In-Lab Observations*

[You can write these on the previous pages if desired. You must write SOME in-lab observations, and you may wish to summarize them here. I do not expect you to fill this space.]

---

### *Analysis and Conclusions*

[Write your explanations for observations here. I do not expect you to fill this space.]

---

*Comments on the Lab, Positive or Negative [Required]*