MSOE EECS Department CE-1911: Week 3 Lab Grading Checklist Dr. Yoder Name:

Item	Points
3-bit up/down locking counter state diagram	/ 2
3-bit up/down locking counter truth table	/ 2
3-bit up/down locking counter Quartus schematic	/ 2
3-bit up/down locking counter simulation. Whenever you print	/ 2
out a simulation result, be sure to mark it up to demonstrate that	
it meets the requirements. Draw arrows to where you would	
point while describing it to me, and hand-write text explaining	
how that part of the simulation result demonstrates that the	
circuit meets the requirements.	
3-bit up-even/down-odd counter state diagram	/ 2
3-bit up-even/down-odd counter truth table	/ 2
3-bit up-even/down-odd counter Quartus schematic	/ 2
3-bit up-even/down-odd counter simulation. Be sure to annotate	/ 2
this simulation using the instructions above.	
Demonstrate the simulations on your screen during the lab	/ 2
period.	
Following Submission Instructions	/ 2
Total	/ 20

- **Staple** this lab cover sheet on top of all the materials you are submitting.
- In addition to the materials above, submit any other supporting materials you create while working the lab (sketches, truth-tables, etc.) where they fit best in your report.
- Submit your work in the *order* listed above.
- Your demo is due during the lab period. Your lab packet is due by 9 AM on the day after the lab
 is performed. You may do your (late) demonstration after submitting your lab packet if
 necessary. There is a 1 point per day late penalty on the demo. The maximum late penalty for
 the report+demo per day is 2 points. Slip your submitted lab packet under my office door or
 submit your packet to me during the laboratory.